
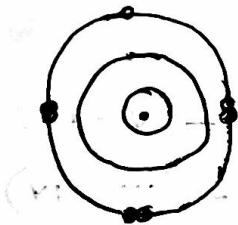


Atomic Structure :

Bohr's atomic model

Bohr's model

Quantum mechanics

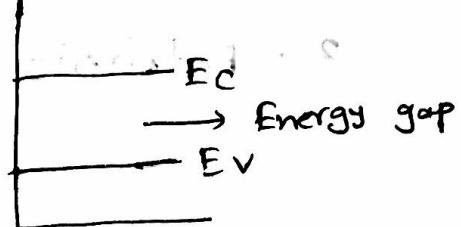


\* Valence band  $\rightarrow$  conduction band's definition

Classification of solid based on Energy gap (Picture)

1. Insulator


2. Semi-conductor

3. Conductor

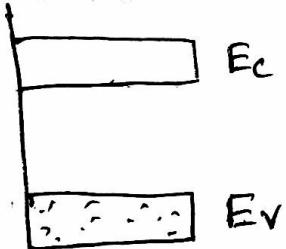


$$Eg \approx 1.1 \text{ eV}$$

(Si)

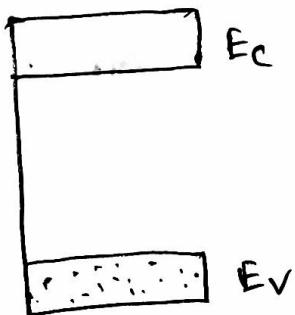

$$Eg > 10 \text{ eV}$$


(OK)

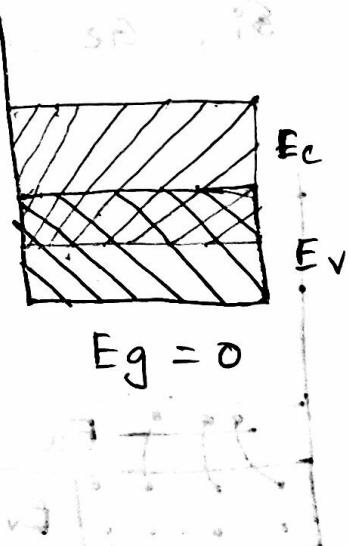

$$Eg = 0$$

## \* Semi-Conductor :

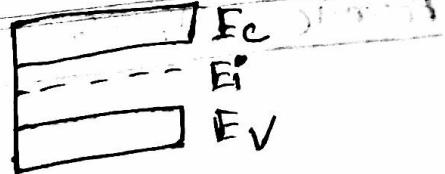1. Intrinsic Material  
 2. Extrinsic Material  
 No. term  $\rightarrow$



Material



$$\rightarrow N \text{ type} : -(V - I^N)$$

$$\rightarrow P \text{ type} : (I^{III} - I^N)$$


silicium eind mettende



Si eind op band kloof

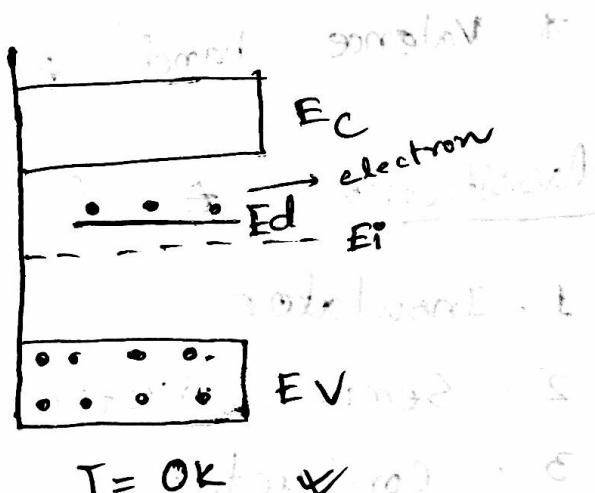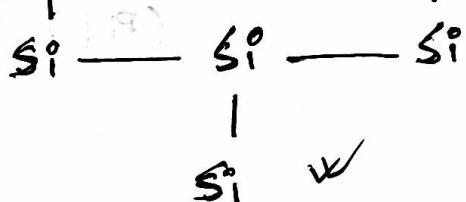


Si, Ge, Ga

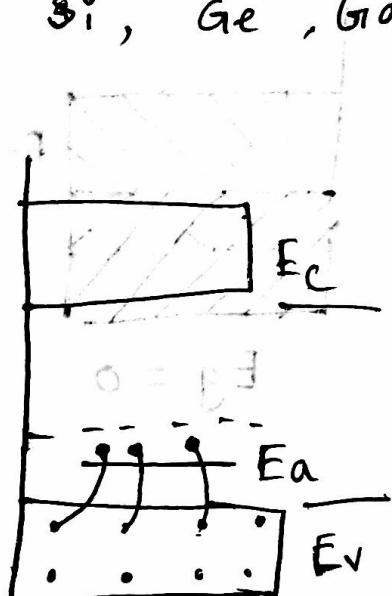




Energy Gap/  
forbidden Energy  
Gap

$$T = 0K$$



$$T = 50K$$

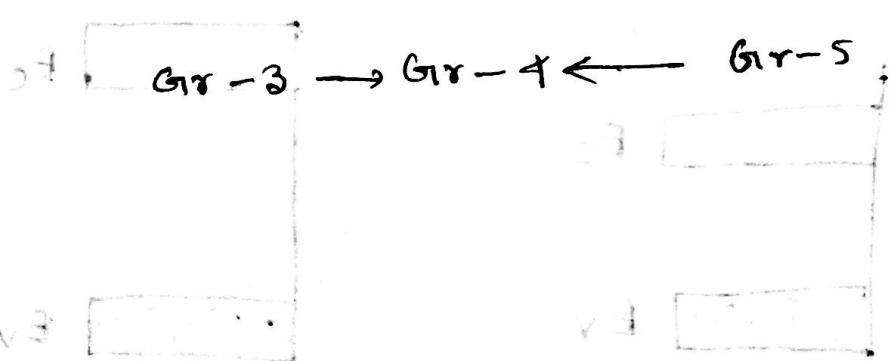

$V_{0.13} \text{ eV}$   
(1e)

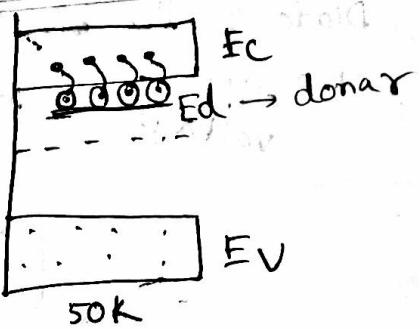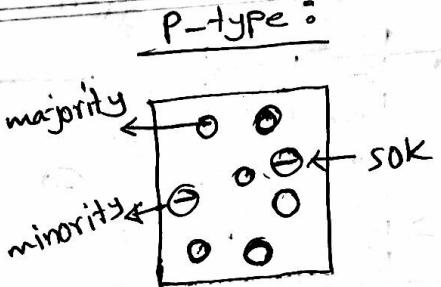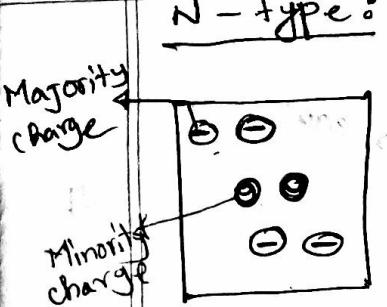

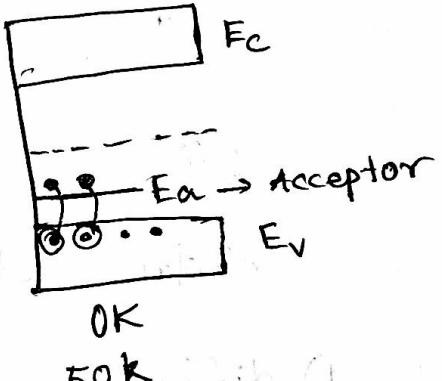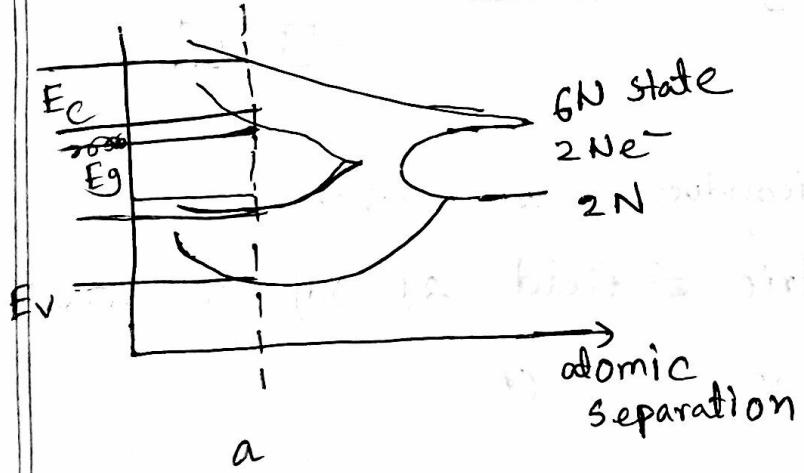\* OK සිල්ඩ් ප්‍රතිස්ථාපනය කළ තුළු මෙහෙයුම්




15.05.16


Space charge region / depletion region

Diode : without bias /

No applied voltage

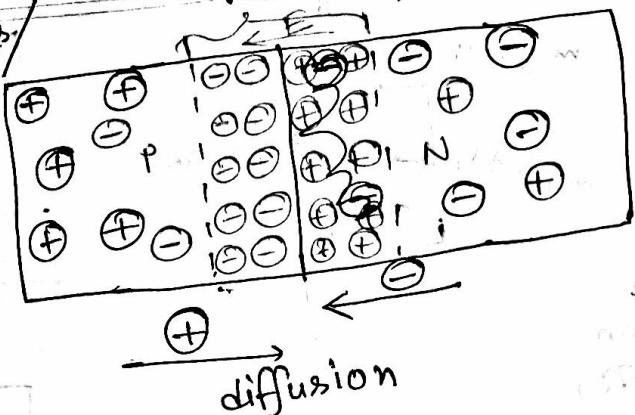

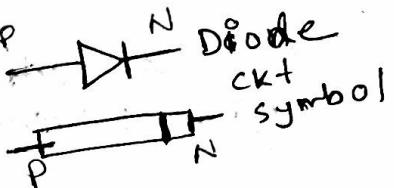→ equilibrium condition  
diffusion = drift




diffusion  $\leftrightarrow$  density difference

electric field  $\rightarrow E$

- 1) diffusion  $\rightarrow$  semiconductor is possible
- 2) drift  $\rightarrow$  electric field  $\Rightarrow$  current  
\* minority carrier move


Forward Bias:  $[V_d > 0]$

- 1) P side +ve  
N side -ve

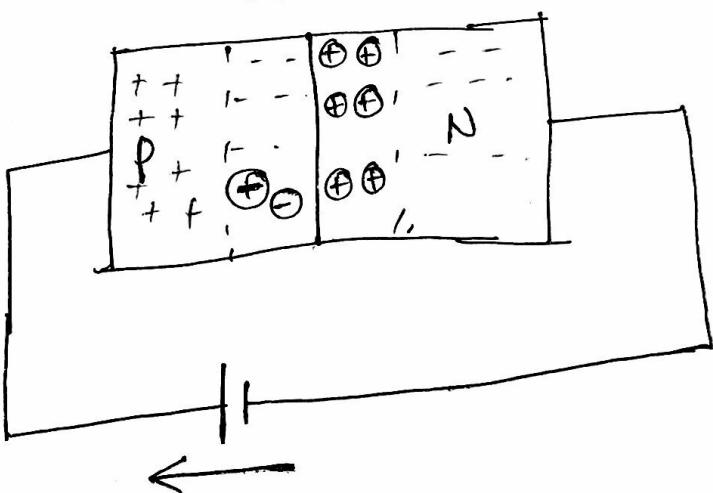

- 2) diffusion will increase
- 3) depletion area will decrease
- 4) current will start to flow


## Reverse bias

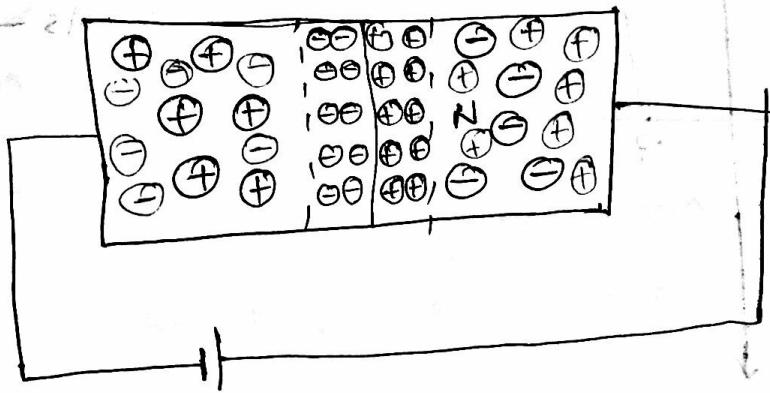


- 1] P side -ve  
N side +ve
- 2] Depletion area will increase
- 3] Diffusion will decrease
- 4) current won't flow

## Diode curve

Diode I-V curve : (Ideal state).

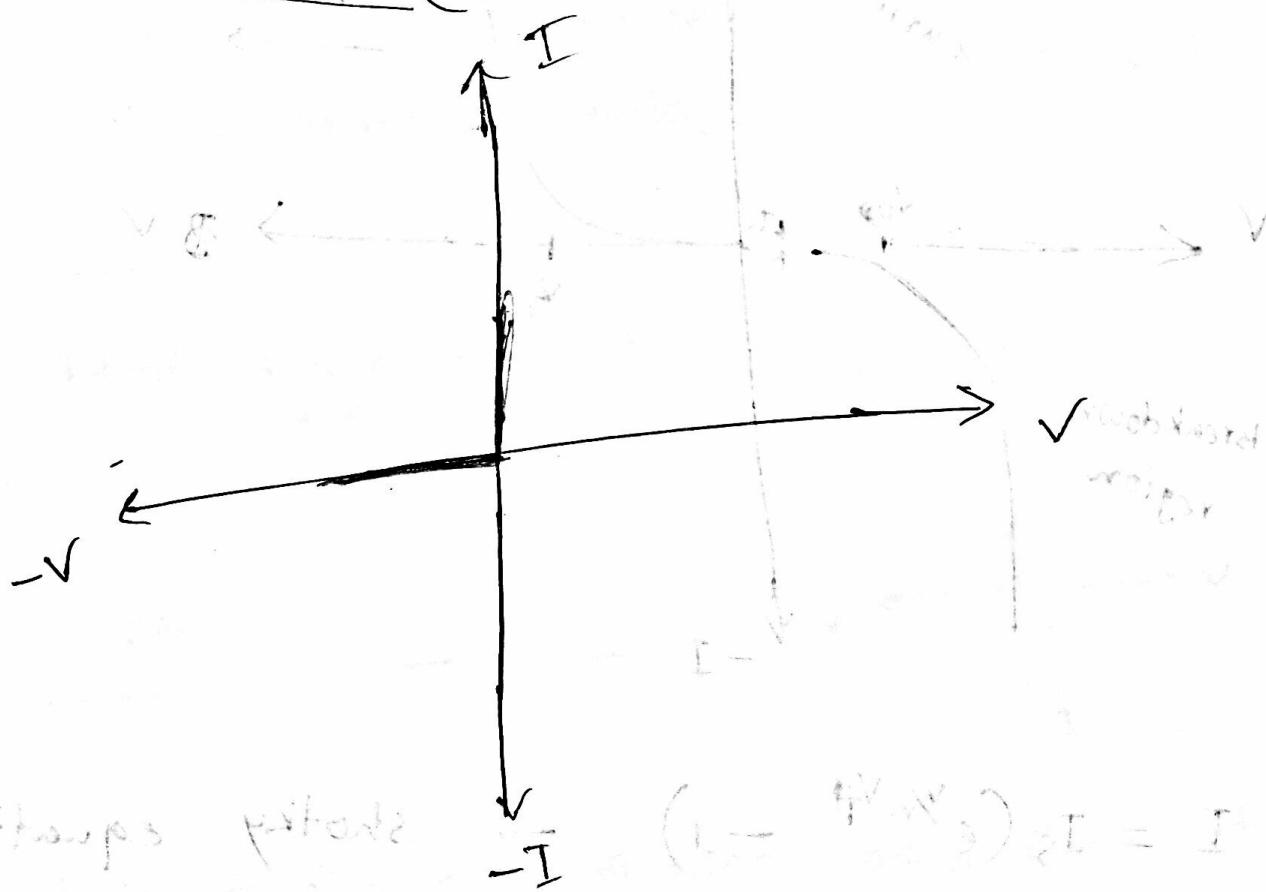


constant voltage drop model

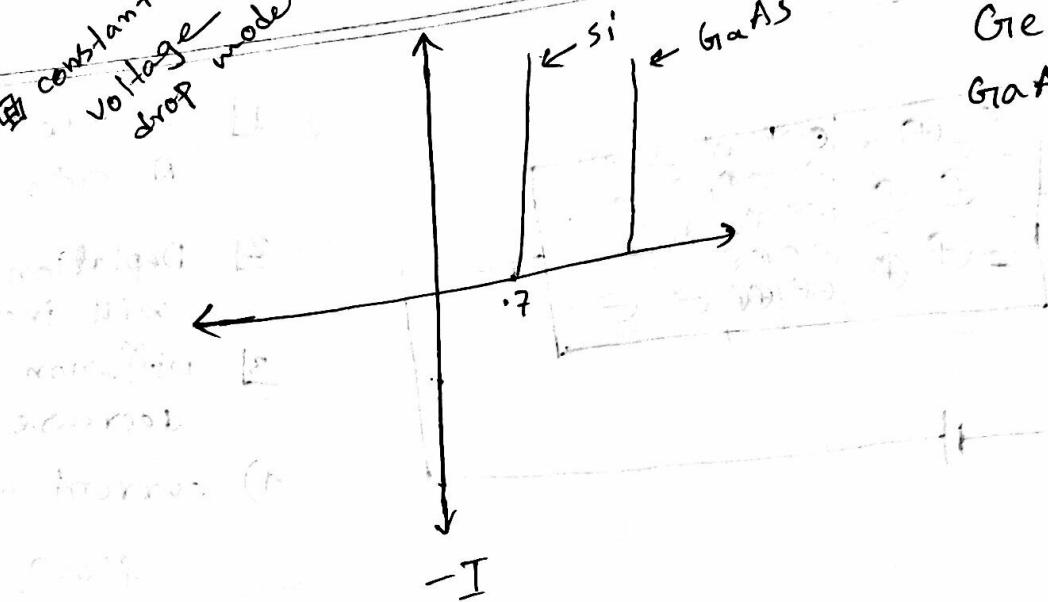

$$\begin{aligned} Si &= 0.7V \\ Ge &\rightarrow 0.3V \\ GaAs &\rightarrow 1.2V \end{aligned}$$

$I_S$  = reverse saturation current

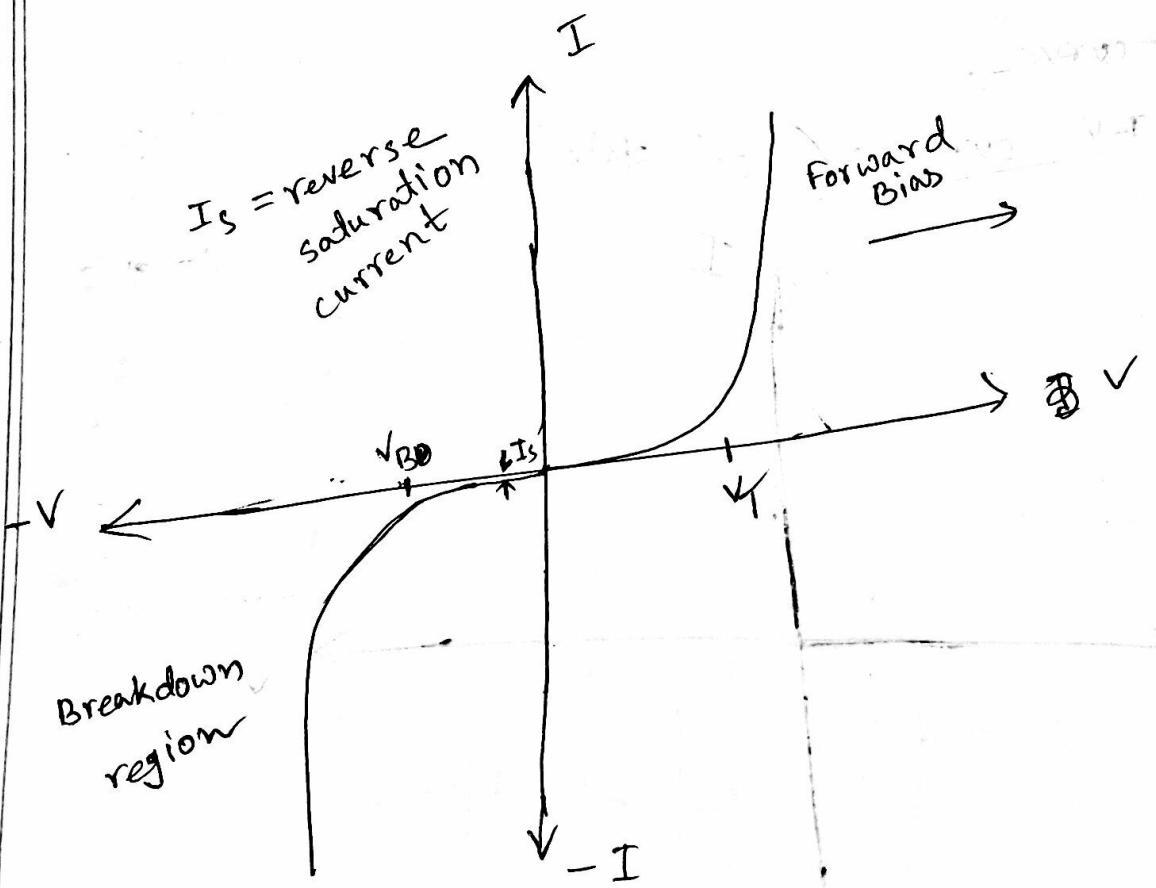

Breakdown region

$$I = I_S (e^{\frac{V}{nV_T}} - 1) \rightarrow \underline{\text{shotky equation}}$$



19.05.16

## Diode models:

1) Ideal diode model

2) constant voltage drop model

3) piece-wise linear model

4) small signal model


$$n = 1, 2$$

$$I = I_s (e^{V/nV_T} - 1)$$



$I_s$  = Reverse saturation current

$V_T$  = Thermal voltage



$V^*$  = Threshold voltage

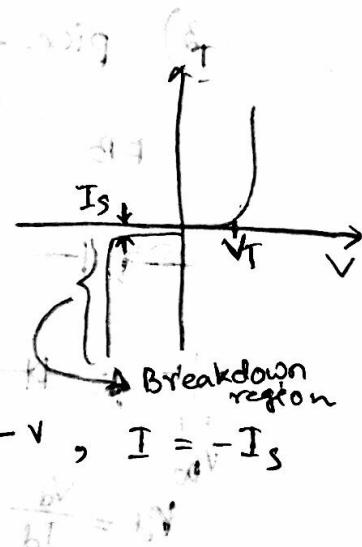


1) Ideal diode model:

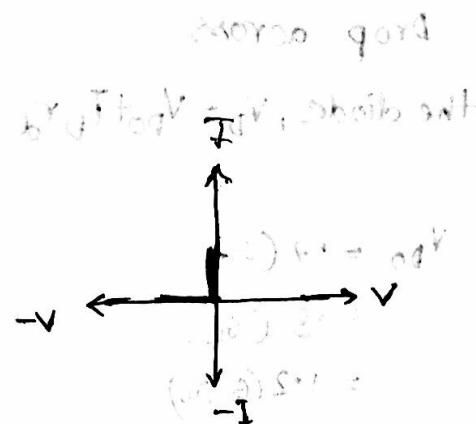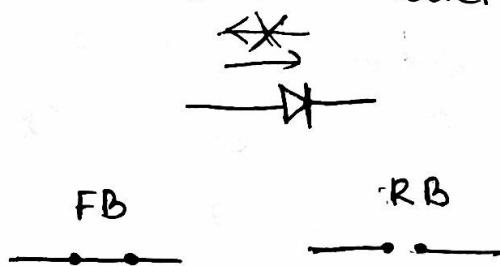

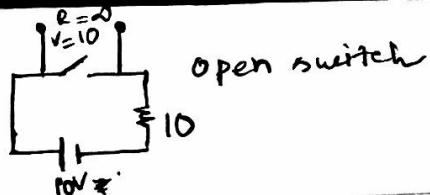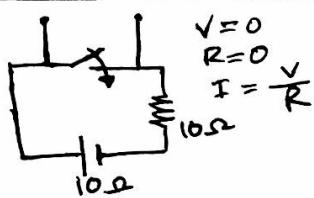
\* diode এ ফিল্ড দেঙ্গু না থাকে তাহলে ideal diode নিতে হবে।



1) Constant voltage drop model :

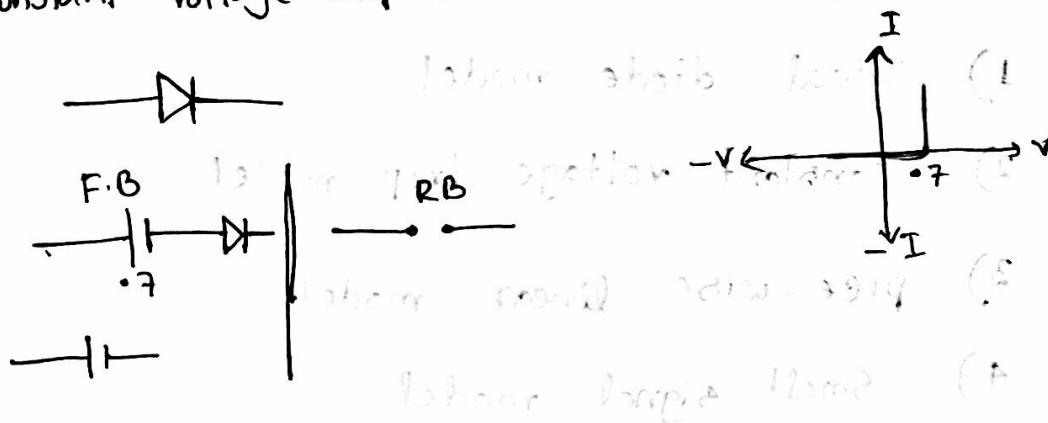

2) piece - wise linear model :

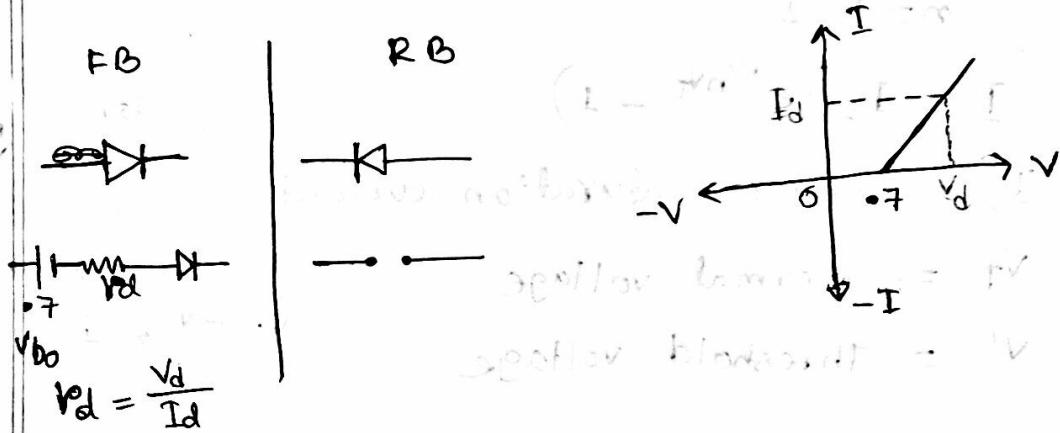

Drop across

the diode,  $V_D = V_{D0} + I_D r_d$

$$V_{D0} = 0.7 \text{ (Si)}$$

$$= 0.3 \text{ (Ge)}$$

$$= 1.2 \text{ (GaAs)}$$

Isotonic switch loss (L)




Isotonic switch loss (L) before diode in (fig 2) part 2 sketch 3

\* How to develop small signal model:

\* from photocopy
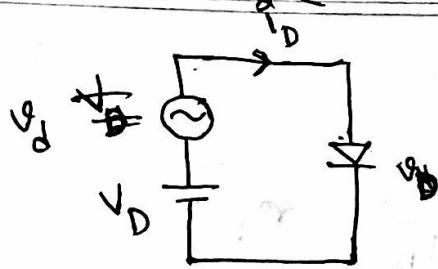
### iv) Small signal model (low frequency)



$$v_D = DC + AC$$

$$v_d = AC$$

$$v_D = AC + DC$$

For DC only

$$I_D = I_s \left[ e^{\frac{v_D}{nV_T}} - 1 \right]$$

$$\approx I_s e^{\frac{v_D}{nV_T}} \quad \text{for } e^{\frac{v_D}{nV_T}} \gg 1$$

for AC + DC

$$i_D = I_s e^{\frac{v_D}{nV_T}}$$

Now,

$$v_D + v_d = v_D$$

From eq-1,

$$i_D(t) = I_s e^{\frac{v_D + v_d}{nV_T}}$$

$$= I_s e^{\frac{v_D}{nV_T}} e^{\frac{v_d}{nV_T}}$$

$$= I_D e^{\frac{v_d}{nV_T}} \left[ e^{qun} - 1 \right]$$

$$= I_D \left[ 1 + \frac{v_d}{nV_T} + \frac{(v_d nV_T)^2}{2!} + \dots \right]$$

$$\approx I_D \left[ 1 + \frac{v_d}{nV_T} \right]$$

$$i_D = I_D + I_D \frac{v_d}{nV_T}$$

(constant  $\text{v}_D$ )  $i_D$  has large linear exp.

$$i_D = I_D + \frac{\frac{v_d}{nV_T}}{I_D}$$

$$= I_D + \frac{v_d}{r_d} \quad \left[ \frac{nV_T}{I_D} = r_d \right]$$

$$i_D = I_D + i_d$$

so

$$v_D = i_D \cdot r_d + v_{DD}$$


$$= (I_D + i_d) r_d + v_{DD}$$

$$= I_D r_d + i_d r_d + v_{DD}$$


$$= (I_D r_d + v_{DD}) + i_d r_d$$

$$= v_D + i_d r_d$$

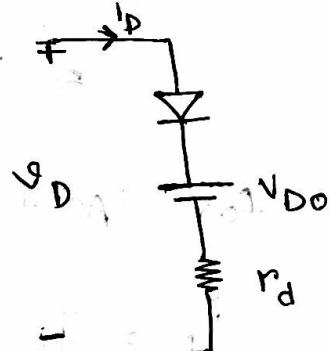
$$\left[ 1 - \frac{v_D}{nV_T} \right] \text{exp} = nT$$



DC equivalent ckt

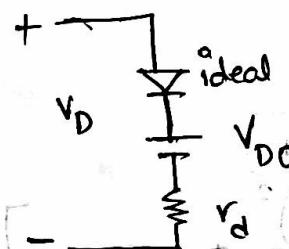


AC eqa ckt

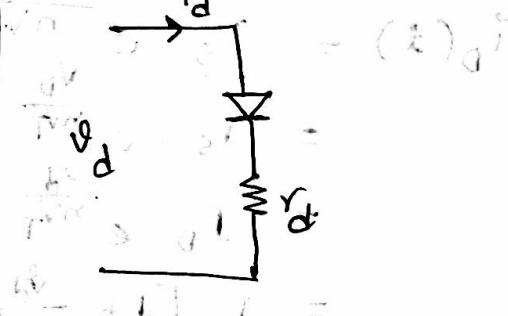

$$\left[ -\frac{R_d}{nV_T} + 1 \right] qf =$$

$$qf + qL = 0$$

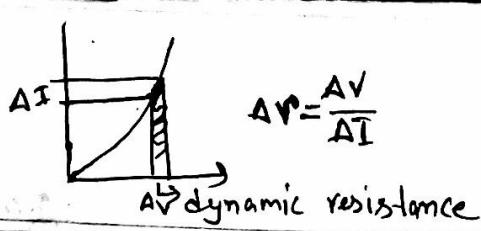

$\rightarrow$  slope different  
 $\rightarrow$   $R$  fixed  
 $\rightarrow$  non linear

$$R = \frac{V}{I}$$

static Resistance

$\swarrow$   $\rightarrow$  Linear


### Load line:

operating point

$\rightarrow$  Q point is the point where characteristic curve and load line intersects

$\rightarrow$  load line represents the linear part of the circuit connect to the non linear device (diode)

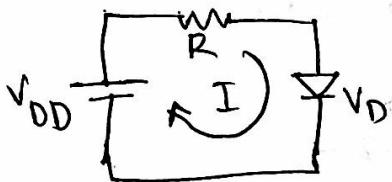$\rightarrow$  load line varies with load (Resistance)



$$-V_{DD} + IR + V_D = 0$$

$$I = 0,$$


$$-V_{DD} + V_D = 0$$

$$\Rightarrow V_D = V_{DD} \quad |_{I=0}$$

$$V_D = 0,$$

$$-V_{DD} + IR = 0$$

$$\Rightarrow I = \frac{V_{DD}}{R} \quad |_{V_D=0}$$

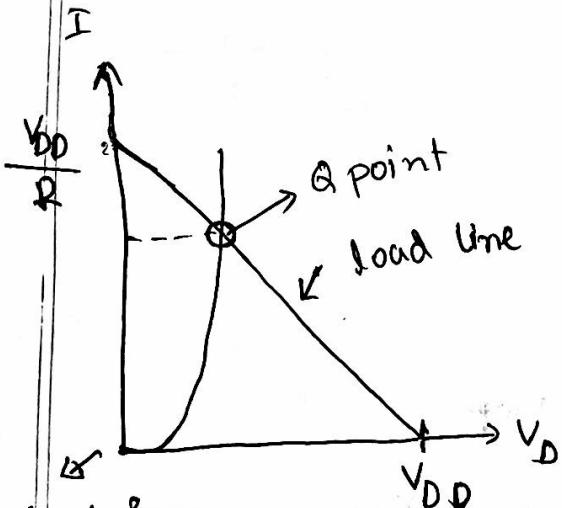

method of ~~solving~~  $\rightarrow$  graphical method of solving

\*  $\rightarrow$  Q point ~~is~~ current in circuit  $\approx$  current

\* Q point ~~is~~ voltage in circuit  $\approx$  voltage drop.

22.05.2016

$$f_B = 2.5 \text{ mV}/^\circ\text{C}$$

$R_B$  for every  $10^\circ\text{C}$  the  $\alpha$  will be

(assuming  $I_S$  doubles)

so  $I_B$  also


reverse  
saturation  
current

will change as  $I_B$  changes


(with) increase

more soft of

more bias

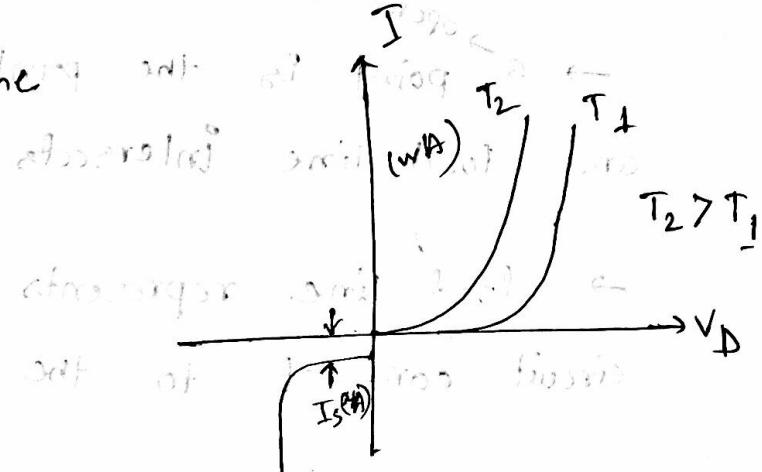


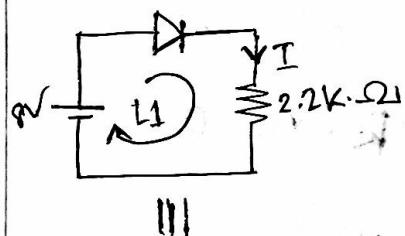(Conclusion) final after assuming soft bias etc.




KVL in loop L1,
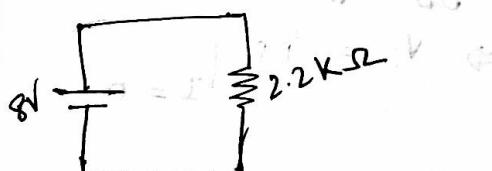
$$0 = 8V + 2.2k\Omega I = \frac{8V}{2.2k\Omega} = 3.636A$$




$$0 = 8V - 2.2k\Omega I$$

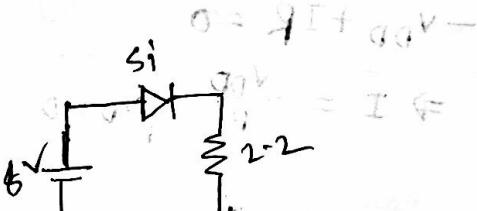

KVL in loop

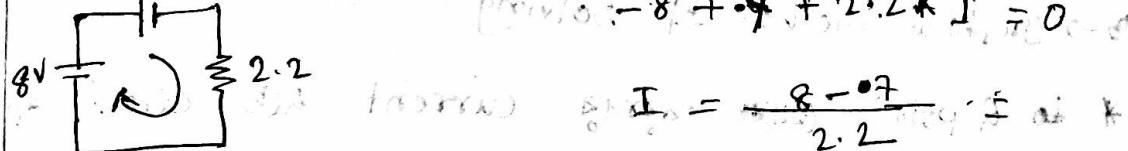
$$0 = -8V + 0.7V + 2.2k\Omega I_3 = 0 \Rightarrow I_3 = 3.636A$$




$$0 = 8V - 0.7V - 2.2k\Omega I_4 = 0 \Rightarrow I_4 = 3.636A$$

and so on for other loops as well from P to S


Polymer  
injection region

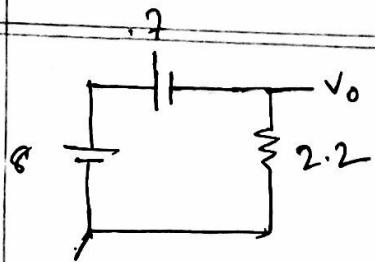


$$V_0 = 2.2 * I$$

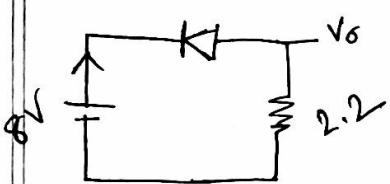


III

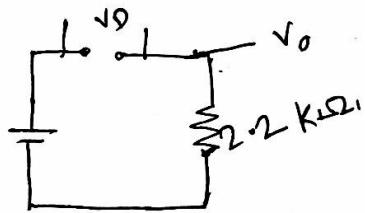

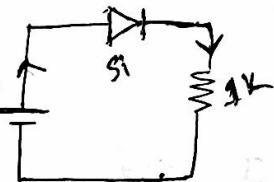~~I~~  
 $I = 0$   
 $V = 0$   
 $V_D = 8 V$






III

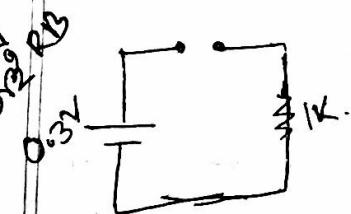

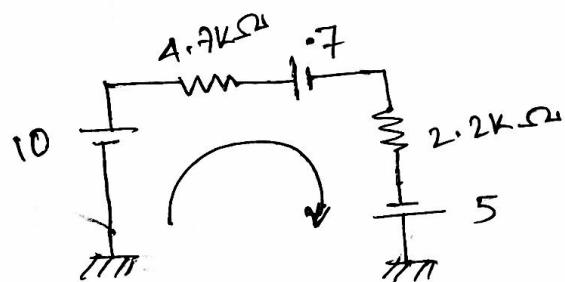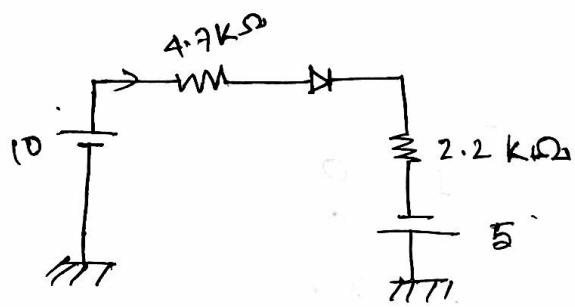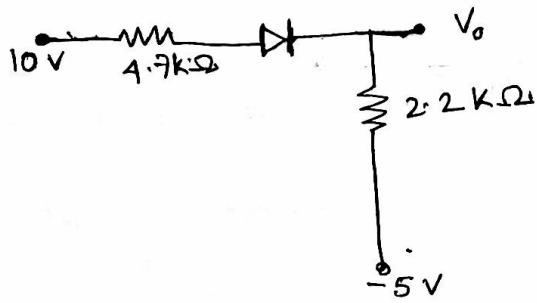0.7  
0.32  
0.729 R<sub>2</sub>

higher potential  $\xrightarrow{\text{current flow}}$  lower potential





$$-10 + 4.7k \cdot I + 2.2k \cdot I - 5 = 0$$

$$\Rightarrow I =$$

$$V_o = 2.2 \cdot I - 5$$

$$=$$

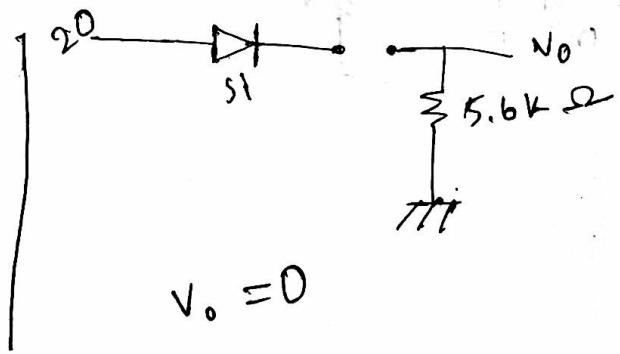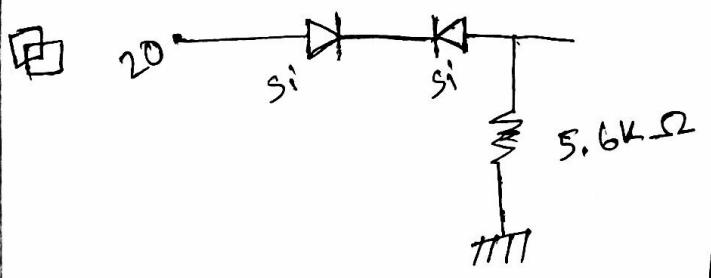



Next Sunday

Quiz - I time - 20 min  
First → 26.05.16 lecture

half set ques  
→ 3 set ques


diode

#


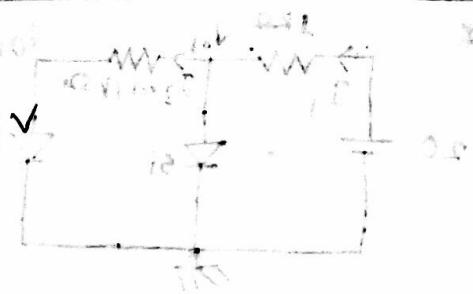
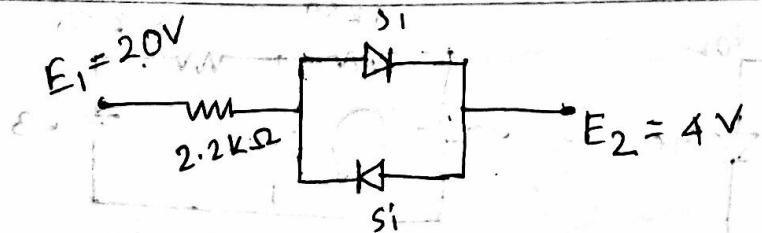


$$0 = 6 + t_1 + 2 \cdot 2 \cdot 1 + 0.6 -$$

$$-20 + 2.2k \cdot I + 7 + 4 = 0$$


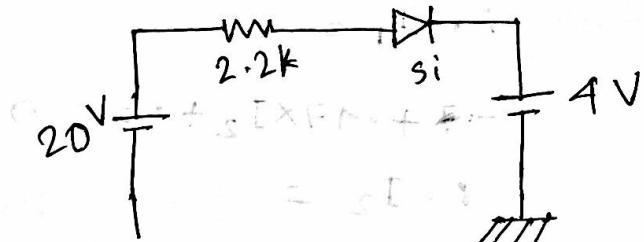


$$I = \frac{6.6}{2.2k} = 3A$$

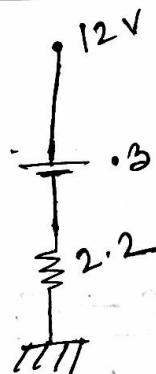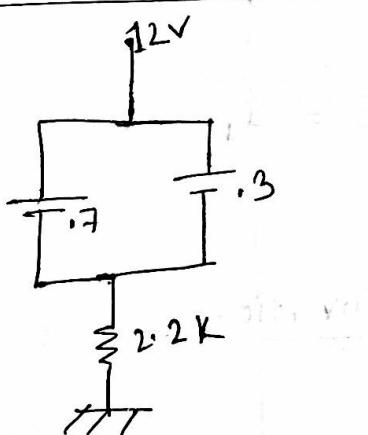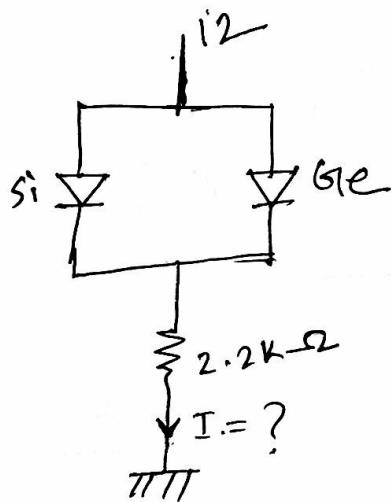

$$-12 + 0.3 + 2.2 \cdot I = 0$$

$$I =$$

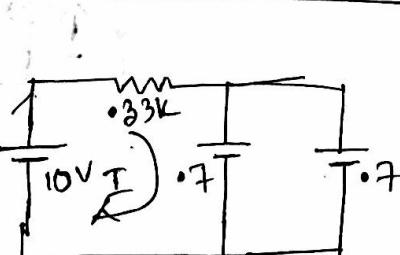
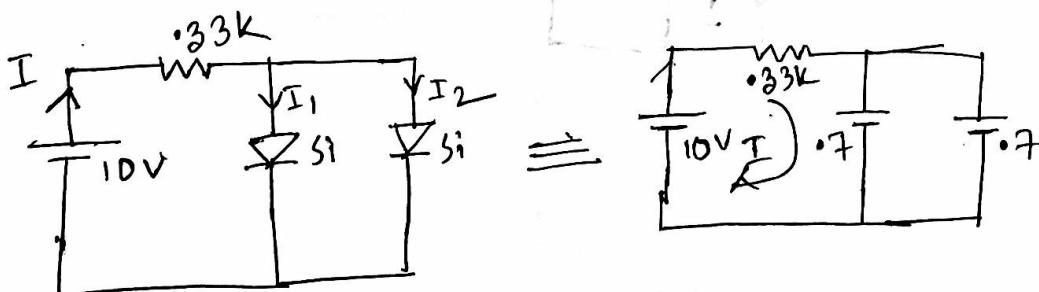


$$I_1 = I_2 = \frac{I}{2}$$

$$-10 + 33 \cdot I + 0.7 = 0$$

$$I = \frac{10 - 0.7}{33} =$$

26.05.16

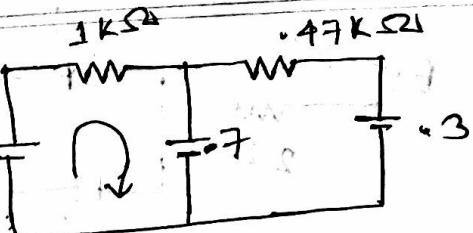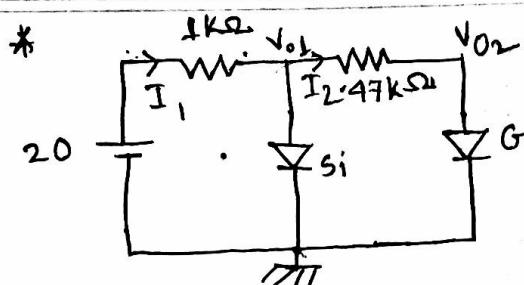

$$-20 + 1k\Omega \times I_1 + .7 = 0$$

$$\therefore V_{O1} = 0.7V$$

$$\therefore V_{O2} = .3V$$

$$\therefore I_1 = \frac{20}{1k\Omega}$$

$$-.7 + .47 \times I_2 + .3 = 0$$



$$\therefore I_2 =$$

KCL at,

$$I = I_1 - I_2$$


### AC $\rightarrow$ DC conversion:

Rectifier

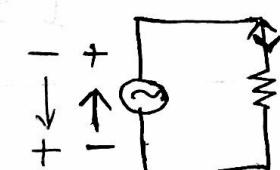
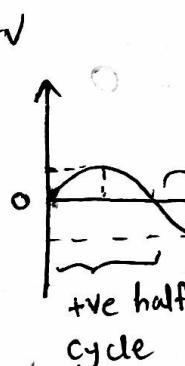


$$RMS = 220V$$

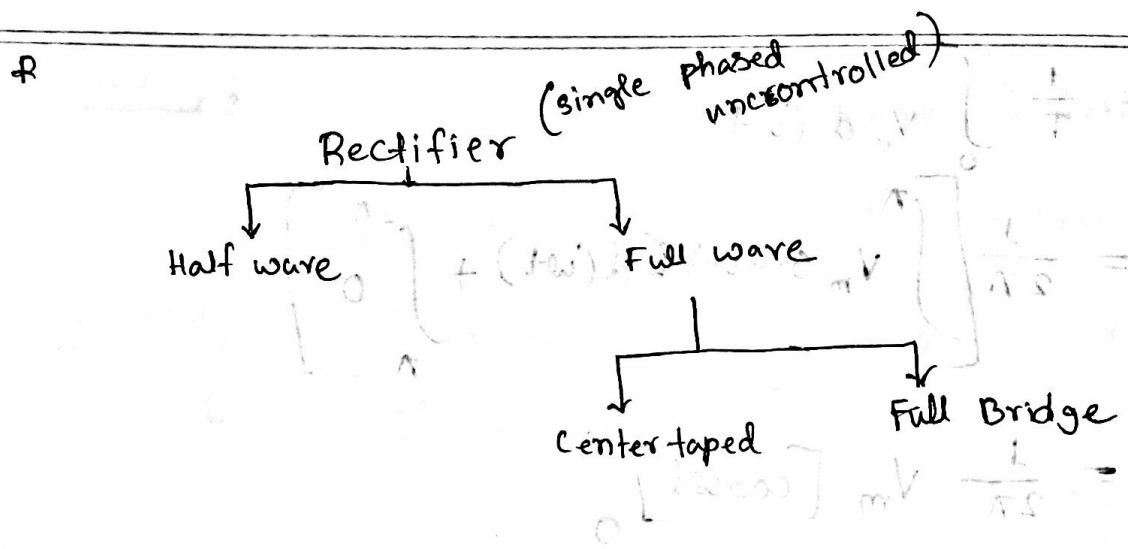
$\rightarrow \text{Time period}, V_{avg} = 0$




Half wave :

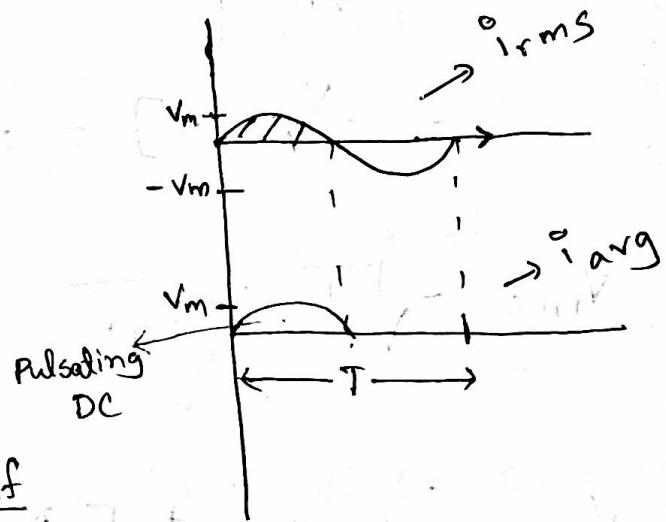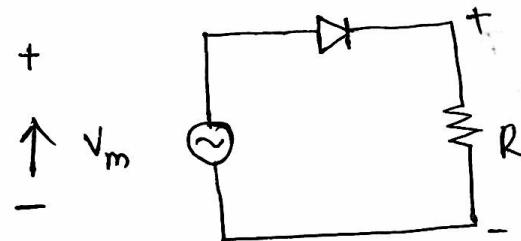


+ ve half

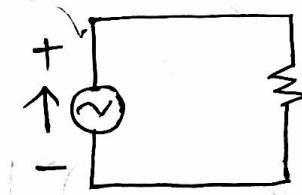

-ve half

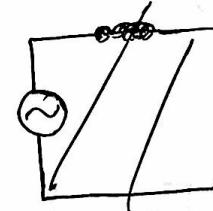

$V_{avg}$

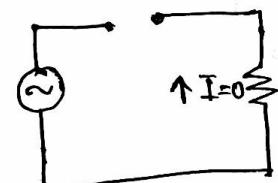

$$V_o = 0 \text{ & } R = 0$$

$$V_{avg} = \frac{1}{T} \int_0^T V_o d(\omega t)$$

$$= \frac{1}{2\pi} \left[ \int_0^\pi V_m \sin \omega t d(\omega t) + \int_\pi^{2\pi} 0 d(\omega t) \right]$$

$$= \frac{1}{2\pi} V_m \left[ \cos \omega t \right]_0^\pi$$

$$= \frac{V_m}{2\pi} \left[ -\cos \pi + \cos 0 \right]$$

$$\therefore = -\frac{V_m}{2\pi} [2] = -\frac{V_m}{\pi}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_o^2 dt}$$


$$V_{rms} = \frac{1}{2\pi} \left[ \int_0^\pi V_m^2 \sin^2 \omega t d(\omega t) + \int_\pi^{2\pi} 0 d(\omega t) \right]$$

$$= \frac{V_m^2}{4\pi} \left[ \pi - \frac{1}{2} (\sin 2\pi - \sin 0) \right]$$

$$= \frac{V_m^2}{4}$$

$$V_{rms} = \frac{V_m}{2}$$

## Efficiency :

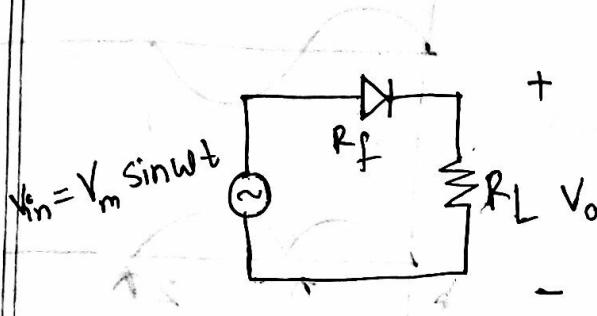

$R_f$  = diode forward resistance

$R_L$  = load resistance

$$\begin{aligned} i &= \frac{V_{in}}{R_f + R_L} = \frac{V_m \sin \omega t}{R_f + R_L} \\ &= \left[ \frac{V_m}{R_L + R_f} \right] \sin \omega t \\ &= I_m \sin \omega t \end{aligned}$$

Here,

$$I_m = \frac{V_m}{R_f + R_L}$$

$$i_{avg} = \frac{I_m}{\pi}$$

$$i_{rms} = \frac{I_m}{2}$$

$$\eta = \frac{P_o}{P_{in}} \times 100\%$$

$$P_o = (i_{avg})^2 R_L$$

$$= \left( \frac{I_m}{\pi} \right)^2 R_L$$

$$= \frac{I_m^2}{\pi^2} R_L$$

$$P_{in} = i_{rms}^2 (R_L + R_f)$$

$$= \frac{I_m^2}{4} (R_L + R_f)$$

$$\eta = \frac{1}{\pi^2} * \frac{R_L}{R_L + R_f} * 100\%$$

for ideal diode  $R_f = 0$



$$\begin{aligned} \eta &= \frac{1}{\pi^2} \times 100\% \\ &= 40.5\% \end{aligned}$$

\* Show that half wave rectifier's efficiency 40.5%.


## Bridge Rectifier:

- Diodeless load = 1A



Pos

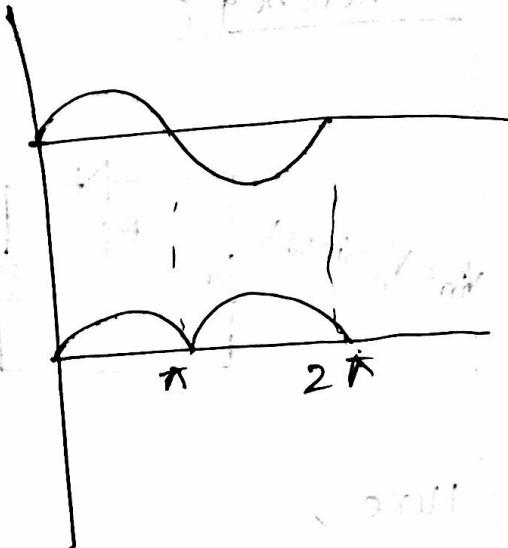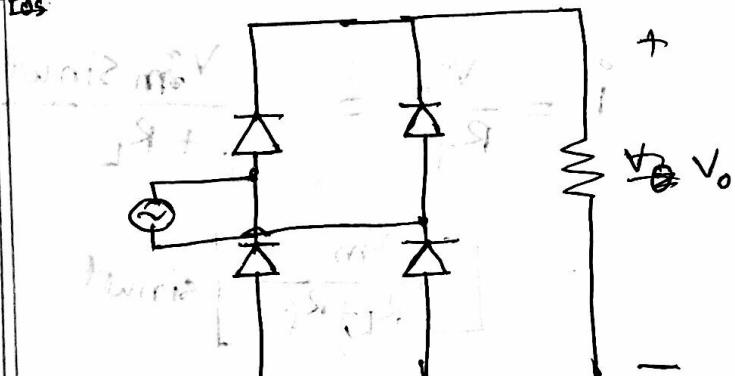

+ve half cycle:

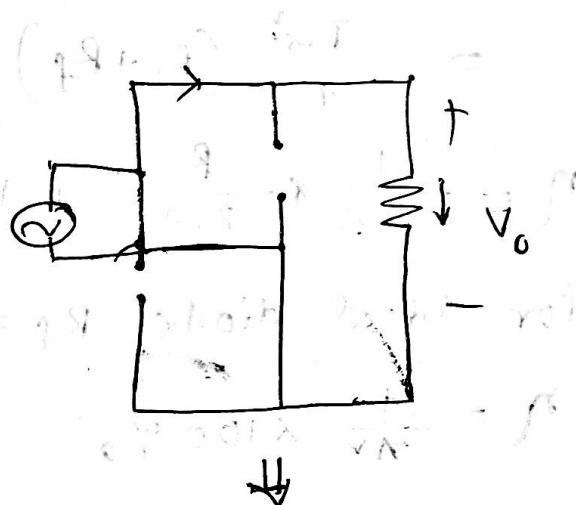

-ve half cycle:

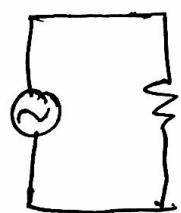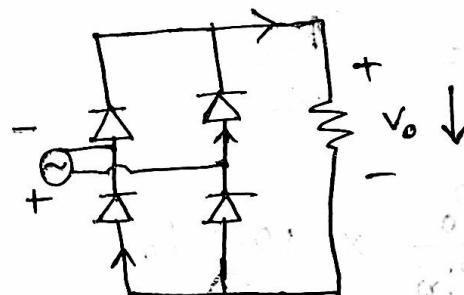

one diodeless load current flows through the load resistor


- \* half wave  $\rightarrow$  avg
- \* half wave  $\rightarrow$  efficiency

$$V_{avg} = \frac{1}{T} \int_0^T V_o dt$$

$$= \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t d(\omega t)$$

$$= \left[ -\frac{V_m}{\pi} \cos \omega t \right]_0^{\pi}$$

$$= \frac{2V_m}{\pi}$$

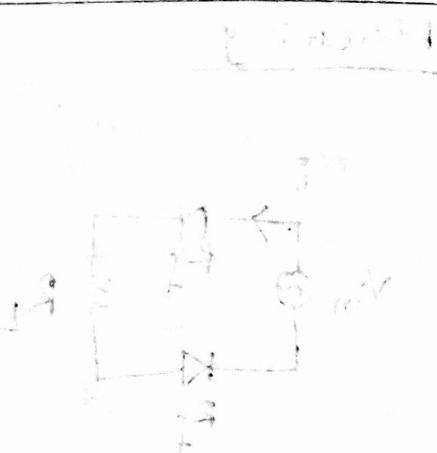

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_o^2 dt}$$

$$V_{rms} = \frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t d(\omega t)$$


$$= \frac{V_m^2}{2\pi} \int [1 - \cos 2\omega t] d(\omega t)$$

$$(1 + j)^2 (1 - j)^2 = (1 + j)^4 = 2\sin^2 \omega t = V_o^2$$

$$= \frac{V_m^2}{2\pi} \times \pi = \frac{V_m^2}{2}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \sqrt{2} = \frac{V_m}{\sqrt{2}}$$

## Efficiency

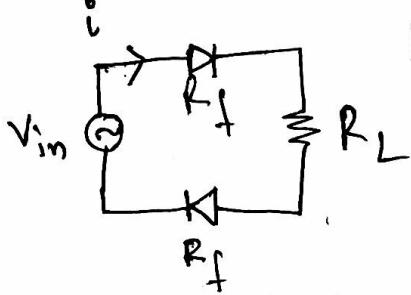

$$V_{in} = V_m \sin \omega t$$

$$i = \frac{V_{in}}{R_f + R_L}$$

$$(i) = i = \frac{V_{in}}{2R_f + R_L}$$

$$= \left[ \frac{V_m}{2R_f + R_L} \right] \sin \omega t$$

$$= i_m \sin \omega t$$

$$i_m = \frac{V_m}{2R_f + R_L}, \quad i_{avg} = \frac{2i_m}{\pi}, \quad i_{rms} = \frac{i_m}{\sqrt{2}}$$

$$\eta = \frac{P_{DC}}{P_{AC}} = \frac{P_o}{P_{in}} * 100\%$$

$$= \frac{V_{avg} I_{avg}}{\sqrt{rms} I_{rms}} * 100\%$$

$$P_o = (i_{avg})^2 R_L = \left( \frac{2i_m}{\pi} \right)^2 R_L$$


$$P_{in} = i_{rms}^2 (R_L + 2R_f) = \left( \frac{i_m}{\sqrt{2}} \right)^2 (R_L + 2R_f)$$

$$\eta = \frac{8}{\pi^2} \left[ \frac{R_L}{R_L + 2R_f} \right] * 100\%$$


for ideal diode  $R_f = 0$

$$\eta = 81\%$$

## Center Tap Rectifier :

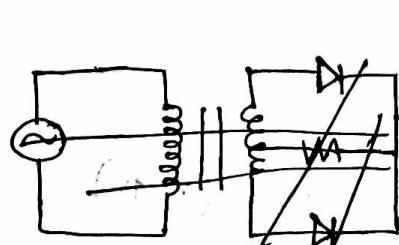

forward half cycle

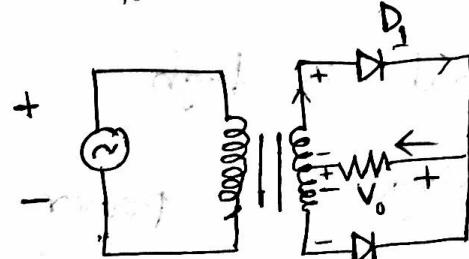


+ve half cycle

D<sub>1</sub> ← current flow direction

-ve half cycle

D<sub>2</sub> ← current flow direction

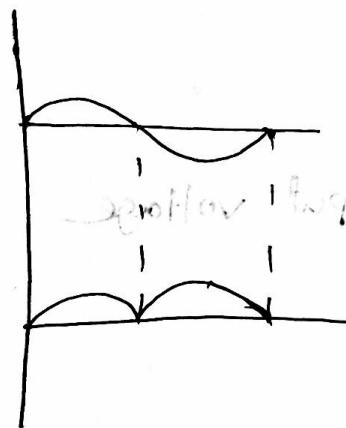

## PIV :

Peak inverse voltage

"It is the voltage rating that must not be exceeded in reverse bias region or the diode will enter junction avalanche region.

## + of full rectifier

Efficiency goes up

1) Output is high


2) Wastage of power is less ( $\eta \uparrow$ )

## - of half wave rectifier

1) Load receive half of input voltage

2) avg. DC is less.

3)  $\eta = 41\%$

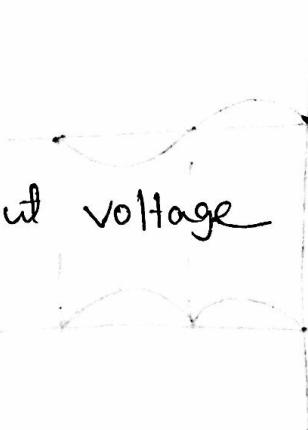

V<sub>eff</sub>

Section 3009


d for better load power section with AC

which will no major load section in half-wave

major section with rated values will

02.06.16

### Clipper:

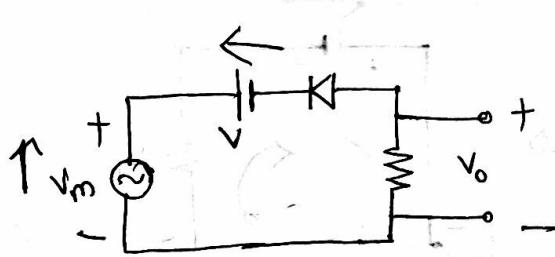

+ve (initial)


$$V > V_m$$

so, diode is F.B.



$$+ V_m - V_o - V = 0$$

$$\Rightarrow V_o = V_m - V \quad \begin{cases} V_m = 0 \\ V_o = -V \end{cases}$$



$V < V_m$  diode is R.B

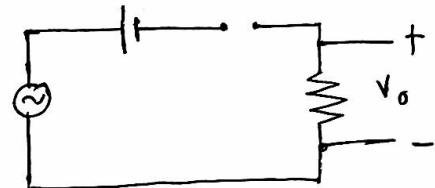

$$V_o = 0$$

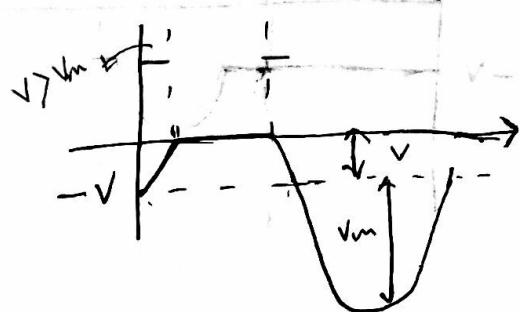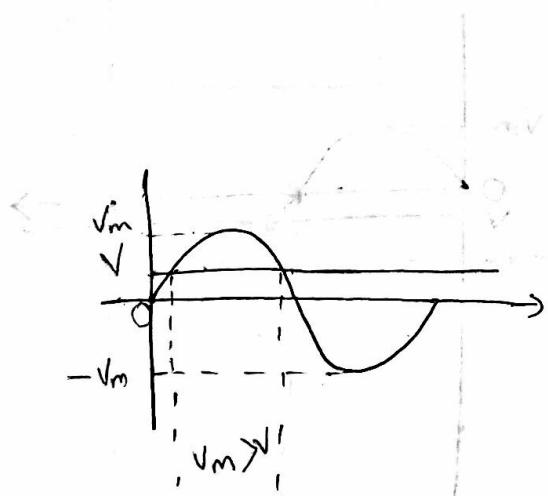

-V<sub>e</sub> half

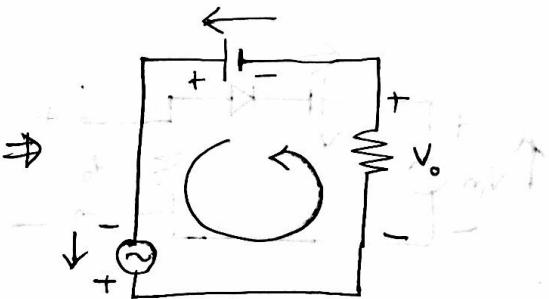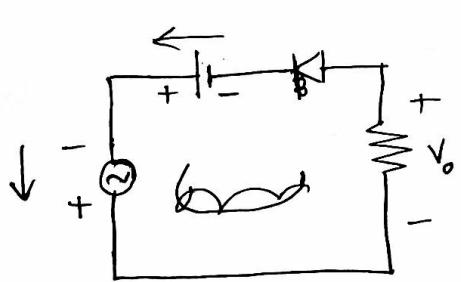



Diode is in FB

$$-V_m - V_o - V = 0 \quad < 0$$

$$\Rightarrow V_o = -V_m - V \quad \text{or} \\ = -(V_m + V)$$

$$V_o = -V_m - V = -V_m \quad \text{as } V > V_m$$

正

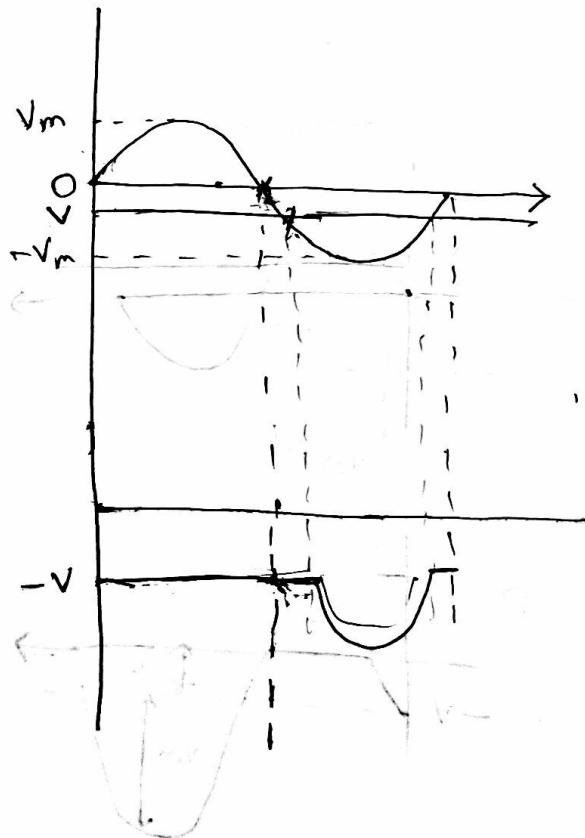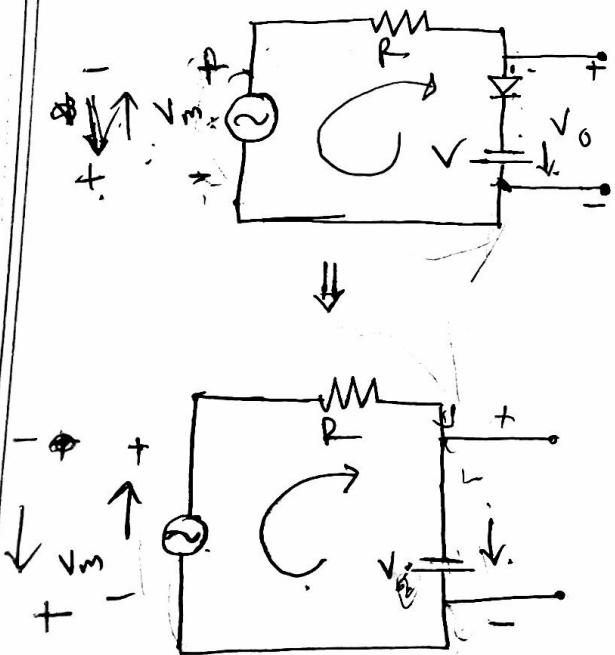

+ Ve half

Diode is in FB

$$-V_o = -V$$



- Ve half

when  $V > V_m$   
diode is in FB  
 $V_o = -V$

when  $V < V_m$

Diode is in RB

$$V_o = -V_m$$

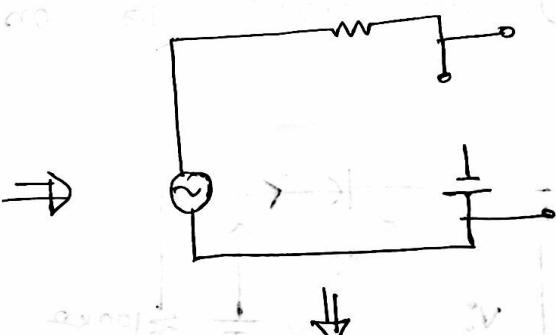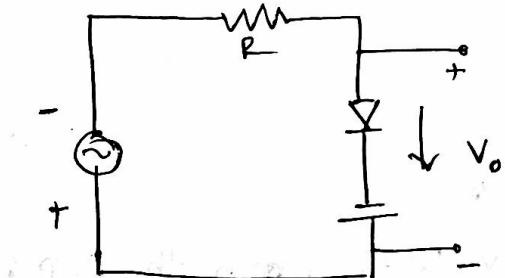


$$V_o = -V + R \cdot I$$

$$2 + 3V = 3V$$

$$2 = 0$$

$$2 = 2$$


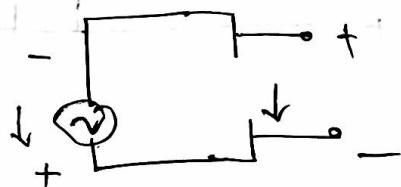


Half cycle


\*  $C = \frac{\epsilon_0}{d} \text{ (permittivity / charge density)}$   
 \* capacitor, DC  $\approx$  open circuit

\* c field current flows  $\perp$  to T  
 Maxwell

### Clamper:

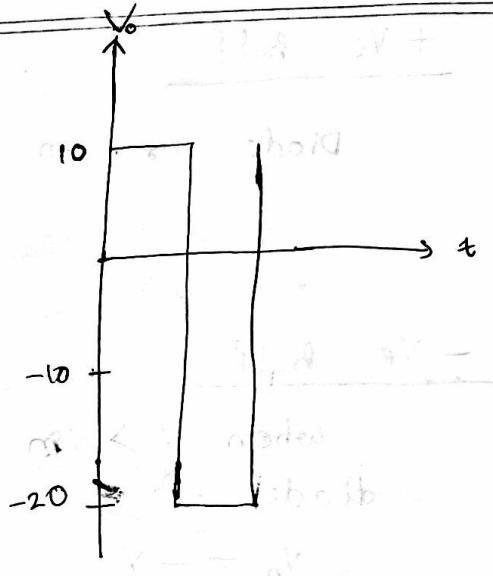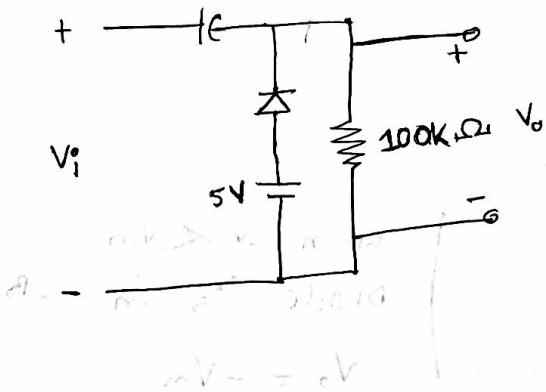

1) the diode is on (-ve half cycle)

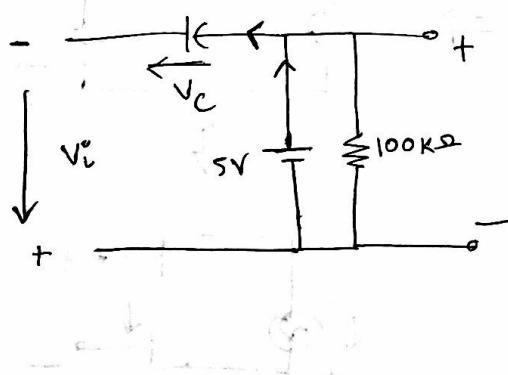

$V_o = 5V$   
 voltage across the cap:

$$-V_i - 5 + V_C = 0$$





$$\Rightarrow V_C = V_o + 5$$

$$= 20 + 5$$

$$= 25$$

-ve half

+ve half cycle

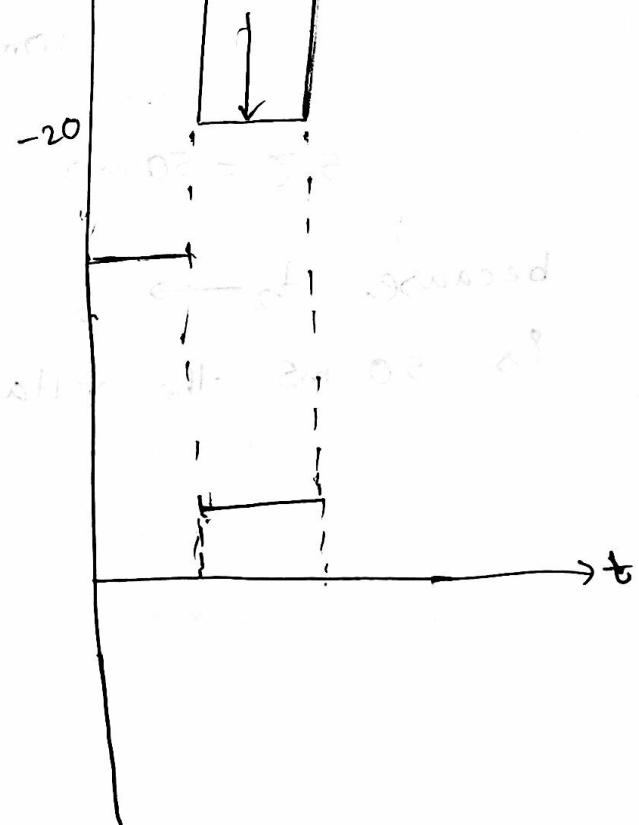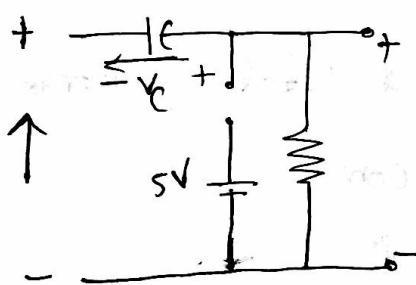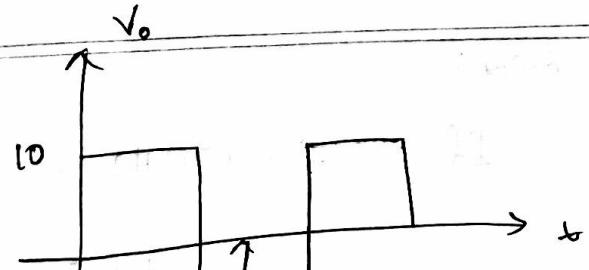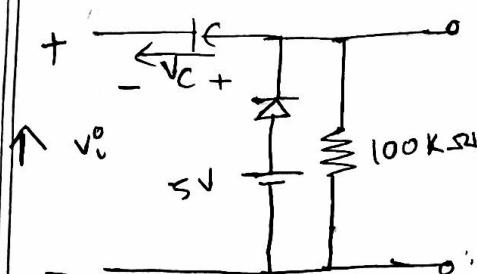

diode is in RB,

$$-V_i - V_C + V_o = 0$$

$$\begin{aligned} \Rightarrow V_o &= V_i + V_C \\ &= 10 + 25 \\ &= 35 \end{aligned}$$

\* Clipper, clamper math  $\rightarrow$  must

Now,

If  $f = 100 \text{ Hz}$   $T = 1 \text{ ms}$

$$C = 1 \mu\text{F}$$

$$R = 100 \text{ k}\Omega$$

$$T = RC = 0.01 \text{ s}$$

$$= 10 \text{ ms}$$

$$5T = 50 \text{ ms}$$

because  $t_2 \rightarrow t_3$  is  $.5 \text{ ms}$  and total discharge time


is  $50 \text{ ms}$  the voltage will be const.

$$V = V_f + jV_r - jV_i$$

$$jV_r + jV_i = j(V_r + V_i)$$




$$= 25 + 0j$$

$$= 25$$

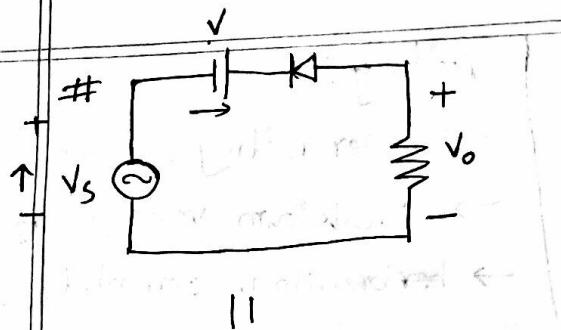+Ve half

diode is in R.B.

$$V_o = I \times R \\ = 0$$

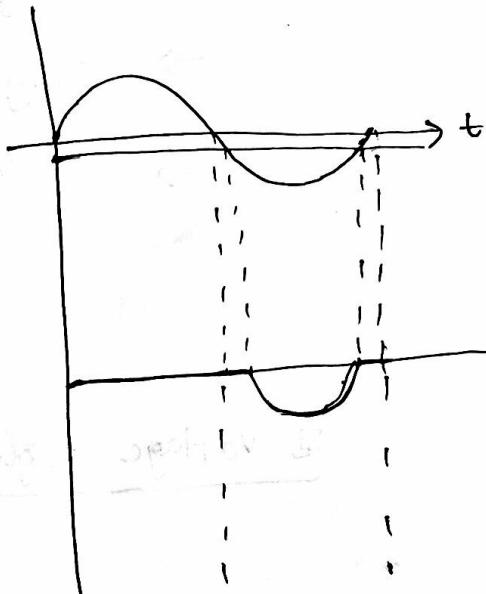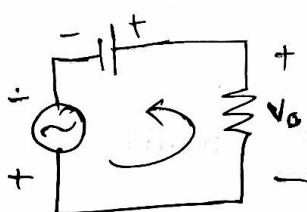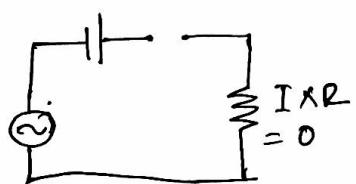-Ve half

$V > V_s$

diode is in R.B.



$V_o = 0$

$V < V_s$

diode is in F.B.

$-V_s - V_o + V = 0$

$\Rightarrow V_o = -V_s + V = -(V_s - V) = -V_s$

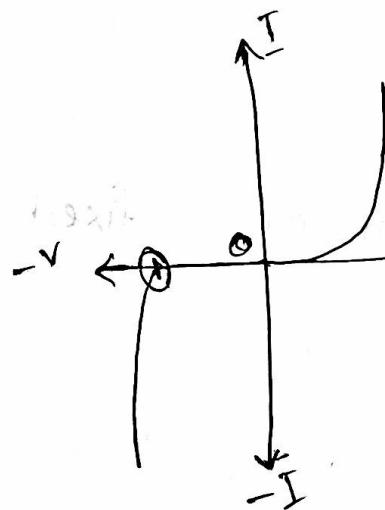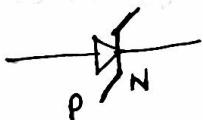Zener diode :Reverse bias  $\Rightarrow$  voltageconduct  $\Rightarrow$  C.G.

$\Rightarrow$  constant but  
current may  
 $\propto V^{-1}$


1. no percentage  
 voltage drop  $\frac{V_o - V_s}{V_s} \times 100\%$   
 2. regulation  $\frac{V_o - V_s}{V_s} \times 100\%$   
 ideal voltage source  $\rightarrow$  terminal voltage always constant,  $V_o$   
 current flow  $I_o$

- Voltage regulation
- Surge protection
- Waveform clipping

rating:

- Power rating,  $P_{max}$
- breakdown voltage,  $V_Z$
- breakdown current,  $I_{Z_{max}}$

### Voltage regulator circuit:

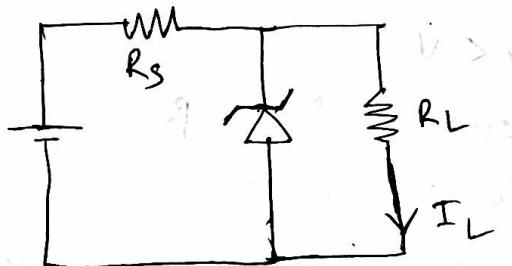

$$\text{line regulation} = \frac{\Delta V_o}{\Delta V_s} \left( \frac{\text{mV}}{\text{V}} \right)$$

output voltage variation  
input voltage variation

$$\text{load } " = \frac{\Delta V_o}{\Delta I_L} \left( \frac{\text{mV}}{\text{mA}} \right)$$


line:

$R_s$ ,  $R_L$  are fixed,  $V_s$  is variable.

load:

$R_s$ ,  $V_{in}$  are fixed,  $R_L$  is variable.

Fixed  $V_i$  variable  $R_L$ :

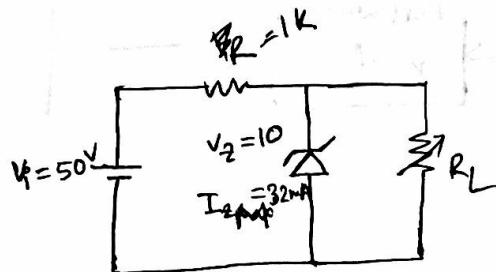

$$V_L = V_2 = \frac{R_L}{R_L + R} V_i$$

$$\Rightarrow R_{L\min} = \frac{V_2}{V_i - V_2} R$$

$$= 250 \Omega$$

So, voltage across  $R$  is,  $V_R = V_i - V_2$

$$= 50 - 10$$

$$= 40V$$

$$I_R = \frac{V_R}{R}$$

$$= \frac{40}{1k \Omega}$$


$$= 40mA$$

The. min  $I_L$ ,

$$I_{L\min} = I_R - I_{2M}$$

$$= 40 - 32$$

$$= 8mA$$

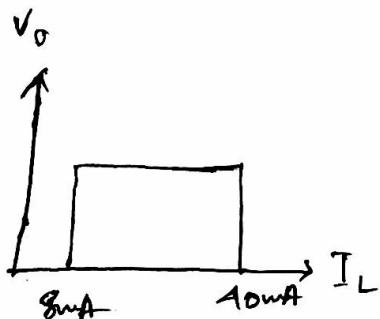


Requirement of  $R_L$


then,

$$R_{L\max} = \frac{V_2}{I_{\min}}$$

$$= \frac{10}{8mA}$$

$$= 1.25 k\Omega$$

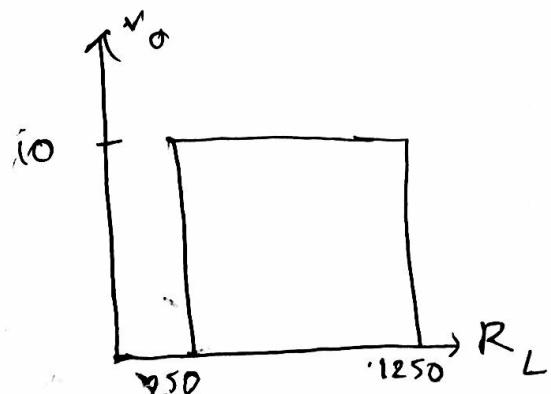


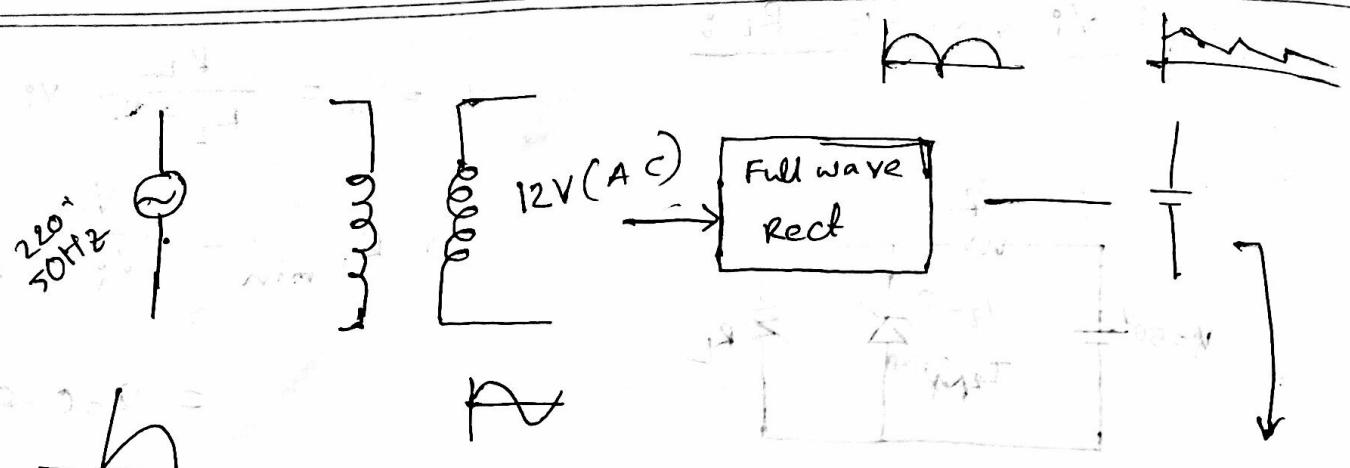

average powersupply




average powersupply

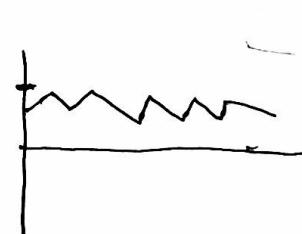

Regulator

7805  
LM337

$12 + 78.1 =$

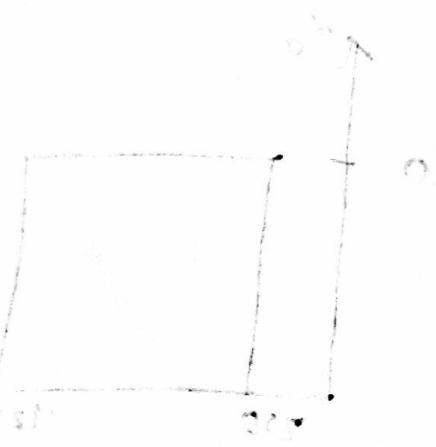


$12.5 - 8.1 = 4.4$   
square wave

$A_{mR} =$





BJT :

Bipolar Junction Transistor :

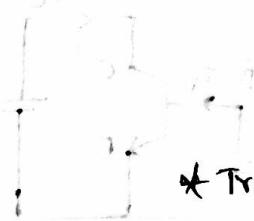

\* Transistor এর প্রয়োগ  
mosfet উপর ভাঙ্গা  
হওয়া,

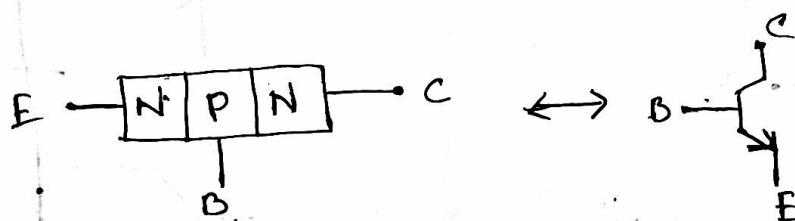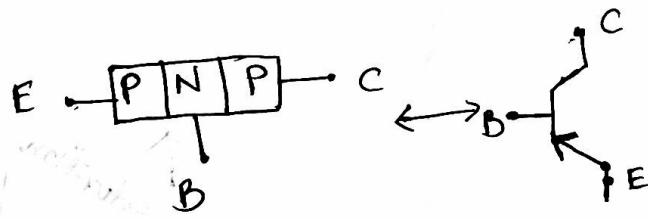Configuration of BJT


i) Common Base

ii) " " collector




iii) " " Emitter



## Common Emitter : (3 terminal device)

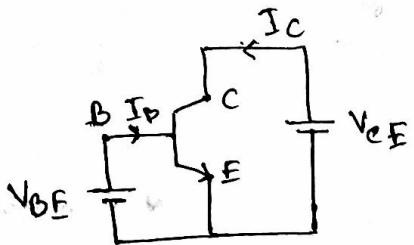


For the given condition

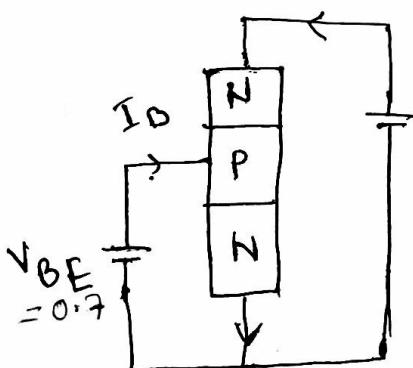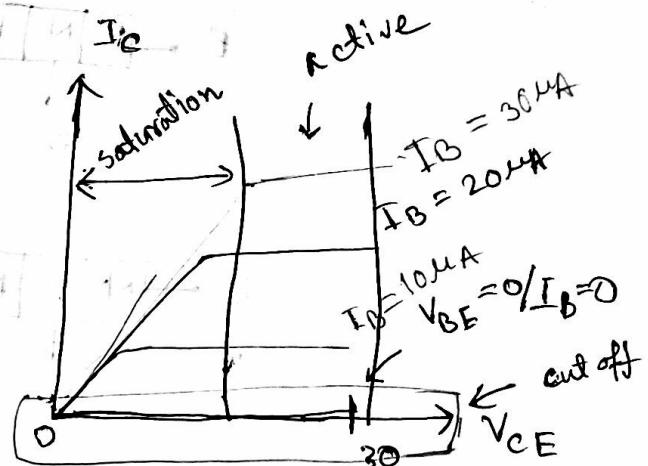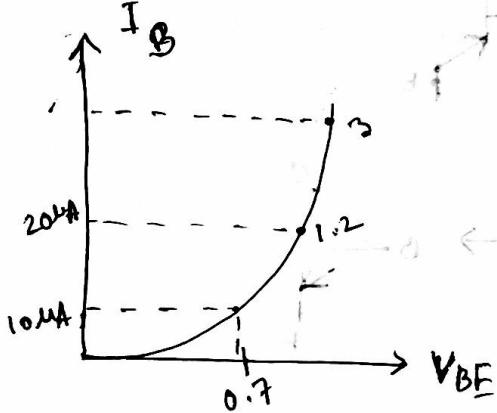


PCD p mitigation




## Explain : Zener breakdown

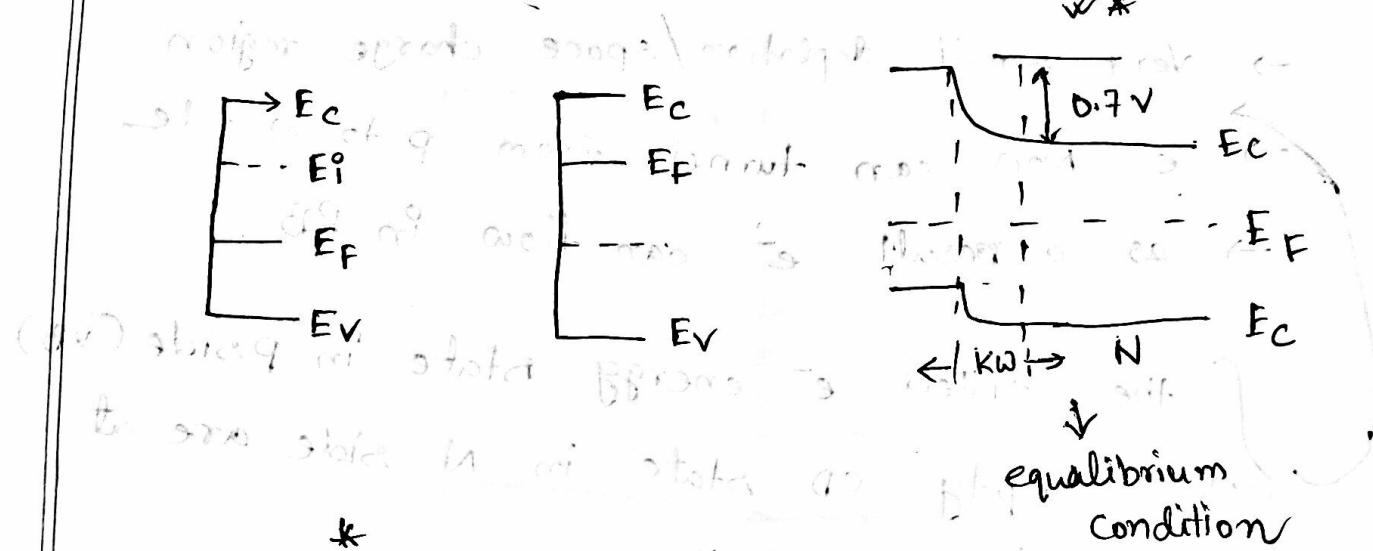

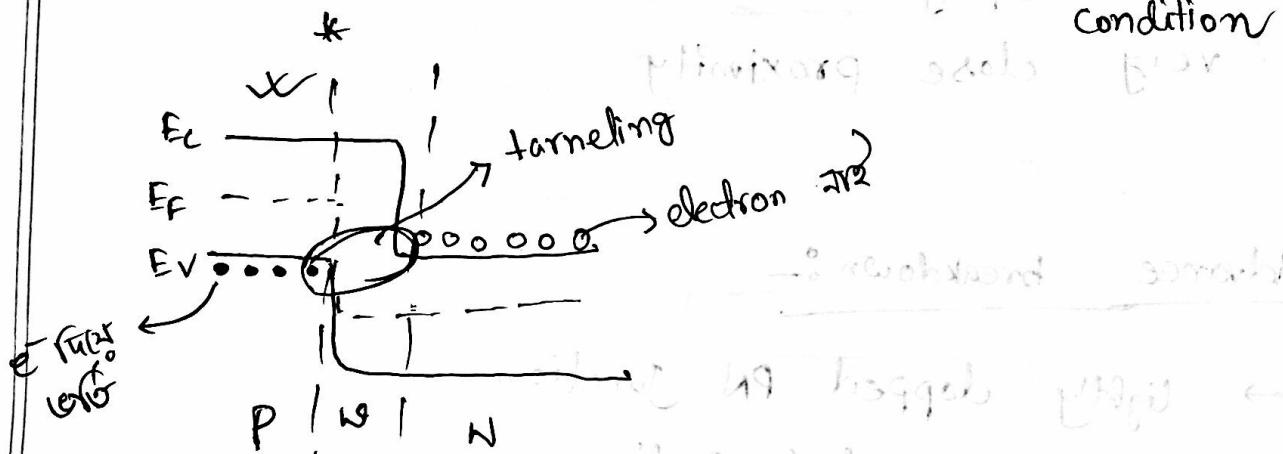
the same state in diode as in zener diode



an insulator

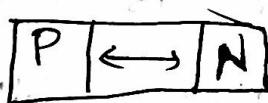

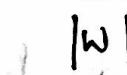in short,  $P^+ \parallel N^+$   $\rightarrow$  no electric field in center



• Q.S. in next

→ Highly dopped

→ very small depletion / space charge region

→  $e^-$  can tunnel from P to N side

→ as a result  $e^-$  can flow in RB.

the filled  $e^-$  energy state in P side (VB)

and empty CB state in N side are at  
very close proximity

### Advance breakdown :-

→ lightly dopped PN Junction



→ involve impact ionization.

→ Electric field is very high in equilibrium region

→  $e^-$  entering from P side is accelerated at very high speed and collide with lattice


→ as a result an  $e^- - h^+$  pair is created.

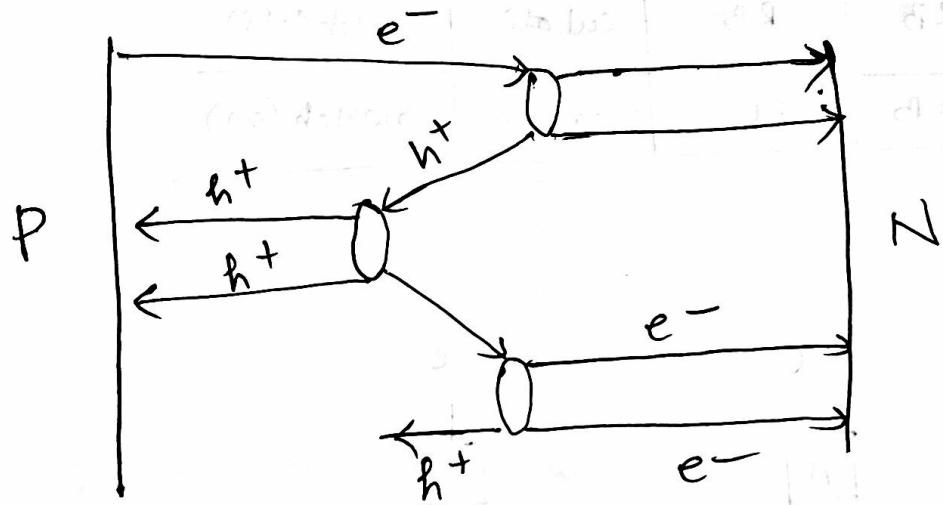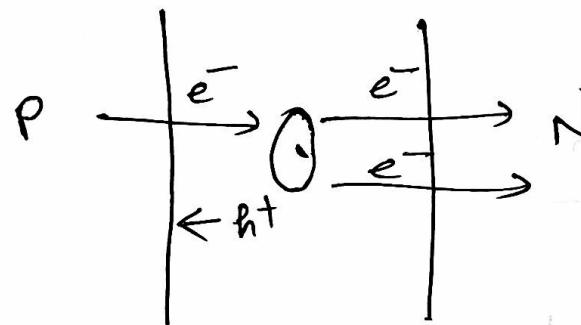→ this cause chain effect and high current can flow in RB.




Transistor :Nodes of operation :


EBJ	CBJ	Mode	Use
FB	RB	Active	Amplifier
RB	RB	Cut off	switch (off)
FB	FB	Saturation	switch (on)

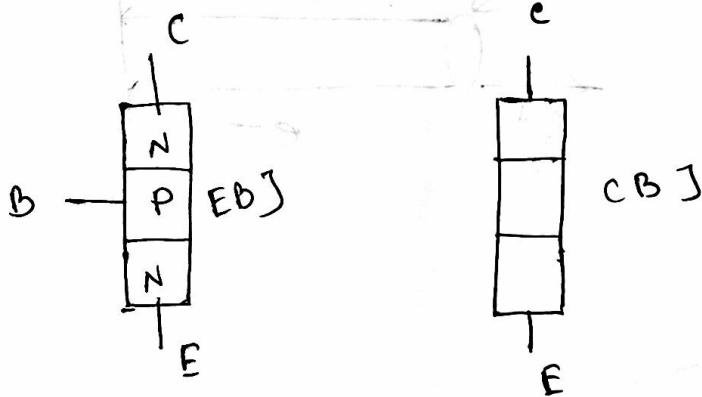

Se - 380 Page


(N-P-N)

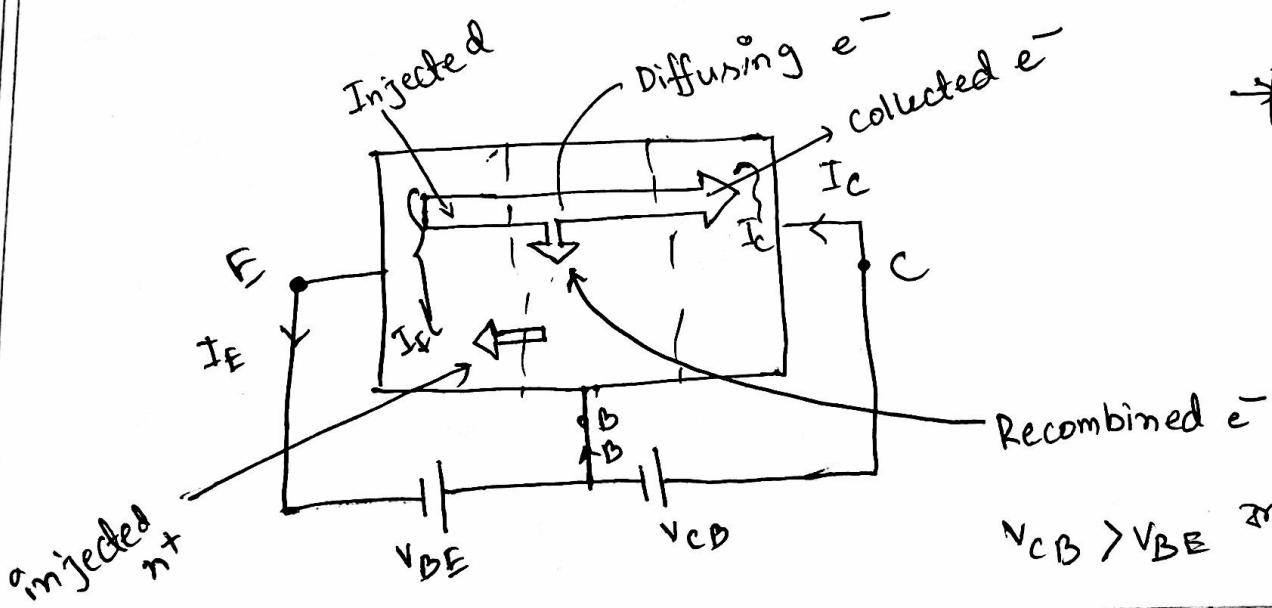

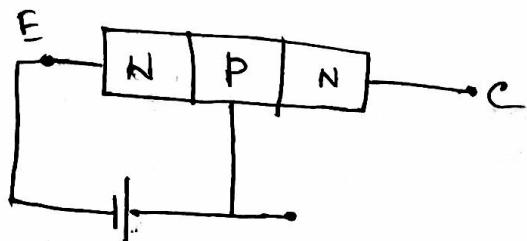

→ EBJ FB

→ majority carrier will flow across EBJ

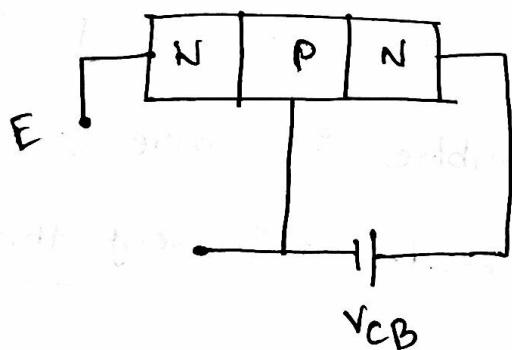

→ CBJ is RB

→ minority carrier will flow across CBJ

- EBJ is FB, then will be two component
- $e^-$  will be injected  $E \rightarrow B$ ,  $h^+$  will be injected from  $B \rightarrow E$
- $e^-$  injection is desirable (N 埸ে P ৰে ক্ষেত্ৰে  $e^-$  flow  
দৃঢ়ান্ত। আৰু P মেঘে n এ রাখ hole  
flow দৃঢ়ান্ত)
- so base is lightly doped and Emitter is heavily doped.

$$\rightarrow I_E = \text{hole current} + e^- \text{ current}$$

$$\rightarrow I_e \gg I_{h^+}$$

- \*  $V_{CB} > V_{BE}$  for activation
- \* neutralize  $\rightarrow$  recombine
  - ① do base  $\gtrsim$  doping light
  - ② base thin

### In Base :

i)  $e^-$  arrived in base from Emitter is now minority.

ii) the minority  $e^-$  will diffuse through base and reach EBJ.

iii)  $e^-$  will be swept across the EBJ to collector

iv) some  $e^-$  will recombine in base ( $\sim 5\%$ ),  
because the base is made ~~is~~ very thin.

Q3V


### Active region :

i)  $V_{CB} > V_{BE}$

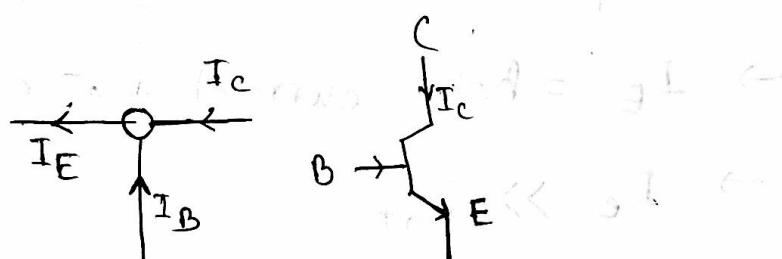ii) Emitter  $\rightarrow$  moderate length / highly doped.

Base  $\rightarrow$  very thin / low doping






Collector  $\rightarrow$  moderate length / moderate doping.



N-P-N

## BJT Configuration :

1. common base ( $c_B$ )
- 2 - common Emitter ( $c_E$ )
- 3 . common collector ( $c_c$ )

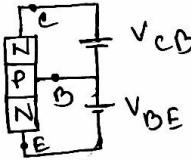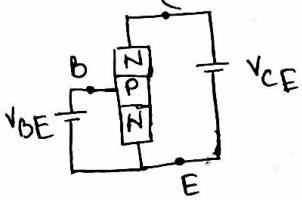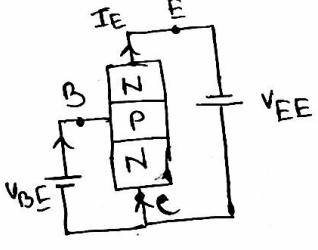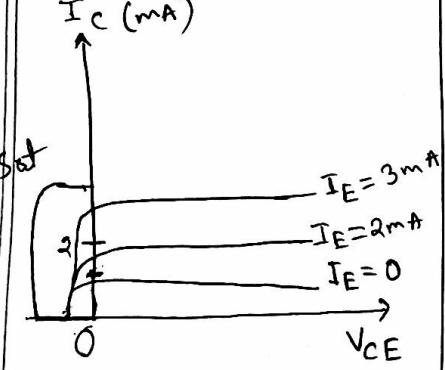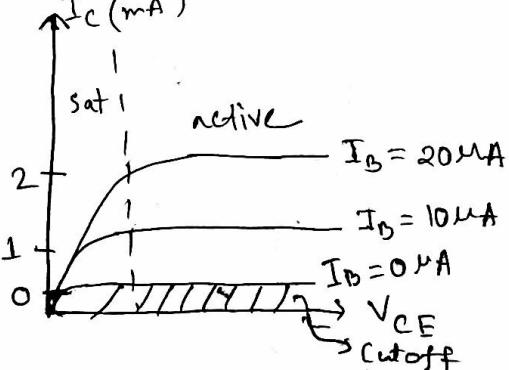$c_B$	$c_E$	$c_c$
input $\rightarrow$ Emitter out $\rightarrow$ collector	in $\rightarrow$ Base out $\rightarrow$ collector	input $\rightarrow$ Base output $\rightarrow$ Emitter
		
output change $\approx$ input change very $\approx$ $\alpha$ , $\beta$	$I_E$ $V_{CB} = 20$ $V_{CE} = 10$ $V_{CB} = 1$ $0.6$	$I_B$ $V_{CE} = 1$ $V_{CE} = 10V$ $V_{CE} = 2$ $0.6$
$I_C$ (mA)	$I_C$ (mA)	$I_C$ (mA)
		$\beta = \frac{I_C}{I_B}$
gain, $\alpha = \frac{I_C}{I_E}$		

## Relation between $\alpha$ and $\beta$ :

We know,

$$\beta = \frac{I_C}{I_B} \rightarrow \textcircled{I} \quad \alpha = \frac{I_C}{I_E} \rightarrow \textcircled{II}$$

Also,

$$I_E = I_C + I_B$$

$$\Rightarrow I_B = I_E - I_C$$

so,

$$\beta = \frac{I_C}{I_E - I_C} \rightarrow \textcircled{III}$$

$$= \frac{\frac{I_C}{I_E}}{\frac{I_E - I_C}{I_E}}$$

$$= \frac{I_C/I_E}{1 - I_C/I_E}$$

$$\boxed{\beta = \frac{\alpha}{1 - \alpha}}$$

Similarly,

$$\alpha = \frac{I_C}{I_C + I_B}$$

$$= \frac{\frac{I_C}{I_B}}{\frac{I_C + I_B}{I_B}}$$

$$\boxed{\alpha = \frac{\beta}{\beta + 1}}$$

$$I_c = \alpha I_E + I_{cBO} \quad \text{--- (1)}$$

$$\text{and, } I_E = I_c + I_B \quad \text{--- (2)}$$

so,



$$I_c = \alpha (I_c + I_B) + I_{cBO}$$

$$I_c = \frac{\alpha}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{cBO}$$

$$= \beta I_B + (\beta + 1) I_{cBO}$$

$$= \beta I_B + I_{CEO}$$
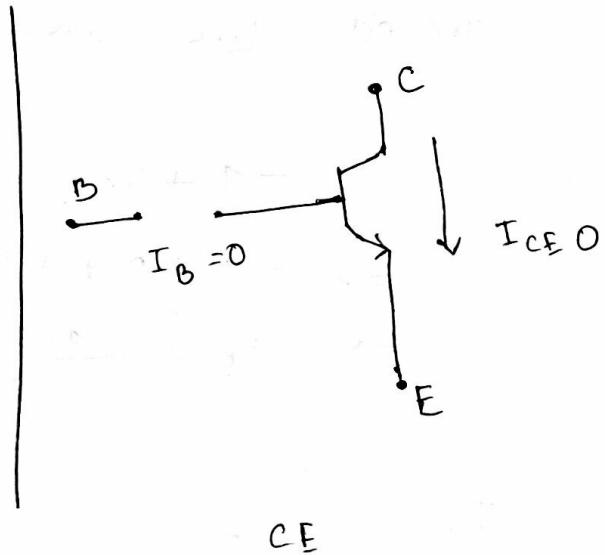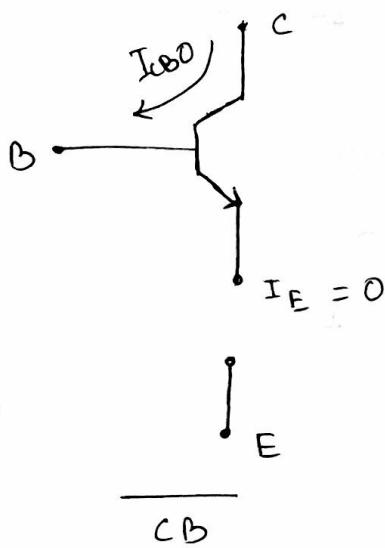
$$\left[ \begin{array}{l} \because \alpha(\beta + 1) I_{cBO} = I_{CEO} \\ \Rightarrow \beta I_{cBO} \approx I_{CEO} \end{array} \right]$$





$I_{cBO}$  = collector to base current for CB configuration

with CBJ RB and base to emitter junction open circuit.

$I_{CEO}$  = collector to emitter current when base is not connected.

Sedra

5.4

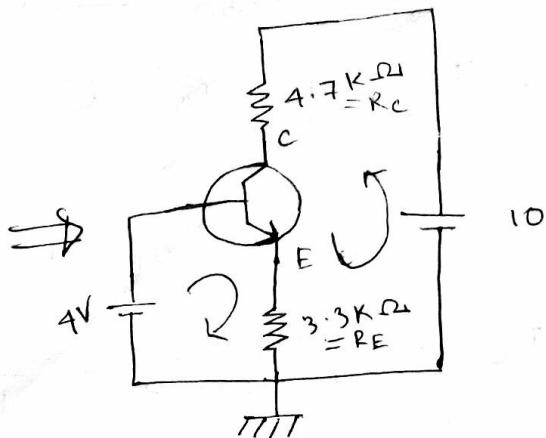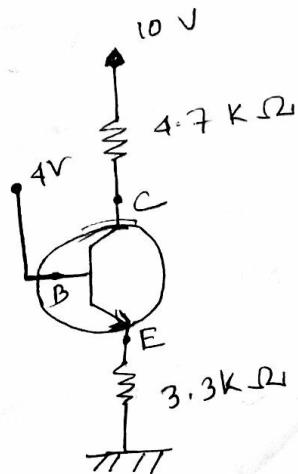

→ Because  $V_B = +4V$  and Emitter is connected to Ground. Let's assume  $V_{BE} \approx 0.7V$

$$-4 + V_{BE} + I_E R_E = 0$$

$$\Rightarrow -4 + 0.7 + I_E R_E = 0$$

$$\Rightarrow I_E = \frac{4 - 0.7}{3.3} = 1 \text{ mA}$$

$$I_C = \alpha I_E$$

$$\Rightarrow \alpha = \frac{\beta}{\beta + 1} = \frac{100}{101} = 0.99 \quad [\beta = 100 \text{ given}]$$

$$I_C = 0.99 \times 1 = 0.99 \text{ mA}$$

KVL at ,

$$-V_{CC} + I_C R_C + \underbrace{V_{CE} + I_E R_E}_{V_C} = 0$$

$$\Rightarrow -V_{CC} + I_C R_C + V_{CE} = 0$$

$$\Rightarrow V_C = 10 - I_C R_C$$

$$= 10 - 0.99 \times 4.7 K$$

$$V_C = 5.3 \text{ volt}$$



CHEK

$$V_{CB} = V_C - V_B$$

$$= 5.3 - 1$$

$$= +1.3$$

→ active mode

$$O = 3 + 38 + 3 =$$

$$38V - 3V = 35V$$

$$35V - 3V = 32V$$

$$I_B = \frac{I_E}{B+1}$$

$$= \frac{1}{101}$$

$$= 0.01 \text{ mA}$$

$$A_{vdb} = -\frac{2V}{3V} = -\frac{2}{3}$$

$$0.4V + 3V = 3.4V$$

$$3.4V - 3V = 0.4V$$


$$0.4V = 0.4V$$

$$0.4V - 3V = 0.4V - 3V$$


$$-2.6V = -0.4V$$

∴ the solution is at point T(4.6V)

Sedra Ex. 5.5

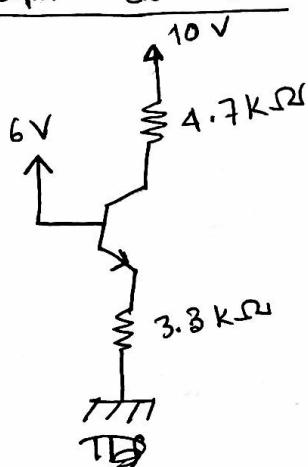

=

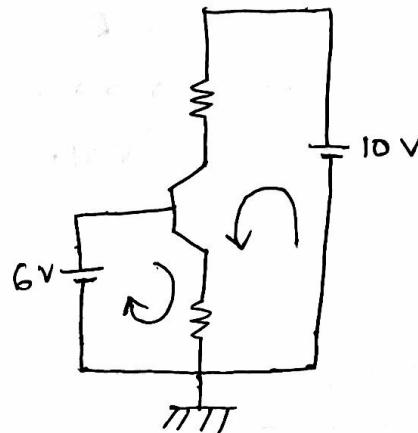

Assume active mode,

$$\begin{aligned} -V_B + V_{BE} + V_E &= 0 \\ \Rightarrow V_E &= V_B - V_{BE} \\ &= 6 - 0.7 = 5.3 \end{aligned}$$

~~Now~~

$$I_E = \frac{V_E}{R_E} = 1.6 \text{ mA}$$

Now,  $-V_{CC} + I_C R_C + V_{CE} + V_E = 0$

$$\Rightarrow -V_{CC} + I_C R_C + V_C = 0$$

$$V_C = V_{CC} - I_C R_C$$

$$= 10 - 1.6 \times 5.2$$

$$= 2.48$$

$$\begin{aligned} \text{So, } V_{CB} &= V_C - V_B \\ &= 2.48 - 6 = -3.52 \end{aligned}$$

So, BJT can't be in active state

S.S - 5.6, 5.7, 5.8

# Assume saturation mode,

$$V_E = 6 + .7 = 5.3 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = \frac{5.3}{3.3} = 1.6 \text{ mA}$$

$$V_C = V_E + V_{CE} \quad \text{Sat.}$$

$$\Rightarrow V_C = 5.3 + 1.2 = 6.5 \text{ V} \quad \text{①}$$

$$= 5.5$$

$$I_C = \frac{V_{CC} - V_C}{R} = \frac{8.5 - 5.5}{2} = 1.5 \text{ mA}$$

$$= 0.96 \text{ mA} \quad \text{②}$$

$$I_C + I_B = I_E = 1.6 \text{ mA} \quad \text{③}$$

$$\Rightarrow I_B = I_E - I_C = 1.6 - 0.96$$

$$= 0.64 \text{ mA}$$

$$= 0.64 \text{ mA}$$

$$\text{so, } \beta_{\text{forced}} = \frac{I_C}{I_B}$$

$$= \frac{0.96}{0.64}$$

$$= 1.5$$

5.


$$A_{VOC} = 0^{\circ}$$

$$A_{VBE} = 0^{\circ}$$

$$A_{VCE} = 0^{\circ}$$

$$(V)_{AV} = 0^{\circ}$$

fixed bias :

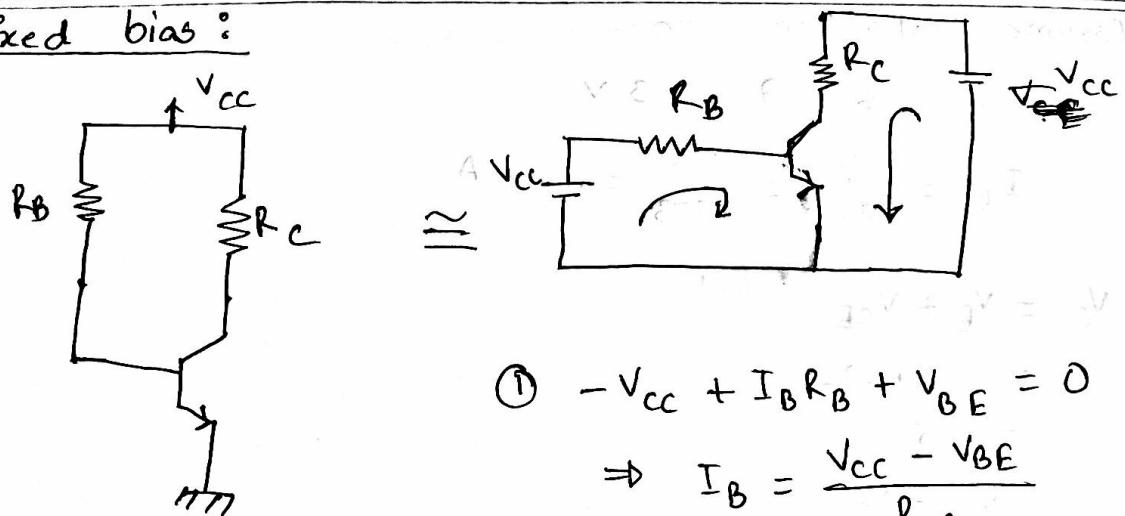

$$\textcircled{1} \quad -V_{CC} + I_B R_B + V_{BE} = 0$$


$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$\textcircled{2} \quad I_C = \beta I_B$$

$$\textcircled{3} \quad -V_{CC} + I_C R_C + V_{CE} = 0$$

$$\Rightarrow V_{CE} = V_{CC} - I_C R_C$$

Ex - 4.3

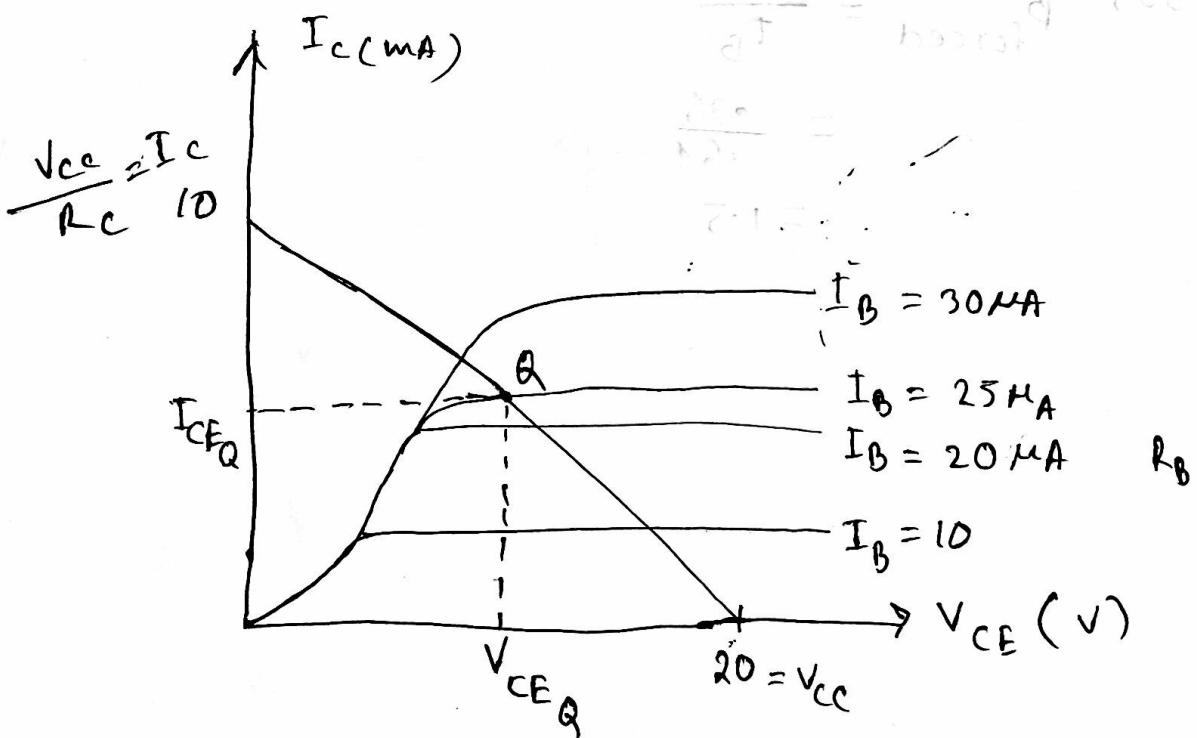

Set,  $V_{CE} = 0$

$$\therefore -V_{CC} + I_C R_C + V_{CE} = 0$$

$$\Rightarrow 0 = V_{CC} - I_C R_C$$

$$\Rightarrow I_C = \frac{V_{CC}}{R_C}$$

Again Set  $I_C = 0$

$$\therefore V_{CE} = V_{CC}$$

$$V_{CC} = 20$$

$$I_C = \frac{V_{CC}}{R_C}$$

$$\Rightarrow R_C = \frac{V_{CC}}{I_C} = \frac{20}{10} = 2 k\Omega$$



We know,

$$I_B = \frac{V_{CC} - V_{CE}}{R_B}$$

$$\Rightarrow 25 \mu A = \frac{20 - 0.7}{R_B}$$

$$\Rightarrow R_B = 772 k\Omega$$

Voltage divider bias :

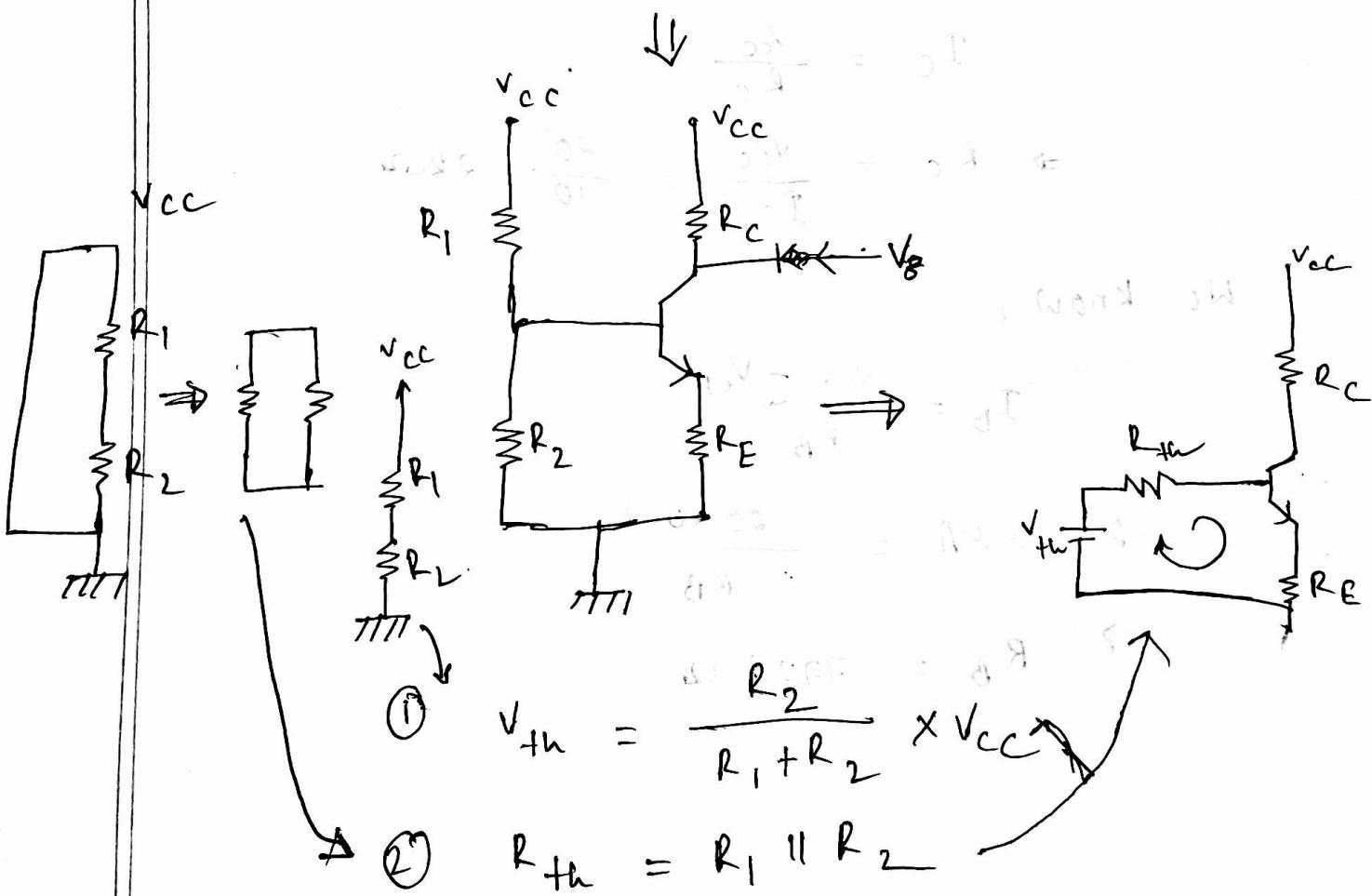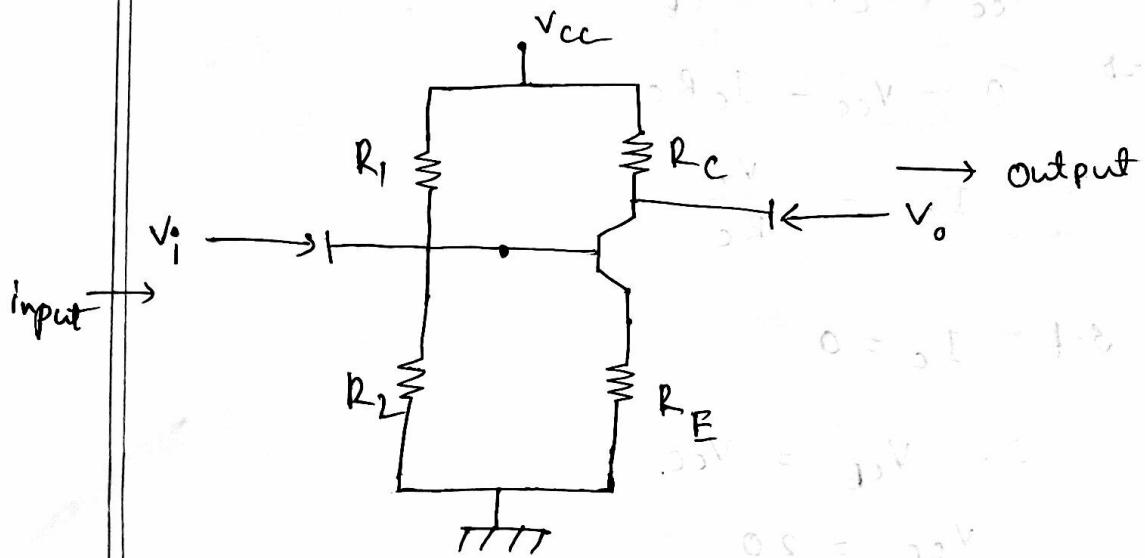

$$\textcircled{3} \quad -V_{th} + I_B R_{th} + V_{BE} + I_E R_E = 0$$

$$\Rightarrow -V_{th} + I_B R_{th} + V_{BE} + (1+\beta) I_B R_E = 0$$

$$\Rightarrow I_B = \frac{V_{th} - V_{BE}}{R_{th} + (1+\beta) R_E}$$

$$\textcircled{4} \quad I_C = I_B \times \beta$$

$$\textcircled{5} \quad -V_{cc} + I_C R_C + V_{CE} + I_E R_E = 0$$

$$\Rightarrow V_{CE} = V_{cc} - I_C (R_C + R_E) \quad [I_E \approx I_C]$$

\*  $I_C \rightarrow I_C = \beta I_B$

\*  $V_{CE} \rightarrow \text{বেঁচে রাখুন}$  : [এখন এটা  $I_B$  বেঁচে রাখতে হবে]

\*  $V_{CE} = 25V$


$$\left\{ \begin{array}{l} 25 = 25 + 8I_E \\ 0 = 25 + 8I_E \end{array} \right.$$

$\alpha \beta$  temperature sensitive

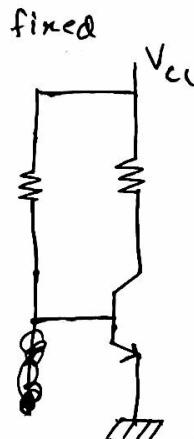
14.07.16

$$I_B = \frac{E_{th} - V_{BE}}{R_{th} + (1+\beta)R_E} \quad \text{at } T + \Delta T = f(t)$$

$$\beta = \frac{\Delta I_B}{\Delta T} = f(t)$$



voltage divider bias

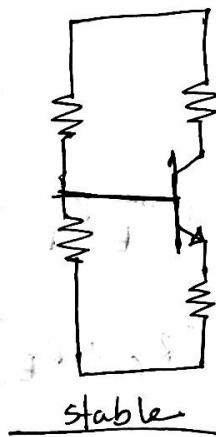



$$V_{CE} = V_c - I_C(R_C + R_E) \quad [I_C \approx I_E]$$

$\beta$	$I_C$	$V_{CE}$
100	0.89	12.39
50	0.81	12.64

Voltage change = 3%

\* Emitter stabilized bias ckt:

\* Capacitor zero bias ZTB

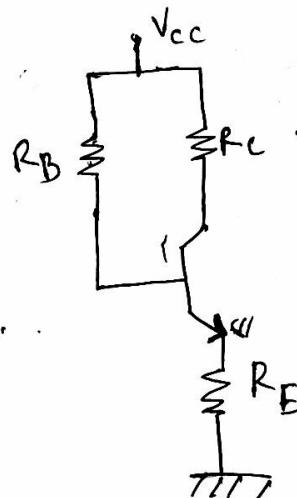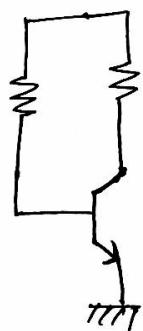

BE Loop

$$-V_{CC} + I_B R_B + V_{BE} + I_E R_E = 0$$

$$\Rightarrow V_{CC} = I_B R_B + V_{BE} + I_B (\beta + 1) R_E$$

$$= I_B [R_B + (\beta + 1) R_E] + V_{BE}$$

$$\begin{aligned} I_E &= I_C + I_B \\ &= \beta I_B + I_B \\ &= (\beta + 1) I_B \end{aligned}$$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + R_E (\beta + 1)}$$

— (1)

Ex - 4.4

### CE loop

$$-V_{ce} + I_c R_c + V_{ce} + I_E R_E = 0$$

$$\Rightarrow V_{ce} \approx V_{cc} - I_c (R_c + R_E) \quad [I_E \approx I_c]$$

Here,

$\Rightarrow$  Temp  $\uparrow\uparrow$

$\Rightarrow \beta \uparrow$

$I_B \downarrow$  to balance  $I_C \downarrow$



fixed bias

temp  $\uparrow\uparrow$

$\beta \uparrow\uparrow$

$I_B = \text{const}$ ,  $I_C \uparrow\uparrow$

Collector Feedback: (~~best~~ ckt)

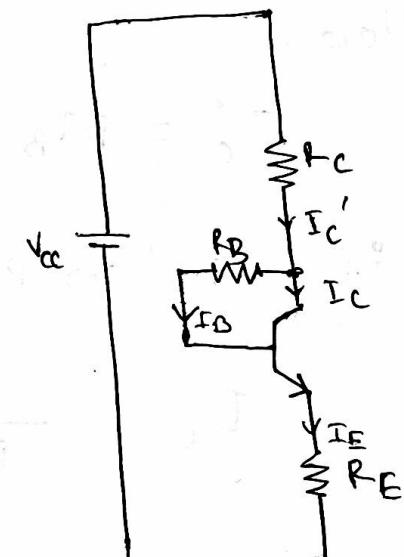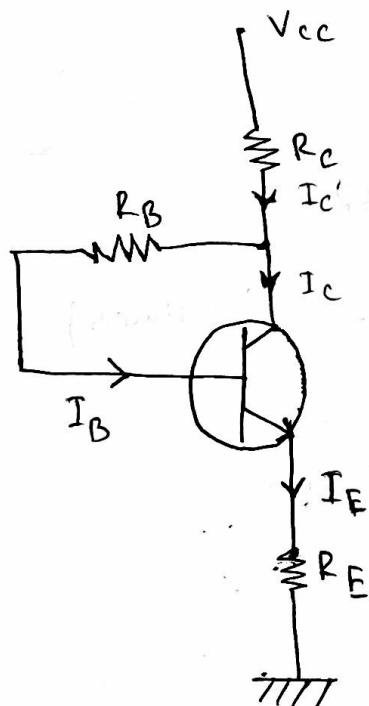

\* Collector feedback is  $\beta$  independent proved

$$-V_{CC} + I_C' R_C + I_B R_B + V_{BE} + I_E R_E = 0$$

$\therefore I_B$  is  $\mu A$   
 $I_C$  is  $mA$   
so  $I_C' \approx I_C$

$$\approx -V_{CC} + I_C R_C + I_B R_B + V_{BE} + I_E R_E = 0$$

$$\Rightarrow -V_{CC} + \beta I_B R_C + I_B R_B + V_{BE} + \beta I_B R_E = 0$$

$$\Rightarrow -V_{CC} + V_{BE} + I_B (\beta R_C + R_B + \beta R_E) = 0$$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)}$$

①

$$I_C = \beta I_B = ②$$

so

$I_E \approx I_C$ ,  $I_C = \beta I_B$

and  $I_C = \beta I_B$   
so  $I_E \approx \beta I_B$

\*  $\beta$  independent :

So,

$$I_B = \frac{V'}{R_B + \beta R'}$$

$$\left[ \begin{array}{l} R' = R_C + R_E \\ V' = V_{CC} - V_{BE} \end{array} \right]$$

Now,

$$I_C = \beta I_B = \frac{V' \beta}{R_B + \beta R'}$$

if  $\beta R' \gg R_B$  then, [10 times]

$$I_C = \frac{V' \beta}{\beta R'} = \frac{V'}{R'}$$


$$-V_{CC} + R_C I_C' + V_{CE} + I_E R_E = 0$$

$$\Rightarrow -V_{CC} + R_C I_C + V_{CE} + I_C R_E = 0$$


$$\Rightarrow V_{CE} = V_{CC} - I_C (R_C + R_E) \quad \text{--- (3)}$$

with base  
 $I_C' \approx I_C$   
 $I_C \approx I_E$

\* Find out load line & Q point.

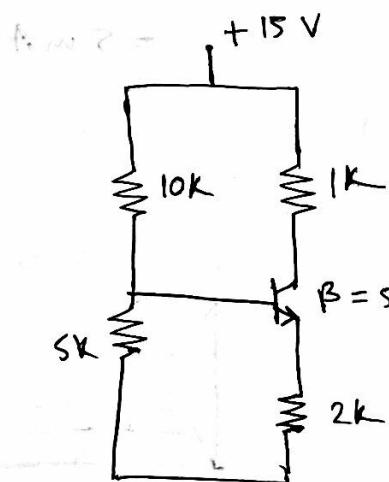

$\Rightarrow$

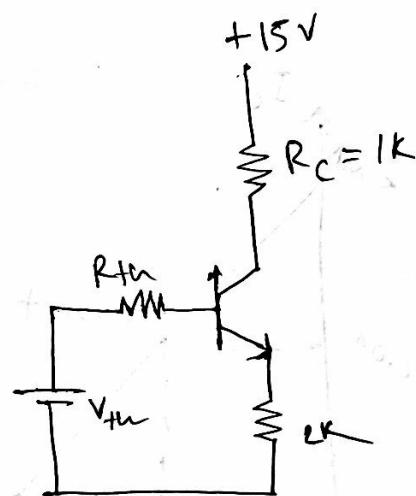

$$V_{th} = \frac{5k}{10+5k} * 15V = 5V$$

$$R_{th} = 5k \parallel 10k = 3.33k\Omega$$

$$\begin{aligned} I_C &= \beta I_B \\ &= (50 \times 40.84) \mu A \\ &= 2.04 \text{ mA} \end{aligned}$$

$$\begin{aligned} I_B &= \frac{V_{th} - V_{BE}}{R_{th} + (1+\beta)R_E} \\ &= \frac{5 - 0.7}{3.33 + (1+50)2k} \\ &= 40.84 \mu A \end{aligned}$$

$$\begin{aligned} V_{CE} &= V_{CC} - I_C (R_C + R_E) \\ &= 15 - 2.04 (1+2) \\ &= 8.87 \text{ Volts} \end{aligned}$$

### Load Line




$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Now,  $I_C = 0$


$$V_{CE} = V_{CC} = 15V$$

$$V_{CE} = 0$$

$$I_C = \frac{V_{CC}}{3k} \\ = 5mA$$

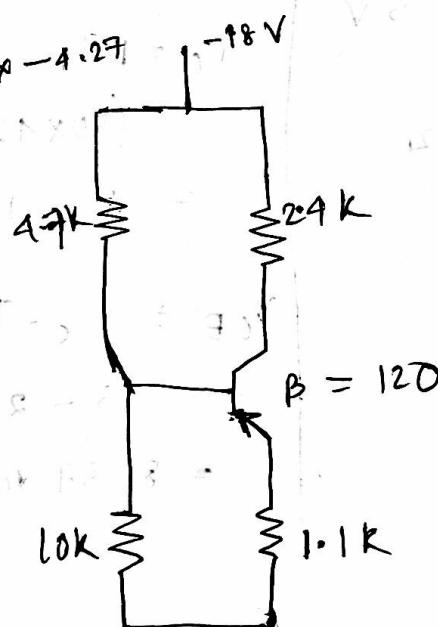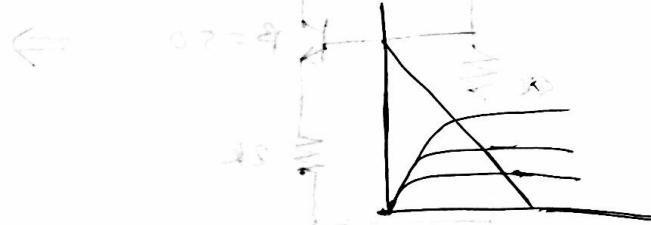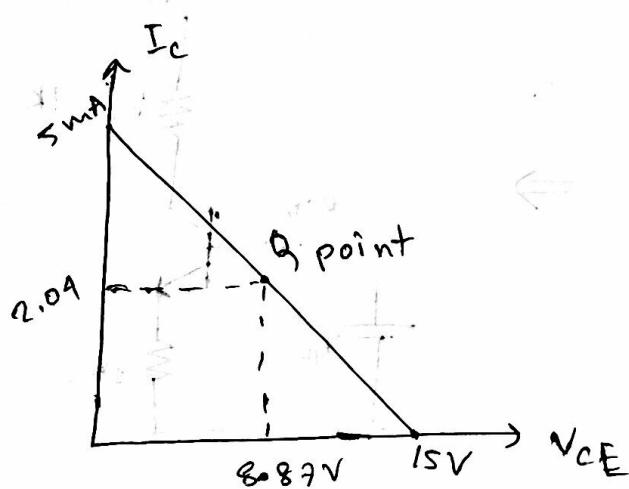

$\equiv$

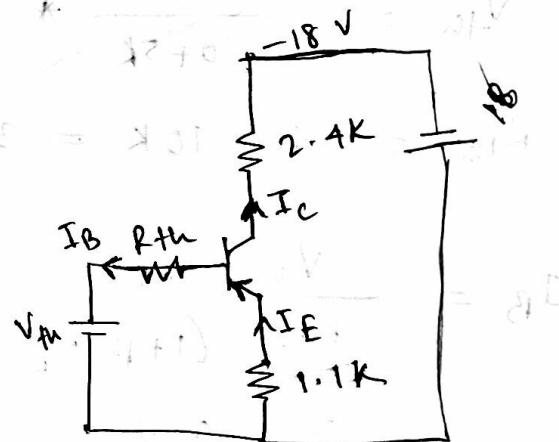

$$R_{th} = 47k \parallel 10k \\ = 8.25k$$

$$V_{th} = \frac{10k}{10k + 47k} * -18 = -3.16V$$

\* clipper, clamper - quiz

### BE Loop.

$$I_E R_E - V_{BE} + I_B R_{th} - 3 \cdot 16 = 0$$

$$\Rightarrow I_B = \frac{3 \cdot 16 + V_{BE}}{R_{th} + R_E(1+\beta)} = 17.40 \mu A$$

Now.

$$I_E = (1+\beta) I_B = 2.1 \text{ mA}$$

### CE Loop

$$I_E R_E - V_{CE} + I_C R_C - V_{CC} = 0$$



$$\Rightarrow I_C R_E - V_{CE} + I_C R_C - V_{CC} = 0$$

$$\Rightarrow V_{CE} = I_C (R_E + R_C) - V_{CC}$$

$$= 7.35 - 18$$

=



# Field Effect Transistor : (FET)

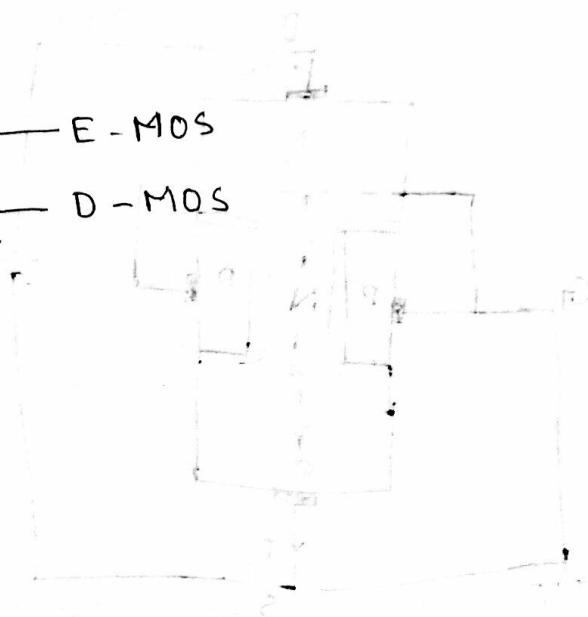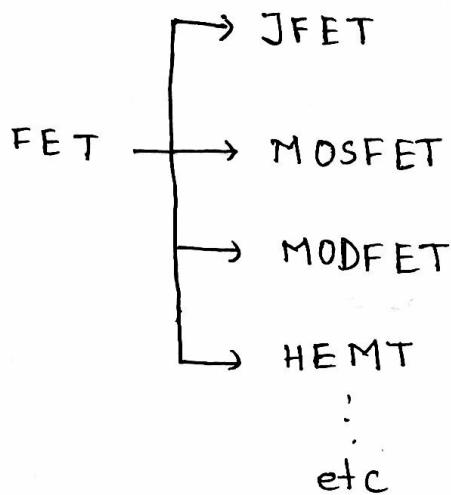

## JFET :

→ Junction Field Effect Transistor

→ N ch and P channel

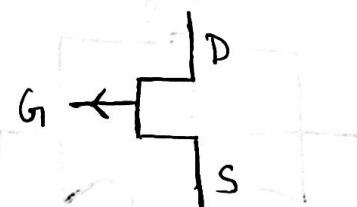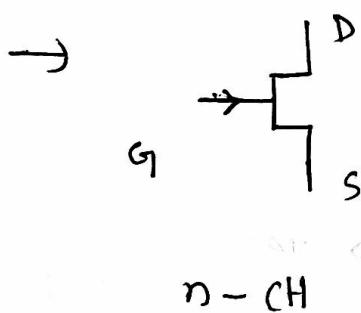


G - Gate

D - Drain


S - Source

## Construction n-CH JFET:

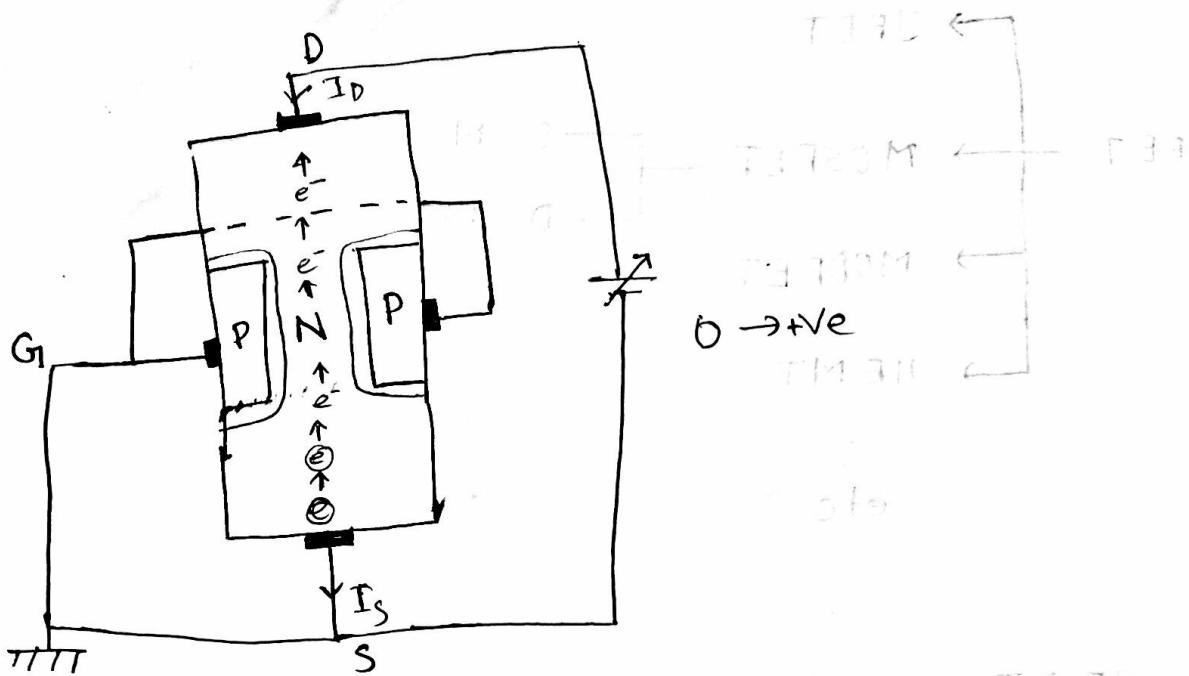
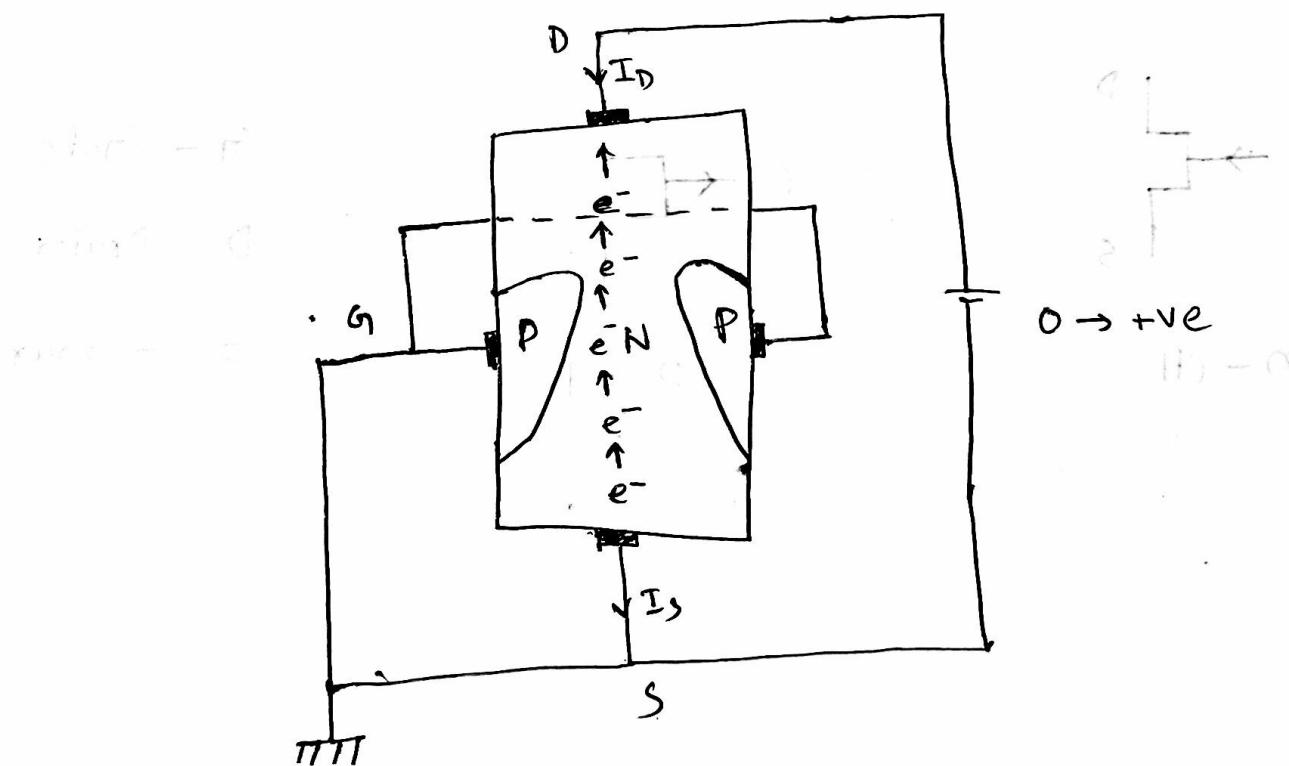
### Operation:


If  $V_{GS} = 0V$  and  $V_{DS} \rightarrow$  Some positive value



→ When  $V_{DS}$  is applied there will be a current  $I_D$  and in the Depletion layer will be wide in the top of both p type material.

→ When  $V_{DS} \uparrow$  the depletion layer will increase and the resistance will increase due to narrowing of channel.



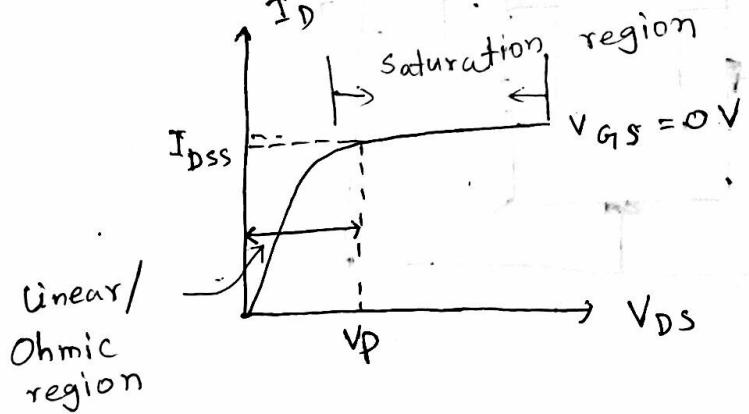
→ At  $V_{DS}$  = some positive value the depletion region of both P-type region will touch. This is called pinch off and voltage called pinch off voltage ( $V_p$ ) .



→ At  $V_{DS} > V_p$ , the current will be fixed at  $I_D = I_{DSS}$  (JFET act like constant current source ,
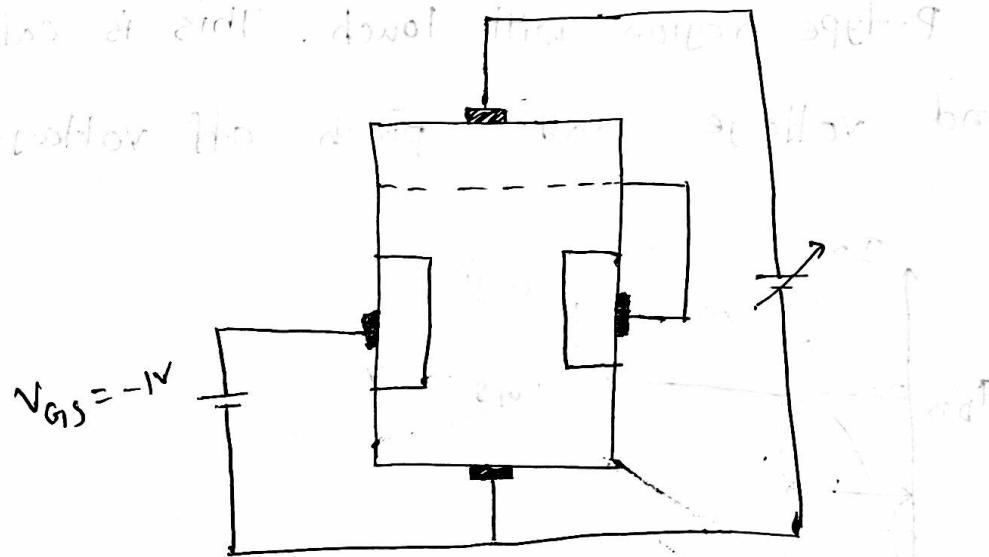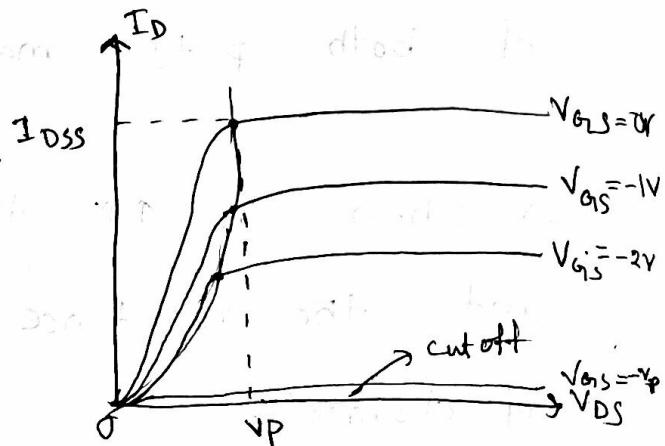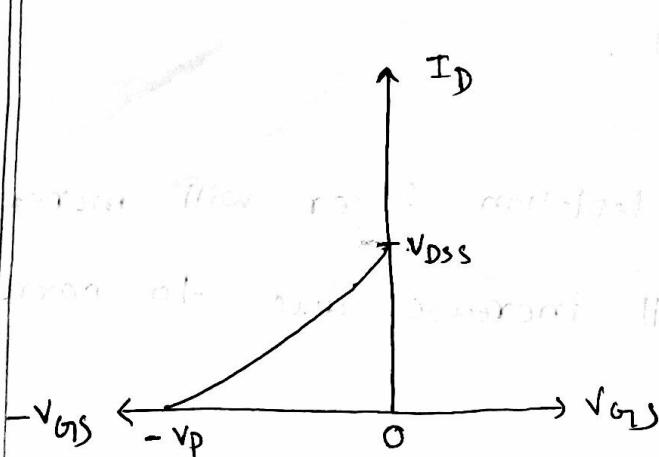
## Operation:

If  $V_{GS} < 0V$  and  $V_{DS} \rightarrow$  some positive value,



\* MOSFET ~~concrete~~ construction

Equation:

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^n$$


$V_{GS}$  → control voltage

for  $V_{GS} = 0V$ ,  $I_D = I_{DSS}$  (max)



for  $V_{GS} = -V_P$ ,  $I_D = 0$

$$\Rightarrow I_D \approx I_S$$

$$\Rightarrow I_G \approx .0A$$

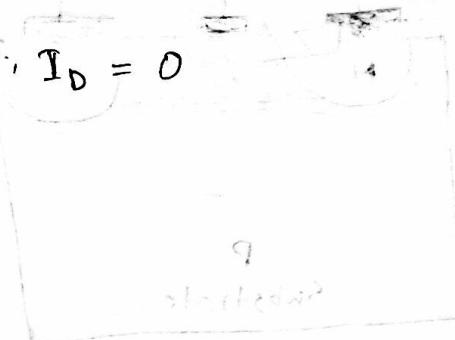

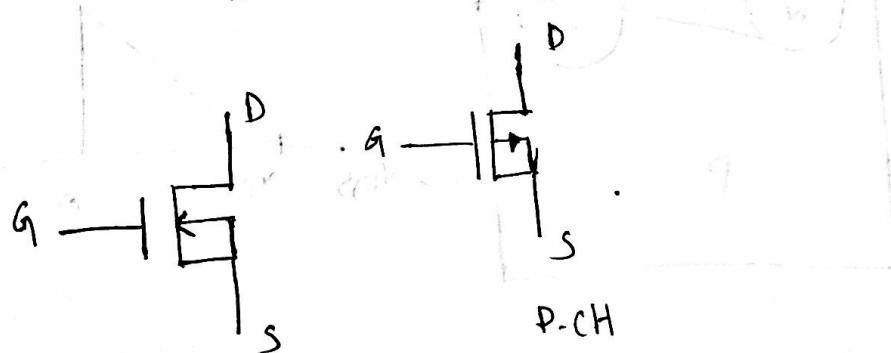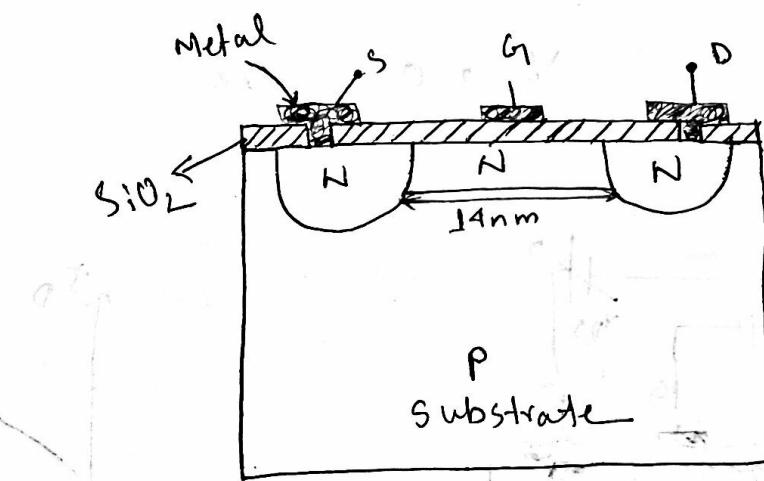④ Depletion type MOSFET: (Metal oxide semiconductor Field Effect Transistor)



N-CH



\* MOSFET  $\rightarrow$  9 factors current (2nd page w/)

Next Quiz

31/07/16
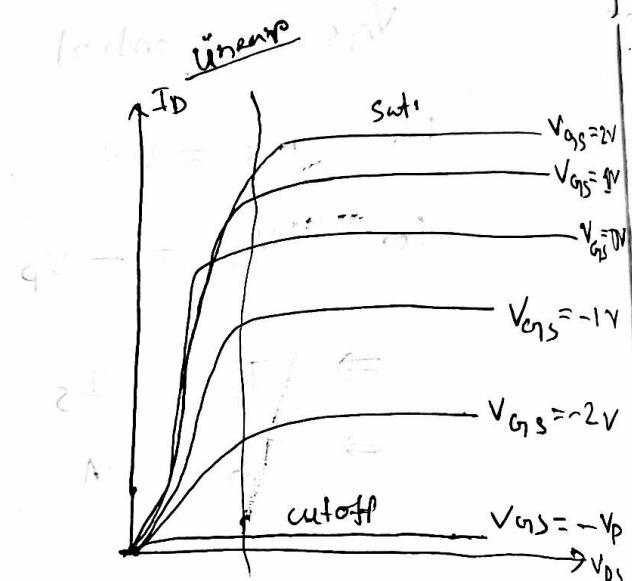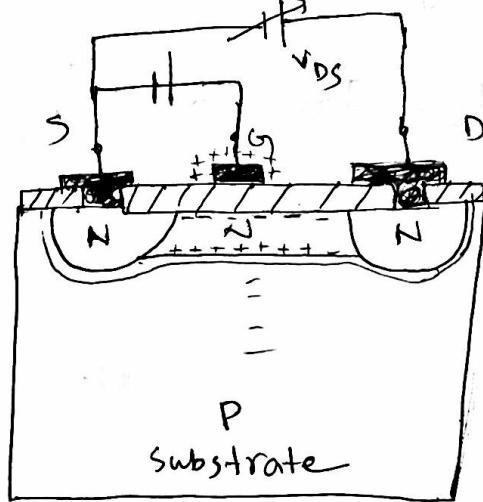
## Operation



$$V_{GS} = 0 \text{ V} \quad \text{and} \quad V_{DS} \rightarrow +\text{Ve}$$



$$V_{GS} = +\text{Ve}$$



$$V_{DS} > 0 \rightarrow +\text{Ve}$$

$$V_G = -\text{Ve}$$

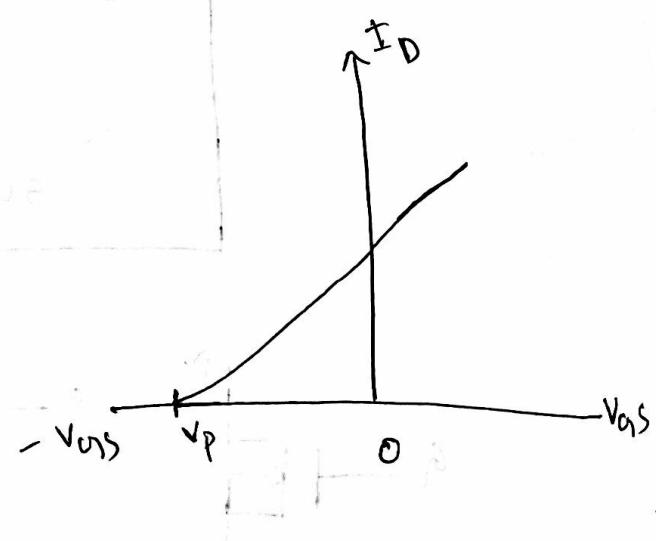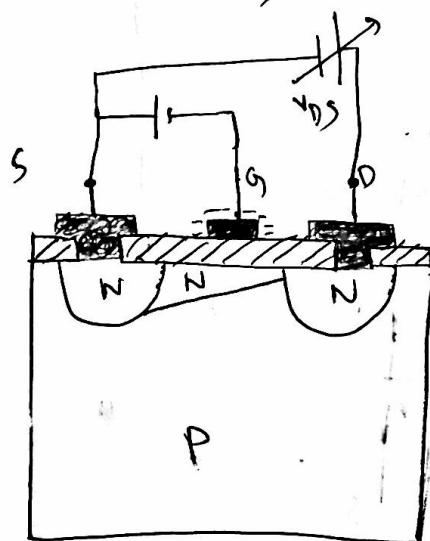



## Enhancement type MOSFET :-

Symbol

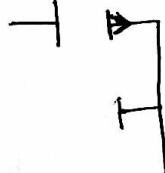
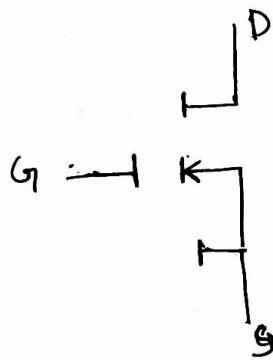


P channel

N channel

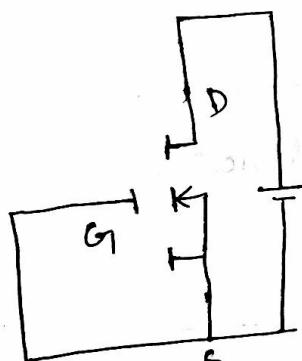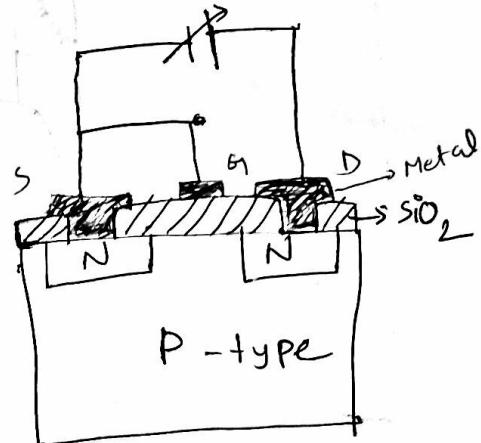


n channel

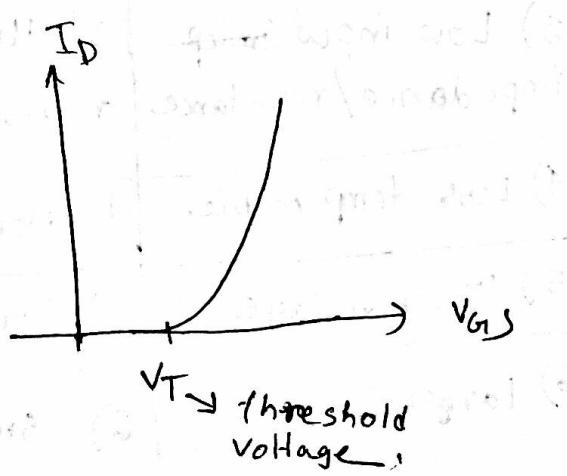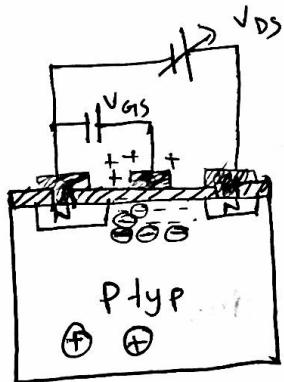

VT  $\rightarrow$  threshold voltage

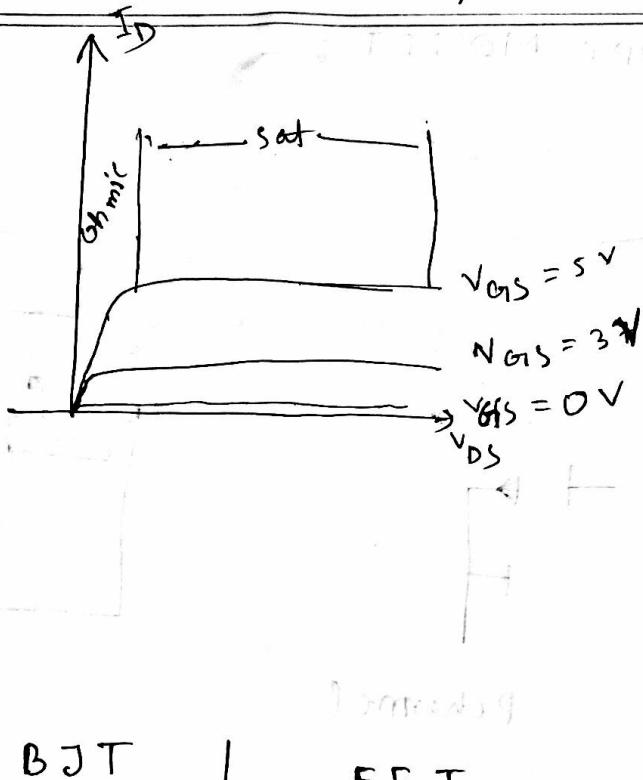- \* Transistor  $\rightarrow$  current control device ( $I_B$ )
  - \* FET  $\rightarrow$  voltage control device ( $V_{GS}$ )
- \* Draw JFET, I operation  
difference  $\rightarrow$  BJT/FET



BJT

FET

1) Bipolar device, depends on both $e^-$ and hole for conduction	1) Unipolar device, depends on $e^-$ or $h^+$ for conduction
--	--

2) Current controlled device, $I_C = f(I_B)$	2) Voltage controlled device $I_D = f(V_{GS})$
--	--

3) Low input impedance	3) High input impedance
------------------------	-------------------------

4) Less temp stable	4) More temp stable
---------------------	---------------------

5) Higher voltage gain	5) Lower voltage gain
------------------------	-----------------------

6) Larger in size	6) Smaller in construction than BJT
-------------------	-------------------------------------

## Opamp :

Operational amplifier :


A high gain amplifier which can do many mathematical operation and to which a feedback can be used to control its gain and output characteristics.

**Operation** (addition, subtraction, multiplication, differentiation, integration etc)

**Amplification**

amplify input signal


Pin configuration :

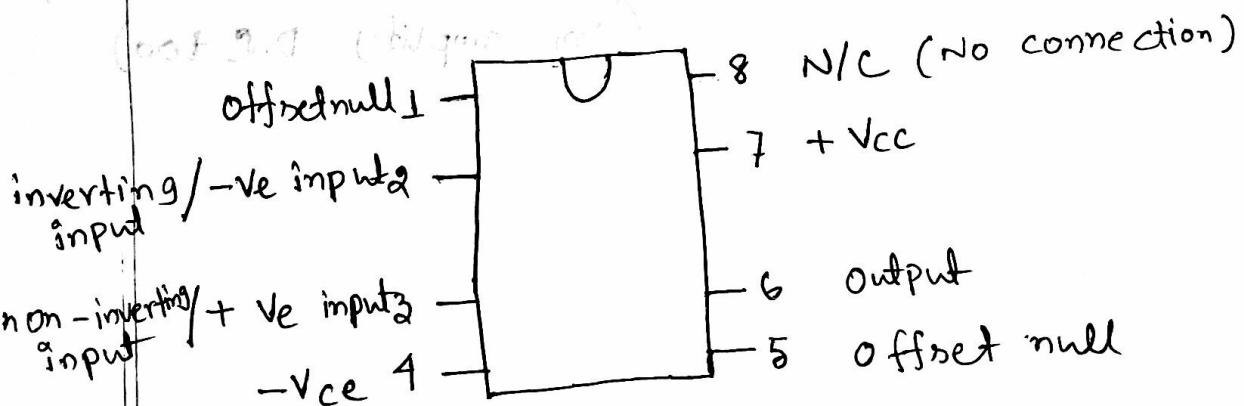

offset null - is used to provide a way to balance out the internal voltage.

\* 14 Br BJT + MOSFET combination

Symbol of opamp :

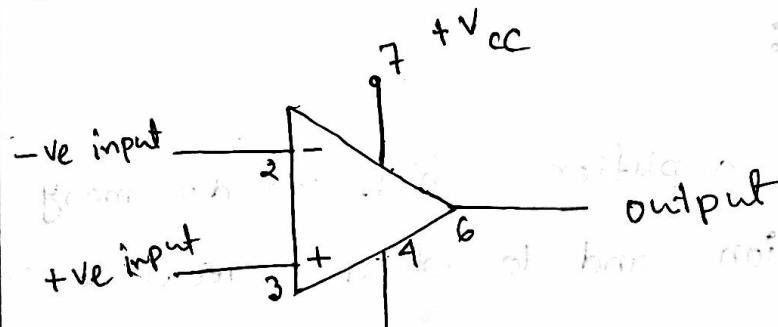


Characteristics of Ideal opamp :

Input characteristics

Output characteristics

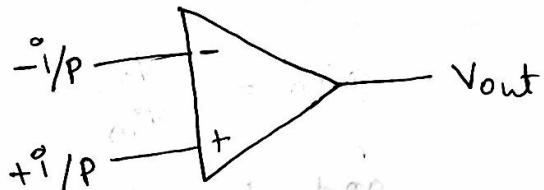- 1) I/p impedance —  $\infty$
- 2) O/p impedance —  $0$
- 3) gain (open loop) —  $\infty$
- 4) BW (bandwidth) —  $\infty$
- 5) Direct coupling — no capacitor, so ~~no~~ direct coupling  
(can amplify D.C too)

Open loop voltage gain: more beauty from truth



$$V_o = E_d \times A_{OL} \quad | \quad E_d = \text{difference between input voltages}$$

$$V_o = \text{output voltage} \quad | \quad A_{OL} = \text{open loop gain}$$

ex  $- + I/P \rightarrow 2V$   
 $- - I/P \rightarrow 1V$

$$V_{out} = (2-1) \times 10$$

$$= 10V$$


if gain ( $A_{OL} = \infty$ ) then  $V_{out} = \infty$  but  $V_{out}$  should be limited within  $+V_{ce}$  and  $-V_{cc}$ .

so  $\max V_{out} = +V_{cc}$

$\min V_{out} = -V_{ce}$

Virtual short, virtual ground:

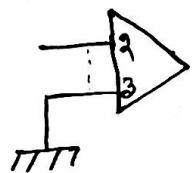pin 2 and 3 are said to be virtually short.



$$\text{gain} = \frac{V_o}{V_{in}}$$

$$\text{and } E_d = V_3 - V_2$$

$$V_o = E_d * \text{gain}$$

$$\Rightarrow E_d = \frac{V_o}{\text{gain}}$$

$$\Rightarrow V_3 - V_2 = \frac{V_o}{\infty}$$

$$\Rightarrow V_3 - V_2 = 0$$

$$\Rightarrow V_3 = V_2$$

$\therefore$  open loop gain =  $\infty$

or  $E_d = 0$  and  $(\infty = 10^6)$  vice versa

Operational mode: either optimal or block




1) Comparator: without feedback

2) Amplifier: with feedback



Comparator :

S. M. T. Zadeh 10852 859005



Non inverting zero crossing detector :

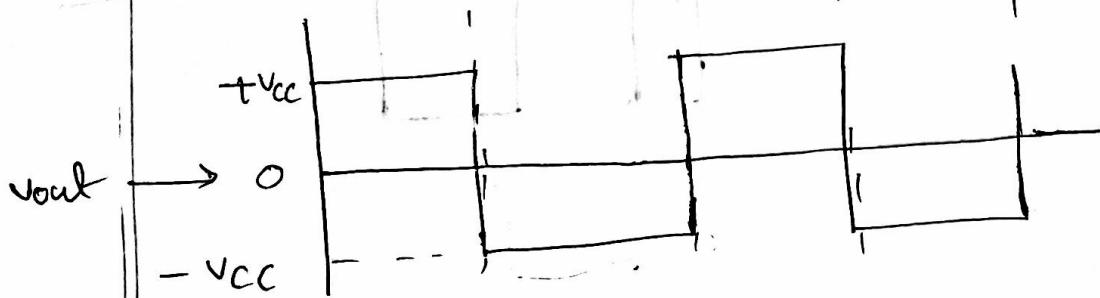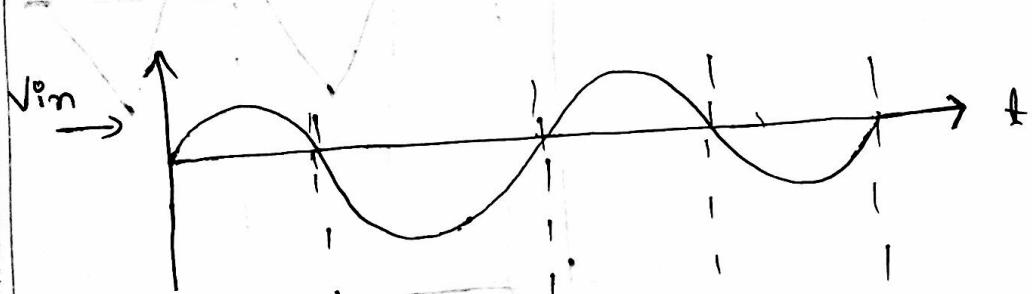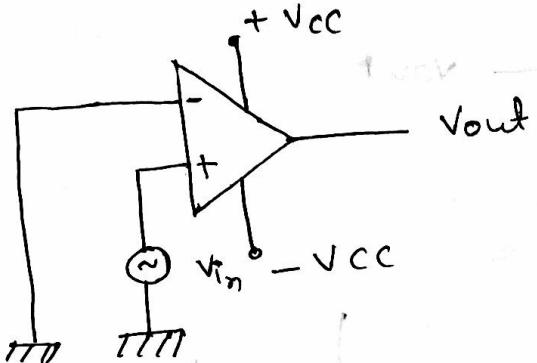



## Positive level detector

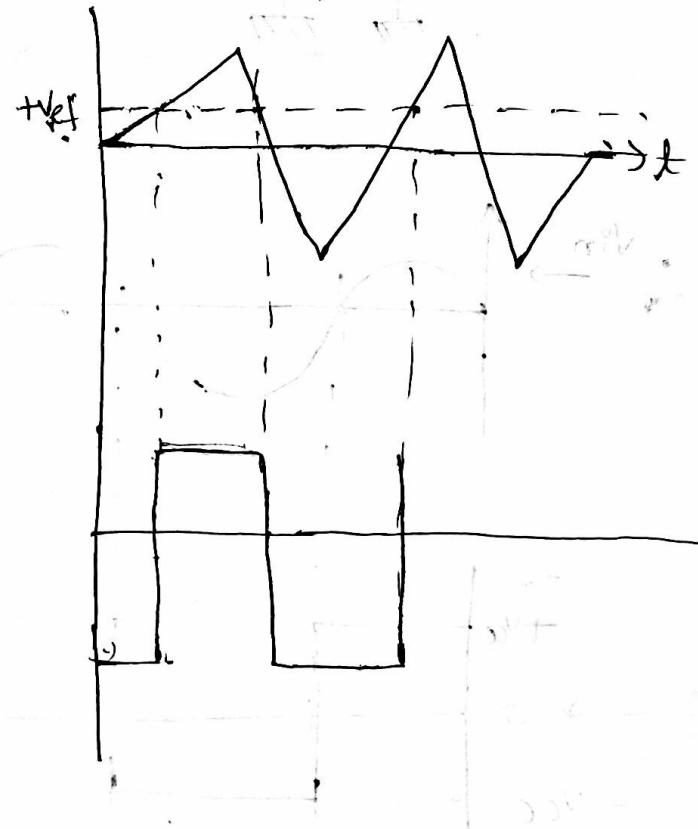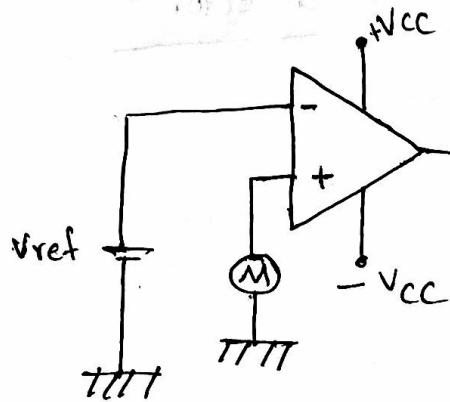



## Negative level detector :

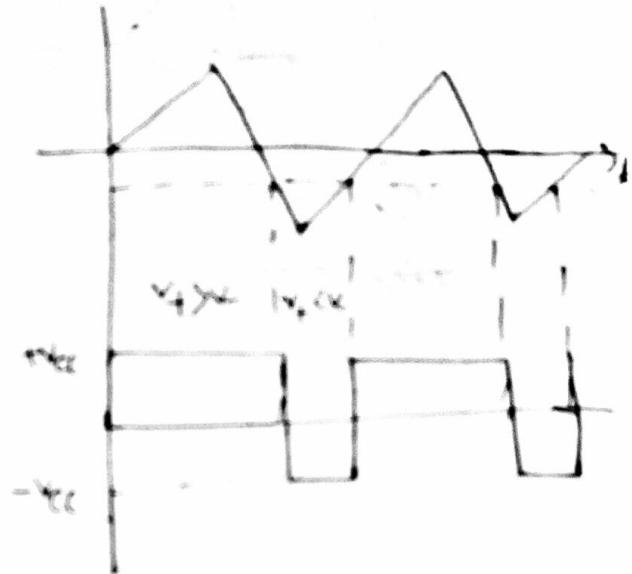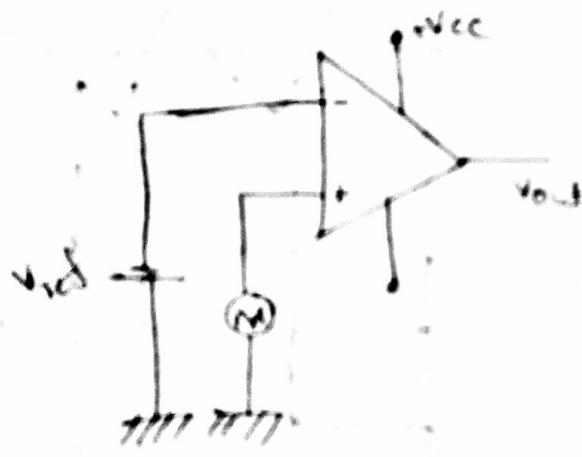


## Inverting zero crossing detector :

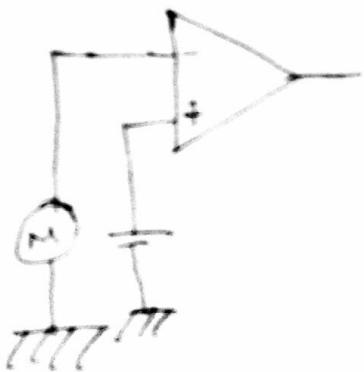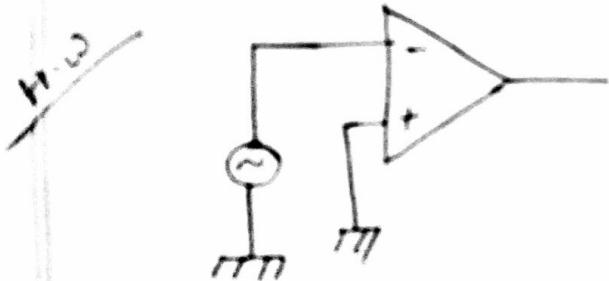

Negative level detector:

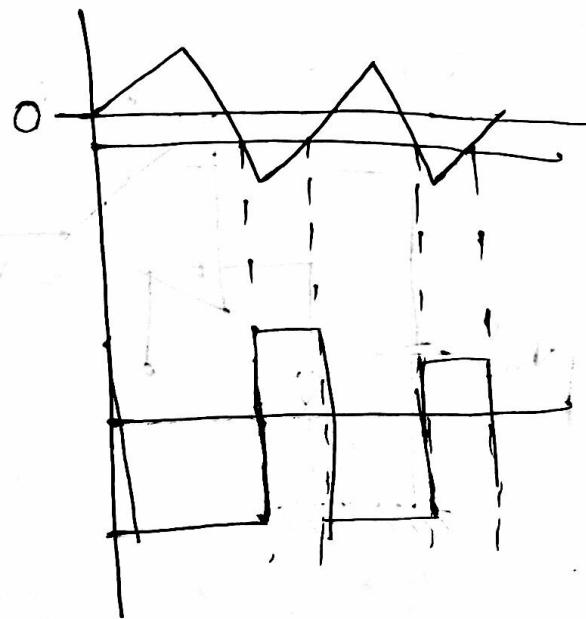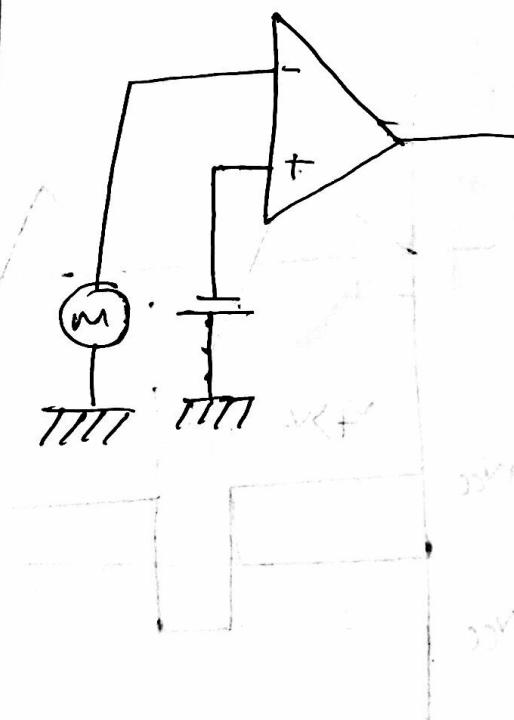

3 variable can be used to control


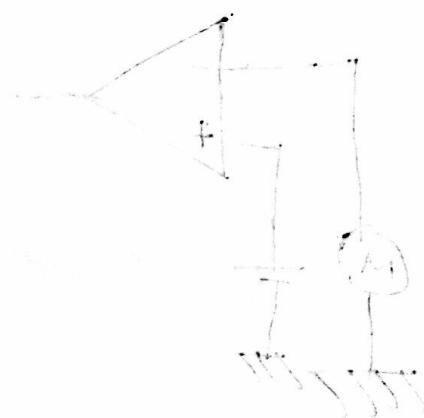


\* +/ - terminal দিয়ে current মাপো আৰি, so 2 input impedance =  $\infty$

04-08-16

close loop:

inverting amplifier:

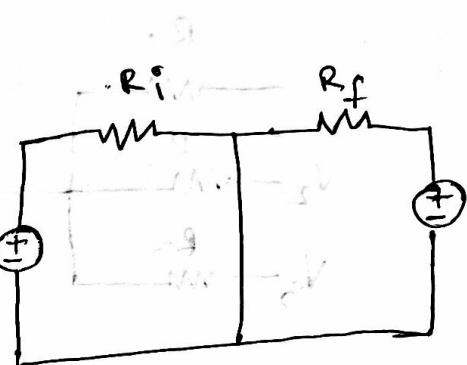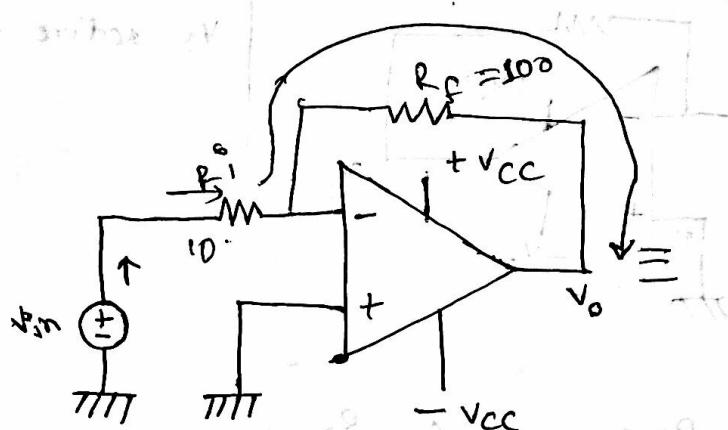

$$v_{in} = iR_i \left( \frac{v_o}{R_f} + s \frac{v_o}{2s} + s \frac{v_o}{s} \right) =$$

$$\Rightarrow i = \frac{v_{in}}{R_i}$$


Also,  $iR_f + v_{out} = 0$

$$\Rightarrow \frac{v_{in}}{R_i} R_f + v_{out} = 0$$

$$\Rightarrow v_{out} = -\frac{R_f}{R_i} v_{in}$$

gain,  $\frac{v_{out}}{v_{in}} = -\frac{R_f}{R_i} v_{in}$

### Inverting Adder:

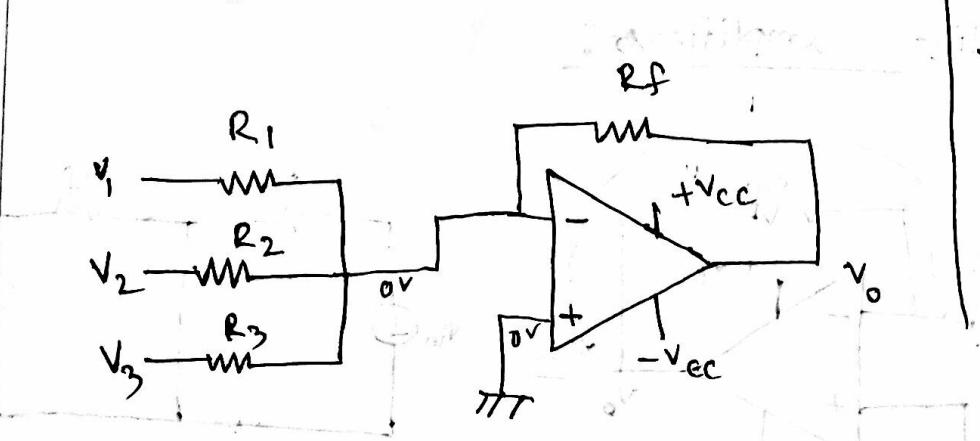

$$V_1 \text{ active } V_{o1} = -\frac{R_f}{R_1} V_1$$

$$V_2 \text{ active } V_{o2} = -\frac{R_f}{R_2} V_2$$

$$V_3 \text{ active } V_{o3} = -\frac{R_f}{R_3} V_3$$



$$V_o = -\frac{R_f}{R_1} V_1 + \left(-\frac{R_f}{R_2}\right) V_2 + \left(-\frac{R_f}{R_3}\right) V_3$$

$$= -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3\right)$$

if,  $R_1 = R_2 = R_3 = R_f$

$$V_o = -(V_1 + V_2 + V_3)$$

### Non-Inverting amplifier:

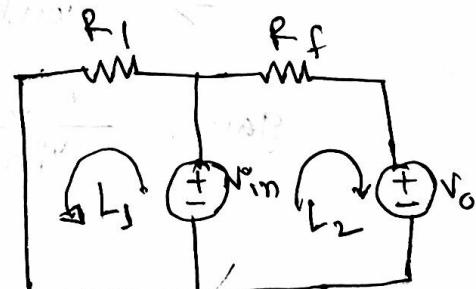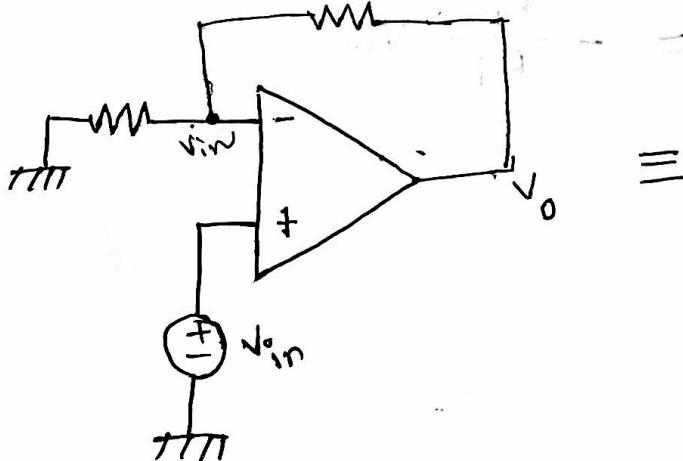

loop 1

$$-V_{in} + R_1 I = 0$$

$$\Rightarrow I = \frac{V_{in}}{R_1}$$

loop 2

$$-V_{out} + I R_f + V_{in} = 0$$

$$\Rightarrow V_{out} = I R_f + V_{in}$$

$$\Rightarrow V_{out} = V_{in} + \frac{V_{in}}{R_1} R_f$$

$$V_{out} = V_{in} \left( 1 + \frac{R_f}{R_1} \right)$$

$$\text{gain } \frac{V_o}{V_i} = 1 + \frac{R_f}{R_1} = 2$$

$$\Rightarrow \frac{R_f}{R_1} = 1$$

$$\therefore R_f = R_1$$

gain 3 time,


$$1 + \frac{R_f}{R_1} = 3$$

$$\frac{R_f}{R_1} = 2$$

$$\therefore R_f = 2R_1$$




- Non Inverting Adder :

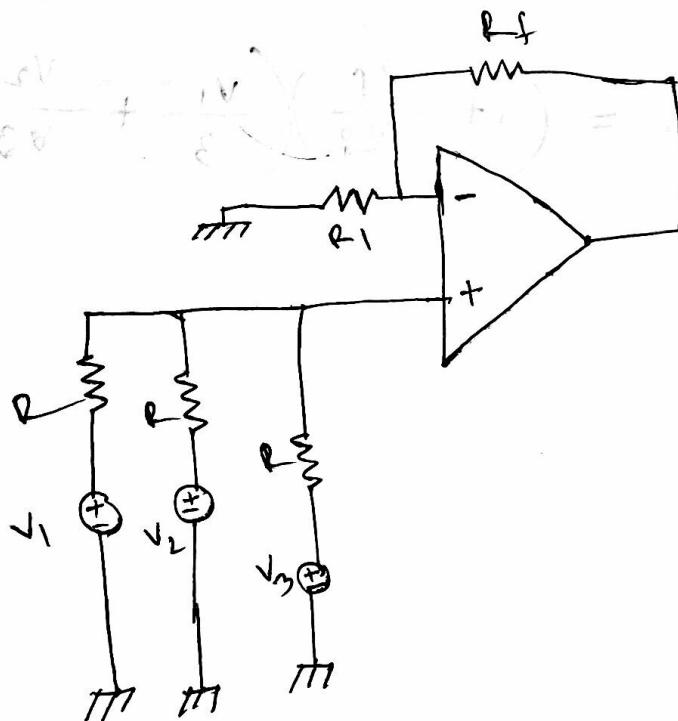

When  $V_1$  active,
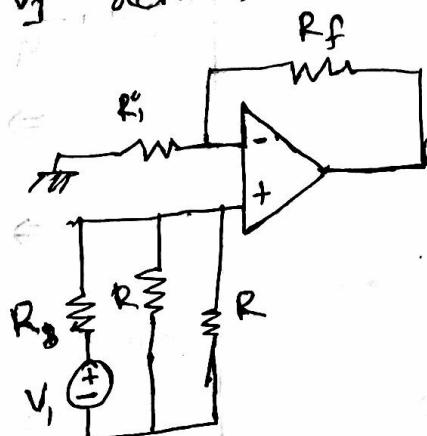
$$R \parallel R = \frac{R \times R}{R+R} = \frac{R}{2}$$




$$V_{1o1} = \frac{R/2}{R+R/2} V_1$$

$$= \frac{R/2}{3R/2} V_1$$

$$0 = aV + \beta V + \gamma V \\ = \frac{R}{2} \times \frac{2}{3R} V_1$$
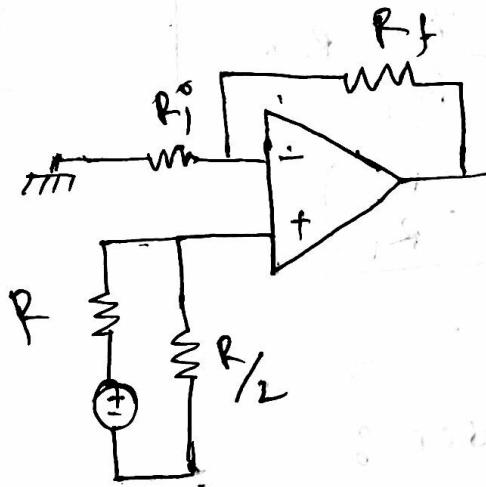
$$aV + \beta V = \gamma V \\ = \frac{V_1}{3}$$



Similarly,


$$V_{2o1} = \frac{V_2}{3}$$

$$V_{3o1} = \frac{V_3}{3}$$

$$\therefore V_{out} = \left(1 + \frac{R_f}{R_i}\right) \left(\frac{V_1}{3} + \frac{V_2}{3} + \frac{V_3}{3}\right)$$

◻ Voltage follower / Buffer:

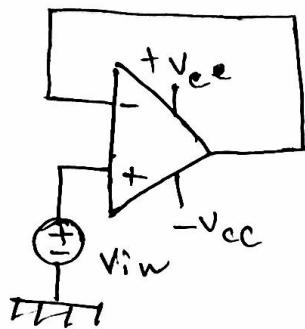→ unity gain amplifier / source follower / isolation amplifier / Buffer



$$V_o = \left(1 + \frac{R_f}{R_{o_1}}\right) V_{in}$$


$$R_f = 0 \Omega$$

$$R_{o_1} = \infty$$

$$V_o = (1+0) V_{in}$$

$$V_o = V_{in}$$

Problem :

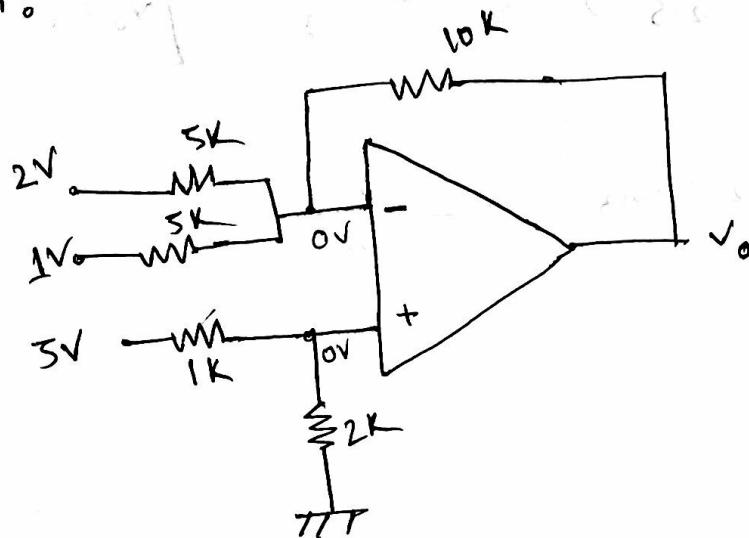

Soln. When  $2V$  active ,  
 $V_{o1} = \frac{10}{5} (-2) = -4V$   $\left[ V_o = -\frac{R_f}{R_i} V_{in} \right]$

When  $1V$  active ,

$$V_{o2} = \frac{10}{5} (-1) = -2V$$


When  $5V$  active ,

$$\begin{aligned} V_x &= \frac{2K}{2K+1K} \times 5 \\ &= \frac{2K}{3K} \times 5 \\ &= \frac{10}{3} \end{aligned}$$

$$R_{in} = 511 = \frac{5 \times 5}{5+5} = 2.5$$

$$50, \quad V_{o_3} = \left(1 + \frac{10}{2.5}\right) \frac{10}{3} = \frac{50}{3} \quad [V_o = \left(1 + \frac{R_f}{R_i}\right) V_{in}]$$
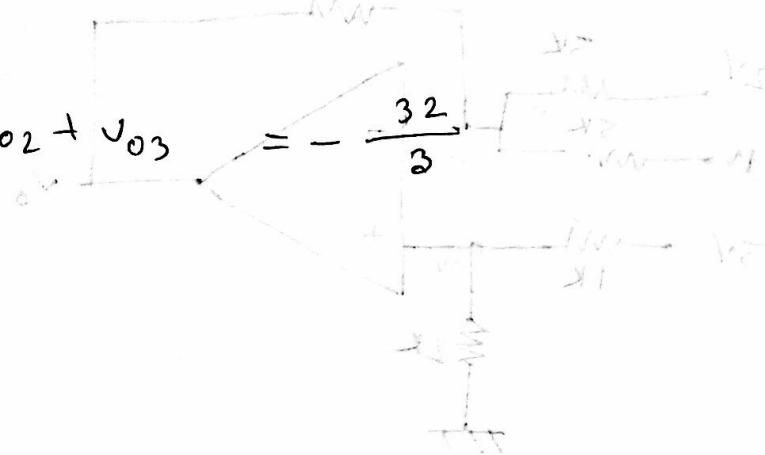
$$50, \quad V_o = V_{o_1} + V_{o_2} + V_{o_3} = -\frac{32}{3}$$



with  $V_L$  added

$$\text{Hovp} = (1 + \frac{50}{3}) = 10V$$

without  $V_L$  added

$$\text{Hovp} = (1 + \frac{50}{2}) = 25V$$

with  $V_L$  added

$$25 - \frac{25}{21.67} = 8V$$


$$25 - \frac{25}{20} = 5V$$

$$-\frac{50}{8} =$$

$$25 - \frac{25}{20} = 12.5V$$

7/08/16

## Problem 2°

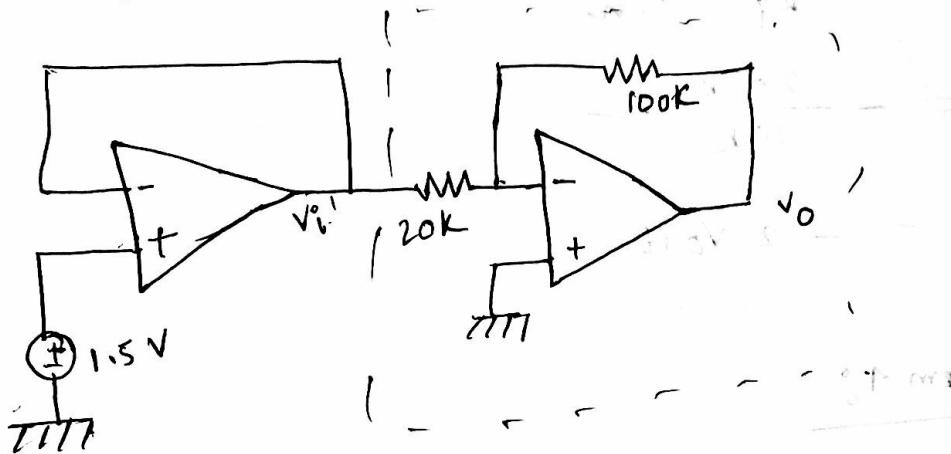


$$V_o' = 1.5 \text{ V}$$

$$V_o = -\frac{R_f}{R_i} V_{in} = -\frac{100k}{20k} * 1.5 = -7.5 \text{ Volt (Ans)}$$



$V_{in} = 1.5 \text{ V}$

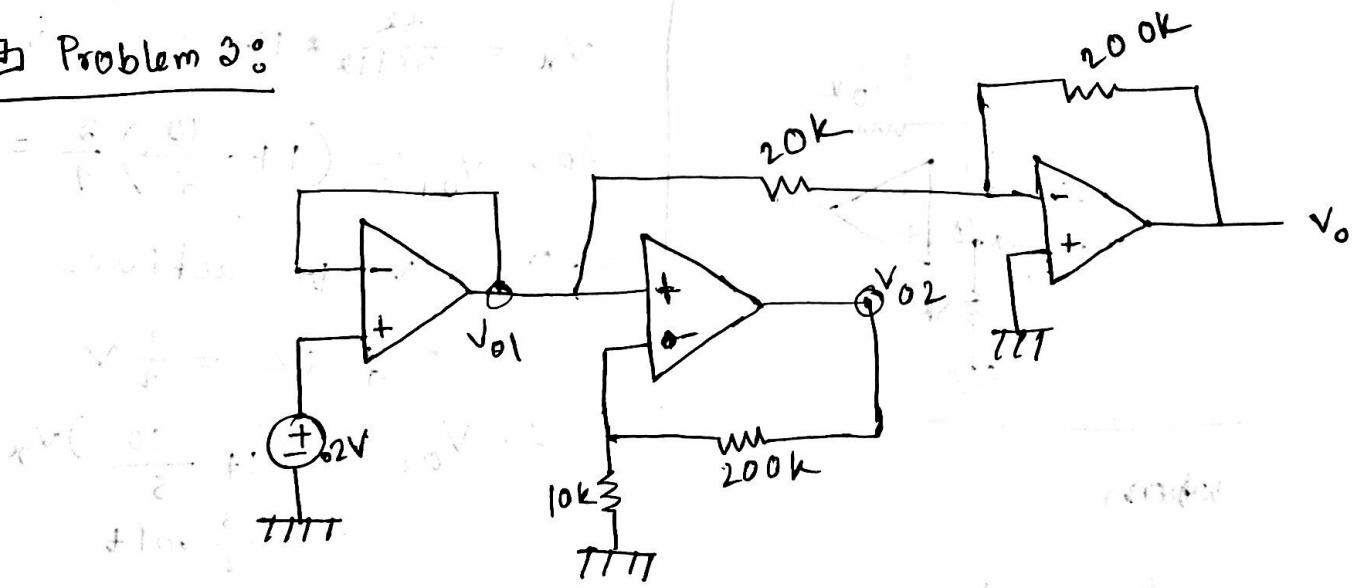Problem 3°

$$V_{o1} = 0.02 \times 0.2 \text{ V}$$


$$V_{o2} = \left(1 + \frac{R_f}{R_i}\right) V_{in} = \left(1 + \frac{200k}{10k}\right) .2 =$$

$$V_o = -\frac{R_f}{R_i} V_{in}$$


$$= -\frac{200k}{20k} \cdot 2$$

$$= -2 \text{ Volt}$$

Problem 1:

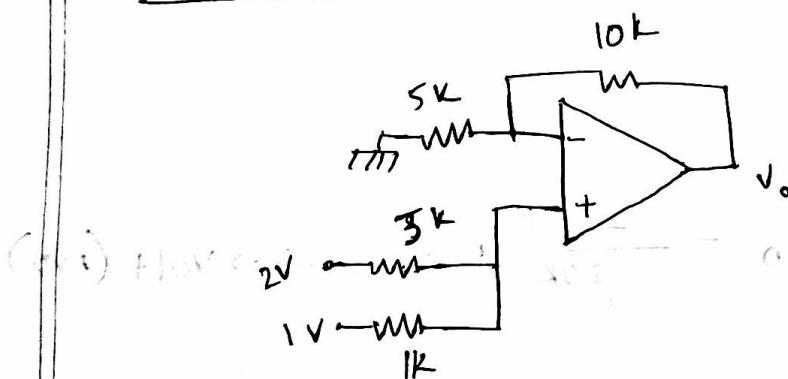

When 1V is active

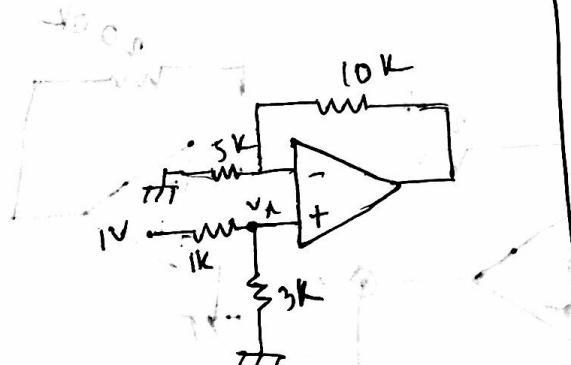

Here,

$$V_x = \frac{3k}{3k+1k} \cdot 1V = \frac{3}{4} \text{ Volt}$$

$$\therefore V_{o1} = \left(1 + \frac{10}{5}\right) \frac{3}{4} = \frac{9}{4} \text{ Volt}$$

When 2V is active

$$V_x = \frac{1}{2} \times 2 = \frac{1}{2} \text{ Volt}$$

$$\therefore V_{o2} = \left(1 + \frac{10}{5}\right) V_x \\ = \frac{3}{2} \text{ Volt}$$


where,

So, when 1V and 2V source are active

$$V_o = V_{o1} + V_{o2} = \frac{9}{4} + \frac{3}{2} = \frac{15}{4} \text{ Volt (Ans)}$$

### Q1 Design

$$V_o = -3V_1 - 4V_2$$

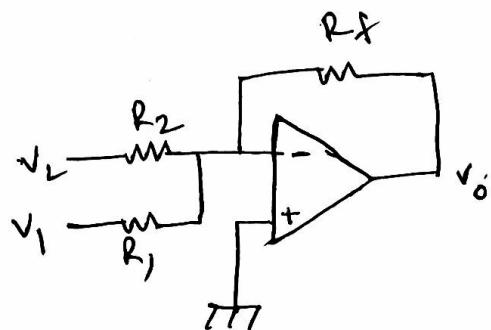

when  $V_1$  is active

$$V_{o1} = -\frac{R_f}{R_1} V_1$$

$$\Rightarrow -3V_1 = -\frac{R_f}{R_1} V_1$$

$$\Rightarrow 3 = \frac{R_f}{R_1}$$

$$\Rightarrow R_1 = \frac{R_f}{3}$$

$V_2$  is active

$$V_{o2} = -\frac{R_f}{R_2} V_2$$

:

:

$$\Rightarrow R_2 = \frac{R_f}{1}$$

Let,  $R_f = 100k$

$$R_1 = \boxed{\phantom{000}}$$

$$R_2 = \boxed{\phantom{000}}$$

### Q2:

$$V_o = -3V_1 + 4V_2$$

