

Date: 24/02/17

Ahsanullah University of Science and Technology

Department of Computer Science and Engineering

Third Year, First Semester

Final Examination, Spring 2017

Course No: CSE 3109

Course Title: Digital System Design

Full Marks: 70

Time: 3 Hours

[There are 7(Seven) questions. Answer any 5(Five) questions.]
[Marks allotted are indicated in the right margin within '[]'.]

1.a) Derive simplified function for D and B₀ of Figure 1. [4]

 


Figure 1: Circuit for 1.a)

b) The following register-transfer operations specify a four-state control of the sequence register and decoder type. G is a 2-bit sequence register and T₀, T₁, T₂ and T₃ are the outputs of the decoder. [5]

xT₀: G ← G+1

yT₀: G ← 10

zT₀: G ← 11

T₁+T₂+T₃: G ← G+1

Draw the state diagram of the control and design the sequence register with JK flip-flops.

c) Design a combinational circuit using a PLA. The circuit accepts a 2-bit number and generates an output binary number equal to the cube of the input number. Derive the PLA program table for this circuit. [5]

2.a) What is mnemonics? Explain with example. [2]

b) How do Program Counter and Ring Counter differ from each other? Explain with example. [2]

c) Translate the following program into SAP-1 machine language. [4]

PC	A	Address	Instruction	
		0H	LDA 9H	00
		1H	ADD AH	01
MAR Input	ALU	2H	ADD BH	01
		3H	SUB CH	01
RAM	B	4H	OUT	0F
		5H	HLT	0F
IR	D	9H	01H	0F
		AH	02H	
CU	D	BH	03H	
		CH	04H	

d) Describe the SAP-1 architecture. [6]

3.

 


Figure 2: control state diagram for problem 3

The state diagram of a control unit is shown in Figure 2. It has four states and two inputs I and R. You must represent the 00 state as T_0 , 01 state as T_1 , 10 state as T_2 and 11 state as T_3 .

- Design the control using four D flip-flops. [4]
- Design the control using two J-K flip-flops and a 2×4 decoder. [5]
- Design the control using a PLA. [5]
- Describe bidirectional register of SAP-2 architecture. [2]
- Explain handshaking of SAP-2 architecture with example. [3]
- How much time delay does this SAP-2 subroutine produce? [4]

MVI A,0AH ¹⁰
 LOOP1: MVI B,64H ¹⁰⁰
 LOOP2: MVI C,47H ⁷¹
 LOOP3: DCR C
 JNZ LOOP3
 DCR B
 JNZ LOOP2
 DCR A
 JNZ LOOP1
 RET

CMA
 NOP
 NOP

8 8 1
 0 1 0
 1 1 0

T states required for MVI, DCR, JNZ and RET is 7, 4, 10/7 and 10 respectively.

- The traffic lights on a main road show green for 90 s, yellow for 10 s, and red for 40 s. Bits 1, 2 and 3 of port 4 of SAP-2 are the control inputs to peripheral equipment that runs these traffic lights. Write a program in mnemonics for SAP-2 that produces time delays of 90, 10 and 40 s for the traffic lights. [5]
- Describe the write and read operations of a RAM. [2]
- What is Shift Register? What are the differences between SRAM and DRAM? [3]
- Design an arithmetic circuit with one selection variable s and two data inputs A and B. When $s = 0$, the circuit performs the addition operation $F = A + B$. When $s = 1$, the circuit performs the decrement operation $F = A - 1$. [3]

0101
 1111
 101001

Page 2 of 3

$A + \bar{B}$
 $A + \bar{B} + 1$

0001
 1110
 1 1 1 1
 1×10^{-6}

- d) Design an arithmetic logic unit with three selection variables S_2 , S_1 and S_0 , that generates the following arithmetic and logic operations. When $S_2=0$ the arithmetic operations are done and when $S_2=1$ the logical operations are done. [6]

S_1	S_0	$C_{in} = 0$	$C_{in} = 1$	$C_{in} = \times$ (don't care)
0	0	$F = A + 1$	$F = A$	$F = AB$ (AND)
0	1	$F = A - B$	$F = A - B - 1$	$F = A \oplus B$ (XOR)
1	0	$F = B - A$	$F = B - A - 1$	$F = A + B$ (OR)
1	1	$F = A + B + 1$	$F = A + B$	$F = A \uparrow B$ (NAND)

- 6.a) What is Modified Booth's algorithm? Explain with example. [3]
b) Design a 3-bit gray code counter as shown in the state diagram of Figure 3. Use J-K flip-flops. [5]


 


Figure 3: State Diagram for problem 6 (b)

 

- T_0 Initialization
 T_1 $B_3 \leftarrow \bar{B}_3$
 T_2 DO nothing
 T_3 $A+B$ $E \leftarrow \text{count}$
 T_4 $A+B+1$ $E \leftarrow \text{count}$
 T_5 $E \leftarrow 0$

- T_6 $A \leftarrow P$ If $m = 110110$, $r = 101101$, $x = 6$ and $y = 6$; using the Booth's multiplication algorithm determine the initial value of A , S and P . Show all the steps of Booth's algorithm to find the final value of P . [6]


- T_7 $A \leftarrow \bar{A}$ Design a hard-wired control to implement the addition and subtraction of two fixed-point binary numbers represented in sign magnitude form. Your design must include the following steps:

- Equipment Configuration [2]
- Derivation of the Algorithm [2]
- Flowchart [2]
- Control state diagram and Sequence of microoperations [4]
- Design of Hard-wired Control [4]

You must use an ALU that has the following function table:

S_2	S_1	S_0	C_{in}	Output
0	0	1	0	$F = A + B$
0	1	0	1	$F = A - B$
1	1	1	0	$F = A'$
0	0	0	1	$F = A + 1$

110110
001001
10

 

$x \ S_2 \ S_1 \ S_0 \ C_{in} \ L \ Y \ Z \ W$
101 101
110 10
001 0110