

date: 23/9/2017

AHSANULLAH UNIVERSITY OF SCIENCE AND TECHNOLOGY
DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING
1ST YEAR 2ND SEMESTER, FINAL EXAMINATION, SPRING-2017
COURSE NO: EEE-1241 COURSE TITLE: BASIC ELECTRICAL ENGINEERING


TIME: 3 HRS

FULL MARKS: 210

There are Eight (8) questions. Answer any Six (6)
Marks allotted for each question are indicated in the right margin
(All resistances are in ohms if not specified)

- 01. (a) State KVL and KCL. Find the value of current I and I_x for the following circuit.**

17

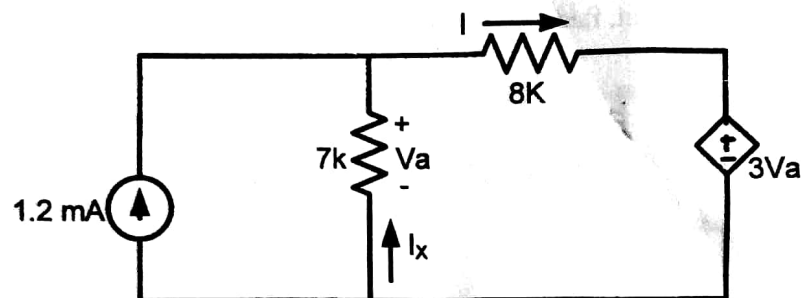


- (b) State Maximum power transfer theorem and prove that, $P_{max} = V_{th}^2 / 4 \cdot R_{th}$. Also Show that the efficiency for maximum power transfer is 50%.**

18


- 02. (a) Determine the equivalent resistance at terminals a-b for the following network**

17

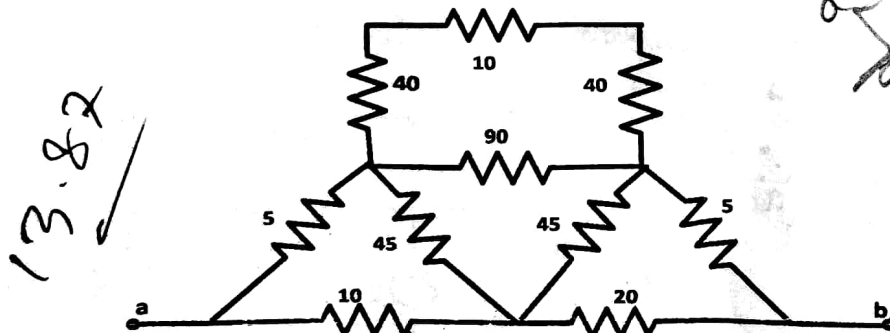

- (b) Determine the value of voltage V for the following circuit using node voltage analysis.**

18

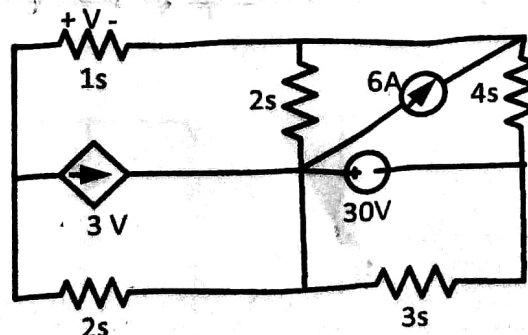


Handwritten notes for equivalent resistance:

$$R_1 = \frac{R_c R_b}{R_a + R_b + R_c}$$


$$R_A = R_2 + R_3 + \frac{249 \Omega}{1}$$

03.

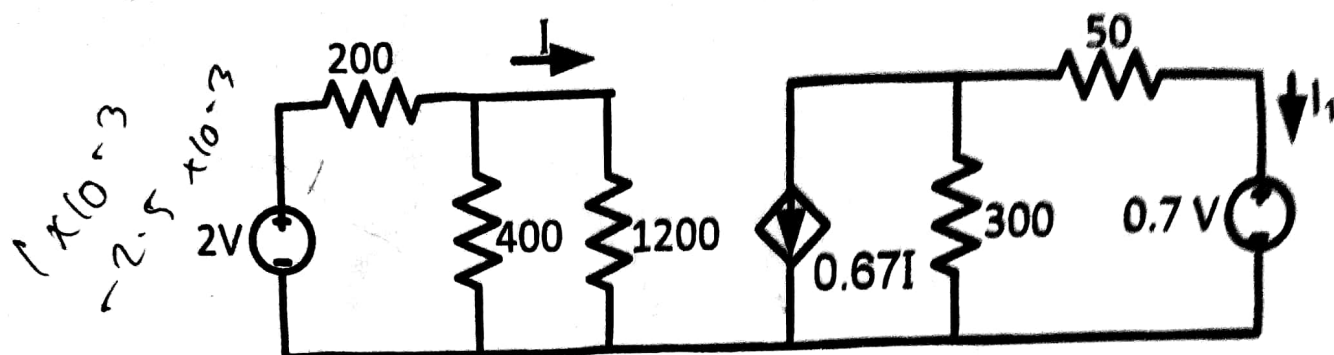- (a) Determine the value of current I and I_1 for the following circuit.




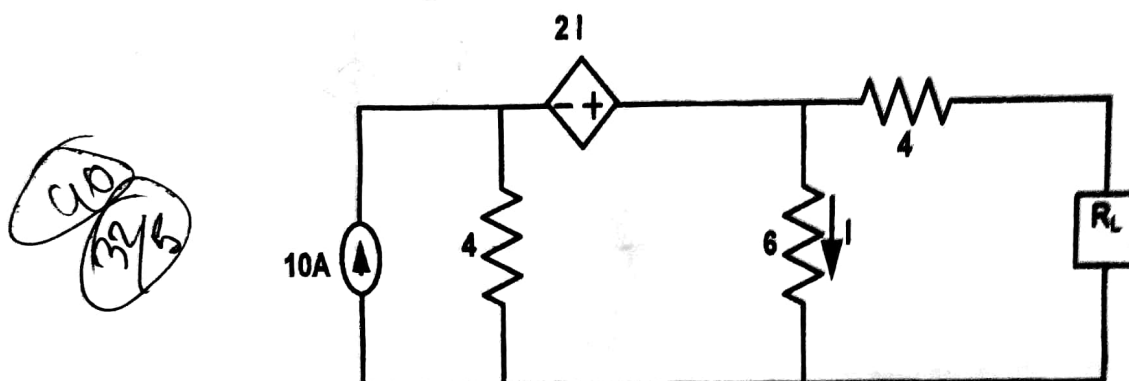- (b) For the following circuit, find the Thevenin's equivalent circuit with respect to the load resistance R_L .




04.

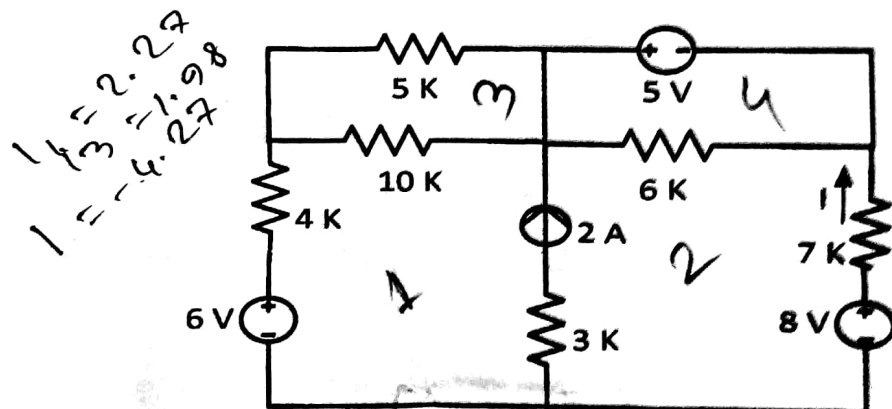- (a) Using mesh current analysis, find out the value of current I for the following circuit.




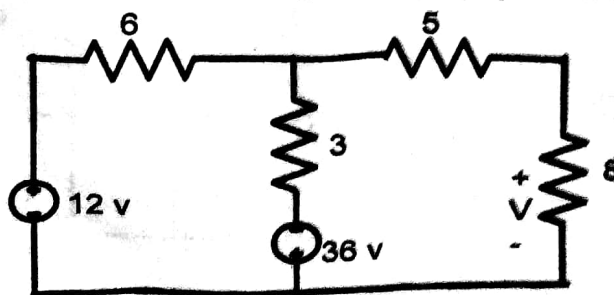- (b) For the following circuit, find the value of voltage V using superposition theorem.



05.

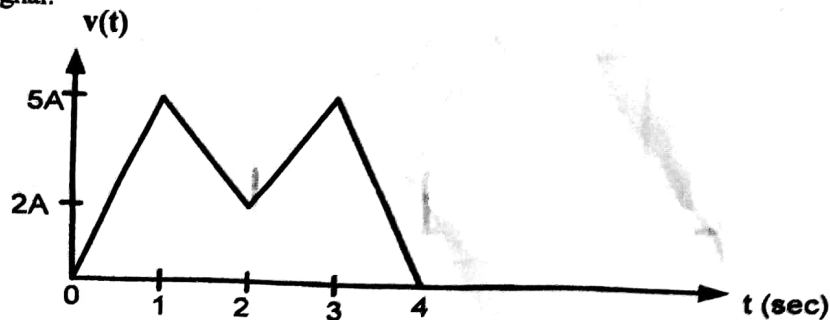
- (a) The voltage across the capacitor of 2mF is represented by the following signal. Draw the current signal. 18



- (b) The current equation and voltage equation of a circuit is represented by $i = -2 \cos(\omega t - 60^\circ)$ and $v = 3 \sin(\omega t - 150^\circ)$ respectively. Draw the voltage and current wave shapes and determine the phase relationship between voltage and current? A 4A dc current component is added to the sinusoidal AC current of peak value 5A . Sketch the resultant wave shape. Also, write down the analytical expression for the resultant current wave shape if the frequency is 60Hz . 17

06.

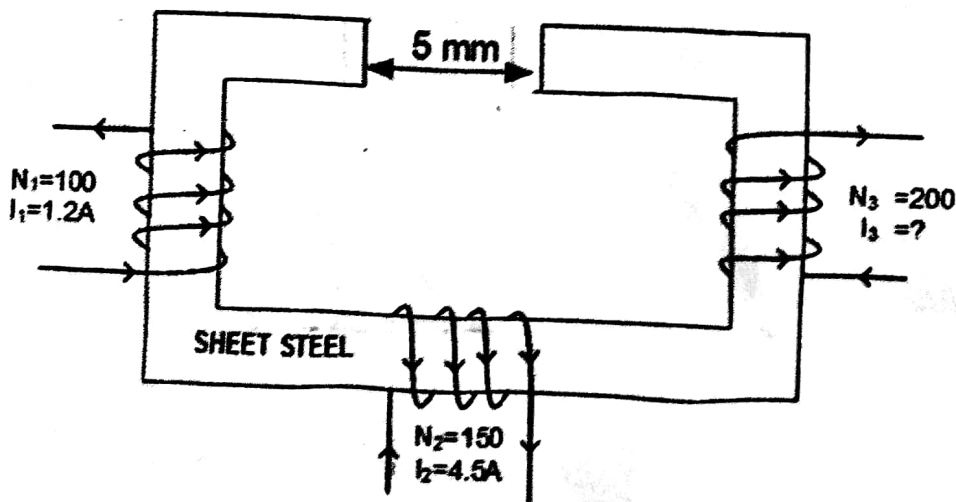
- (a) What do you mean by hysteresis loop for a ferromagnetic material. What is the physical significance of the area inside the hysteresis loop. 15
- (b) Find the current I required to establish the flux, 0.4 mwb in the following magnetic circuit. A set of B-H curve is attached at the end of the question. Mark the appropriate points on the B-H curve and attach the page with your answer script. 20
- Area, $A = 3 \text{ cm}^2$ (throughout)
 $l_{\text{cast steel}} = 100\text{cm}$



07.

- (a) The current passing through R-L-C series circuit is $i = I_m \sin \omega t$. Find out the expression of voltage, power and impedance for the circuit. 17

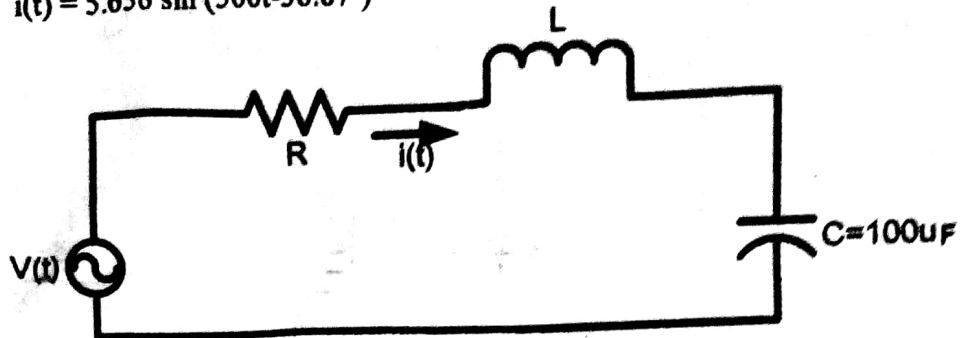- (b) For the following circuit find the value of R and L. If-
 $v(t) = 282.8 \sin 500t$
 $i(t) = 5.656 \sin (500t - 36.87^\circ)$




08.

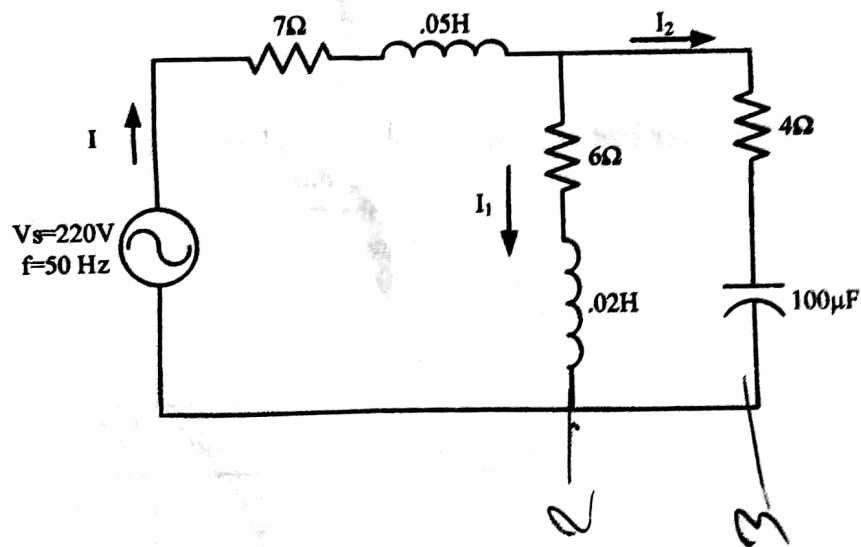- (a) An alternating voltage $v(t) = V_m \sin \omega t$ is applied to the capacitive circuit. Prove that energy received by the capacitor during a quarter cycle is $W_C = \frac{1}{2} C V_m^2$.

(b)

For the following network calculate the currents I, I_1 and I_2 . Also find the power factor of the network.



$i = C \frac{dv}{dt}$
 $V = 1$

Signature of the Invigilator

