

AHSANULLAH UNIVERSITY OF SCIENCE AND TECHNOLOGY
DEPARTMENT OF COMPUTER SCIENCE & ENGINEERING
2ND YEAR 1ST SEMESTER, FINAL EXAMINATION, SPRING-2017
COURSE NO.: EEE-2141 COURSE TITLE: ELECTRONIC DEVICES & CIRCUITS

TIME: 3 HRS

Use separate script for each part.

FULL MARKS: 210

SECTION-A

There are four (4) questions in this section. Answer any three (3)
Marks allotted for each question are indicated in the right margin

4x2=8
0, 1, 2, 3, 4, 5

01

- (a) What is an extrinsic semiconductor? Explain why a pentavalent impurity atom is known as donor-typed impurity. [17]
- (b) Design a clamper circuit to perform the following operation of Fig. 1(b) with necessary equation. [18]

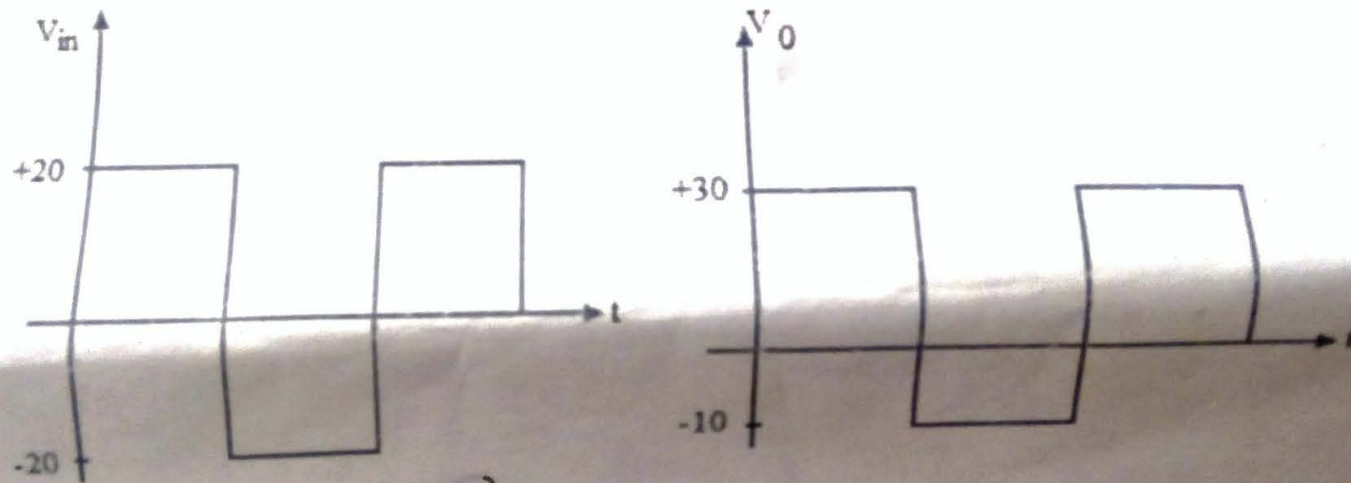


Fig.:1 (b)

02

- (a) Using the small signal diode model show that, $i_d = \frac{I_D}{nV_T} v_d$, $r_d = \frac{nV_T}{I_D}$ where the symbols have their usual meaning. [17]

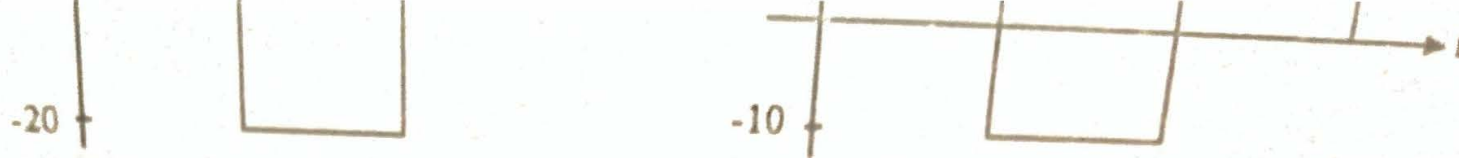


Fig.:1 (b)

- (a) Using the small signal diode model show that, $i_d = \frac{I_D}{nV_T} v_d$, $r_d = \frac{nV_T}{I_D}$ where the [17]
symbols have their usual meaning.

- (b) Find I_D and V_0 of the circuit shown in Fig.:2 (b). [18]

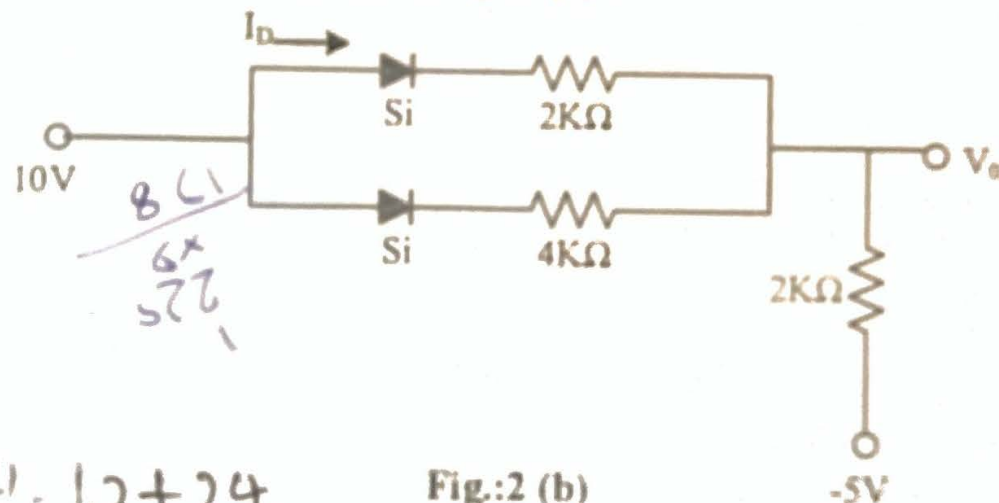


Fig.:2 (b)

- (a) Draw the circuit diagram of a full wave rectifier with input and output wave shapes [17] with bridge connection and explain its working principle. Also derive the expression of rectification efficiency in this case.

- (b) Draw the output wave shapes, V_o of the circuit shown in Fig.: 3 (b) with [18] necessary equations.

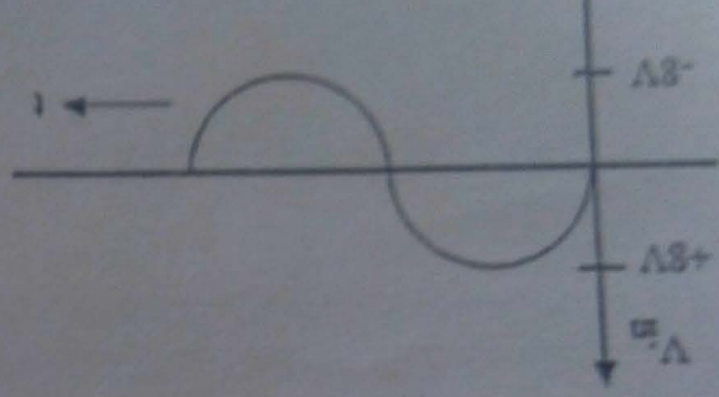


Fig.: 3 (b)

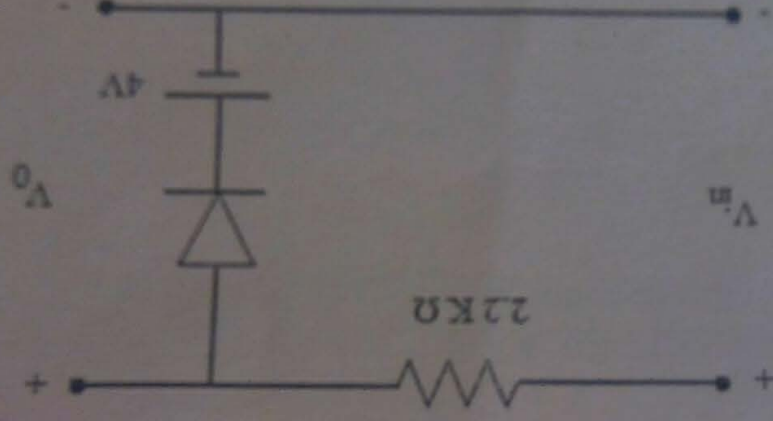




Fig.: 3 (b)

- (a) From the circuit shown in Fig.: 4 (a), determine the range of R_L and I_L that will result V_{RL} being maintained at 10V. [17]

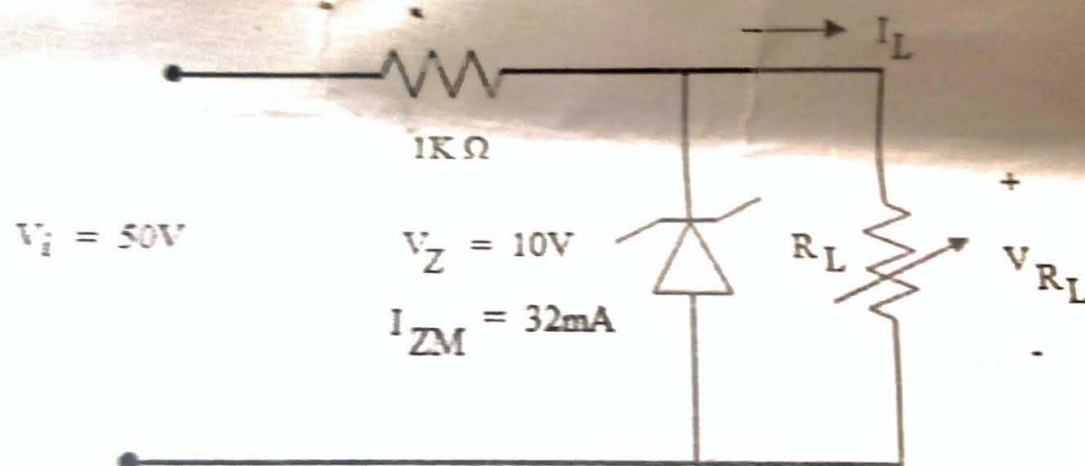


Fig.: 4 (a)

- (b) Draw a NPN transistor in the CB configuration biased for operation in the active region. Also sketch typical CB input and output characteristic curve for an NPN transistor. Label all the variables. [18]

SECTION-B

There are four (4) questions in this section. Answer any three (3)
Marks allotted for each question are indicated in the right margin

05

- (a) What is the difference between depletion type and enhancement type MOSFET. [17]
Describe the construction and operating principle of a N-channel depletion type MOSFET with input and output characteristics curves.
- (b) Draw the output voltage waveform of the following comparator circuit of Fig. 5(b). [18]

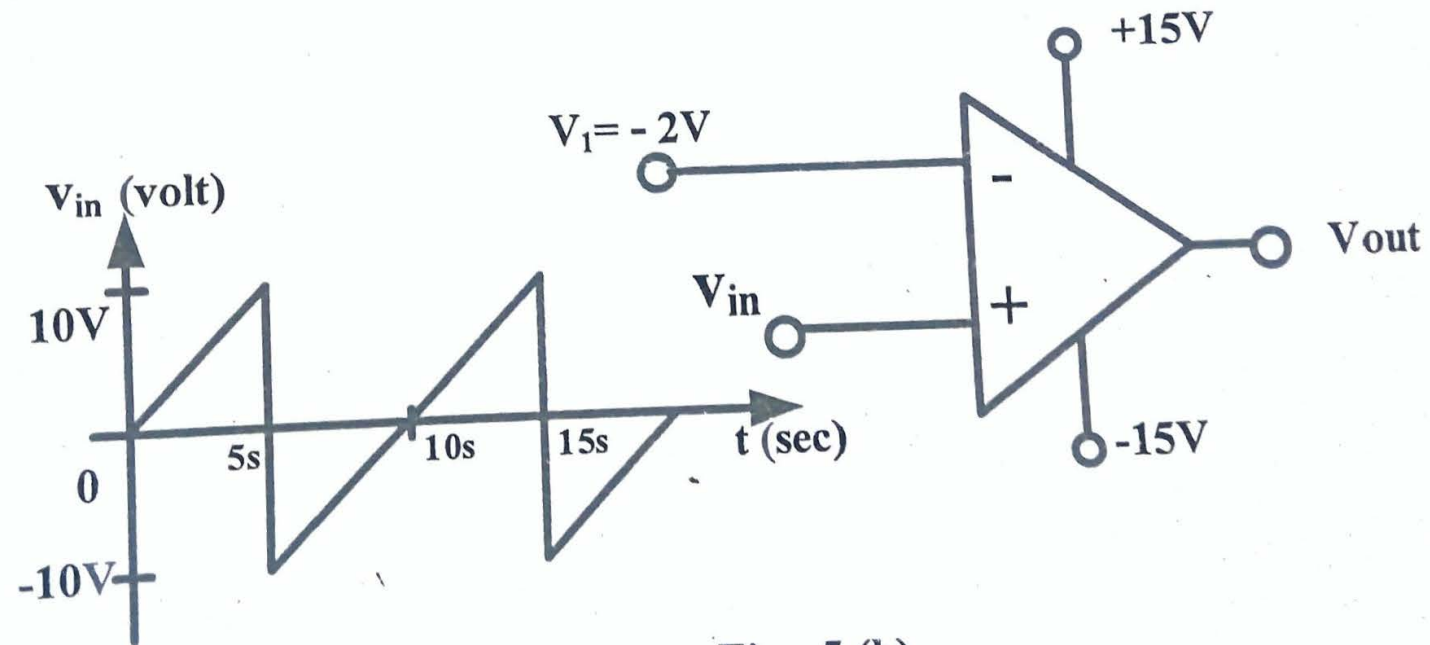


Fig.: 5 (b)

06

- (a) Show that, $I_C = \beta I_B + I_{CEO}$, where the symbols have their usual meaning.

For the circuit shown in Fig. 6 (b), find output voltages, V_1 and V_2 .

(a) Show that, $I_C = \beta I_B + I_{CEO}$, where the symbols have their usual meaning. [17]

(b) For the circuit shown in Fig. 6 (b), find output voltages, V_1 and V_2 . [18]


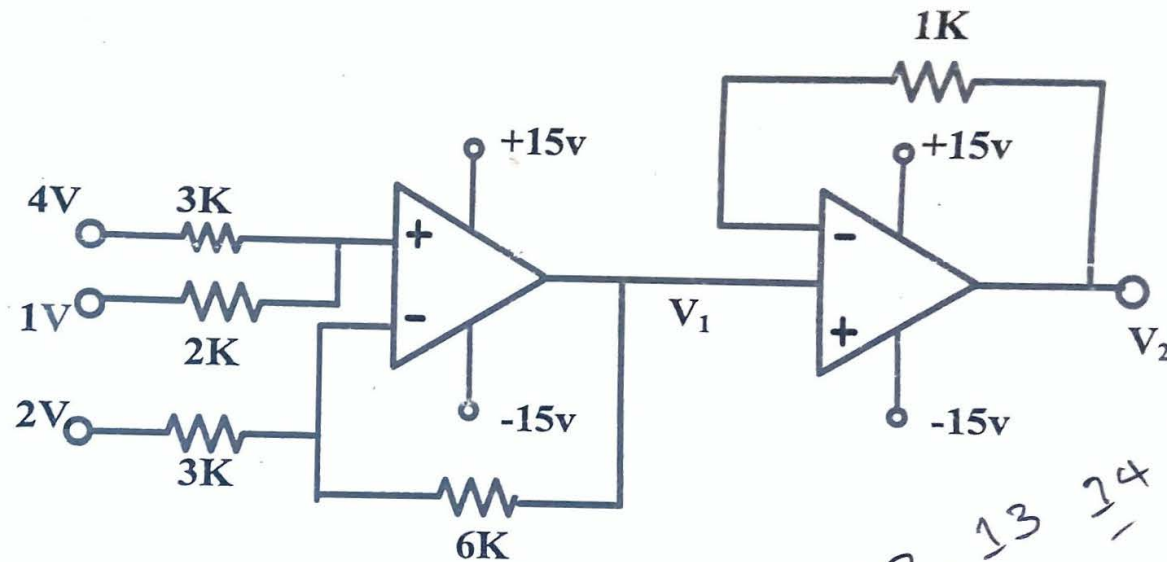


Fig.: 6 (b)

(a) Positive to 1 amplifying action with output figure

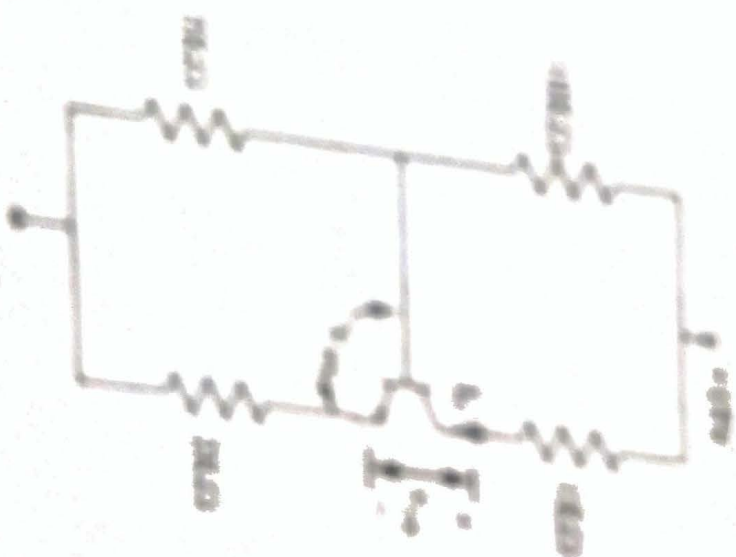(b) A voltage divider like circuit is shown in the fig 7.8. Determine the operating point. Assume $\beta = 100$




1.93

07

(a) Explain BJT amplifying action with relevant figures. [17]

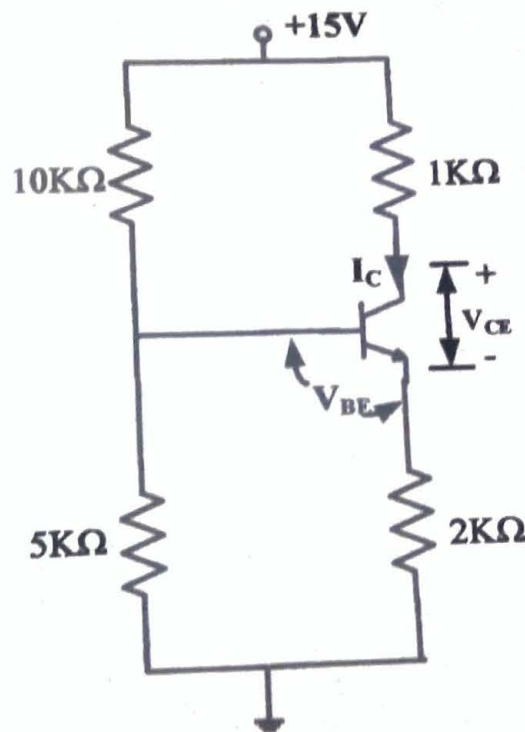(b) A voltage divider bias circuit is shown in the Fig.7 (b). Determine the operating point. [18]
Assume $V_{BE} = 0.7V$,



$$\beta = 78$$

Fig.: 7(b)

08

[17]

(a) Write short notes on:

- i. Controlled full wave rectifier.
- ii. Pinch-off voltage of a MOSFET and
- iii. Ion implantation of IC fabrication.

(b) The emitter-bias configuration of Fig. 8 (b) has the following specifications:
 $I_{CQ} = \frac{1}{2} I_{Csat}$, $I_{Csat} = 8\text{mA}$, $V_C = 18\text{ V}$ and $\beta = 110$. Determine R_C , R_E , and R_B .

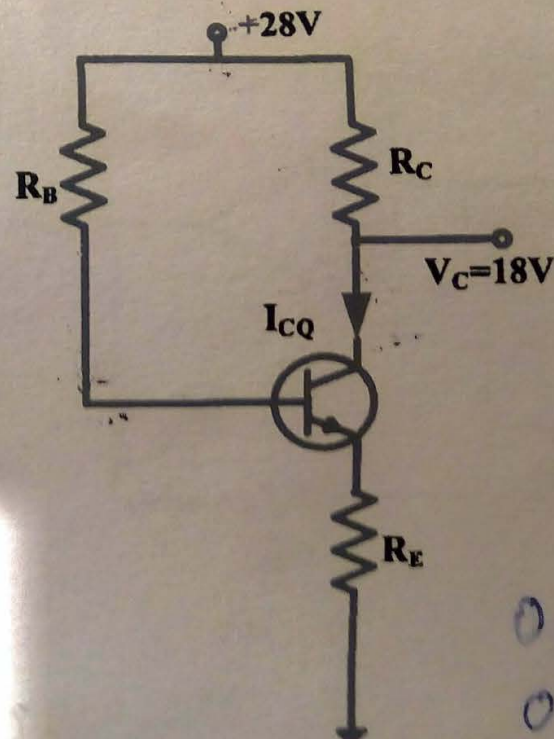


Fig.: 8 (b)

$$\begin{array}{r} .83 \\ 50 \\ \hline 46 \\ 20 \\ \hline 16 \end{array}$$

$$\begin{array}{r} 0.09 \\ 0.45 \\ \hline 0.54 \end{array}$$

$$\frac{0.09}{0.54} = \frac{1}{6}$$

$$\frac{0.54}{0.09} = 6$$

$$\frac{0.45}{0.54} = \frac{5}{6}$$

0 1 2345678 9 9265321