

mixed signal : 2018 25/04/'17

Digital: Analog — Analog signal: range of values: continuous
Digital — Discrete / fixed value

Digital logic: Logic required to design digital ckt.

ON HIGH \rightarrow (2 - 5 V) (5 V as symbol)
OFF LOW \rightarrow (0 - 0.8 V) (0 V as symbol)

HIGH (5V) = Logic 1

LOW (0V) = Logic 0

All ckt's will have input and output as 1 or 0.

DLO \rightarrow All values in binary.

Chapter-1

Number Systems

- Binary, Octal, Decimal, Hexadecimal
- Conversion
- binary addition, subtraction, multiplication
- 1's complement
- 2's complement
 - [Until first bit of (1) is reached, keep the bits as it is. Then flip the rest bits. ($R \rightarrow L$)]

- I/O - bit
- 1011 - 4 bits
- IC - Integrated ckt - many ckts implemented together
- SSI - Small scale integration
- MSI - Medium "
- LSI - Large "
- VLSI - Very large "
- 0-15: learn the binary numbers

Advantage of digital ckt - Transmission, processing, error detecting and storing of digital signal is easier. (Noise = error)

i) Combinational ckt

DLD  ii) Sequential ckt

Combinational ckt - Output depends on input (current) Eg: multiplication

Sequential ckt - Output depends on both current and previous input. Eg: goals in football

Input A	Input B	Output Y
0	0	0
0	1	0
1	0	1
1	1	1

24/04/'17

Introduction to Basic Logic Operations and Basic Digital Circuits

- Logic ckt / digital ckt / switching ckt:

A ckt whose input and output signals are 2 state, either low or high voltages. The basic logic ckt are: OR, AND, NOT gates.

- Gate: a logic ckt with one or more input signals but only one output signal.

- Truth table: A table that shows all input and output possibilities for a logic ckt. For n inputs, there are 2^n input combinations

- i) AND operation:

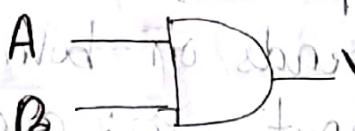


Fig: 2 input AND gate

Logic equation:

$$Y = AB$$

Truth table:

<u>Inputs</u>	<u>Output</u>	
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


ii) OR operation:



$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

iii) NOT operation:

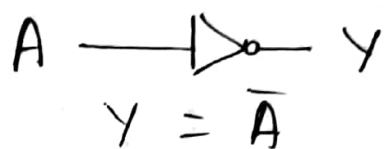


$$Y = \bar{A}$$

$$\text{or, } Y = -A'$$

A	Y
0	1
1	0


iv) NAND operation:

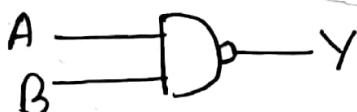

$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

v) NOR operation:

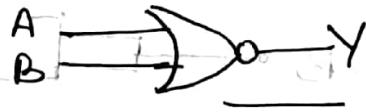

$$Y = \overline{A+B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


Being the only one type of gates either NAND or NOR are sufficient for the realisation of any logical expression, so they are known as universal gates

- Realisation of basic logic operations using NAND gates:


a) NOT:



b) AND:

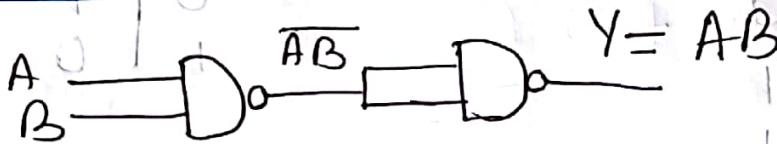


c) OR:

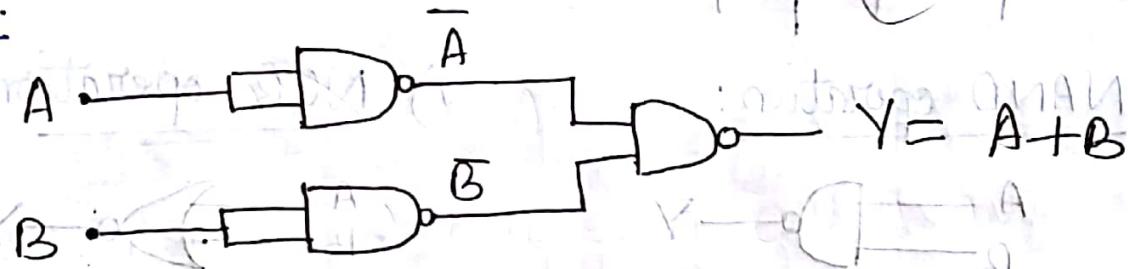


- H/W: Realisation of basic logic operations using NOR gates.


a) NOT:

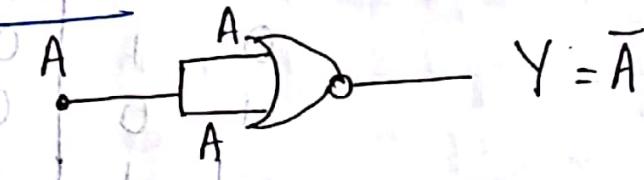


b) OR:

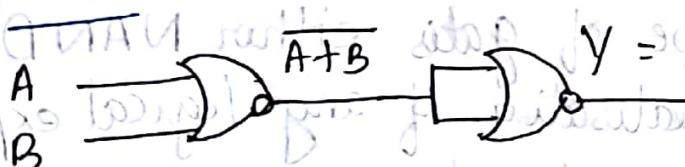

c) AND:

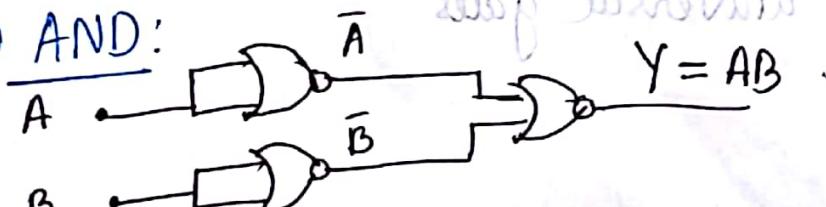

vi) Exclusive OR (Ex-OR/X-OR) operation:

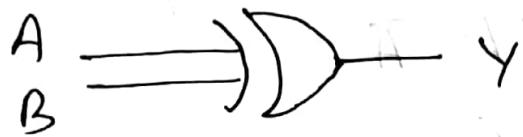

$$Y = A \oplus B = \overline{A}B + \overline{B}A$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

vii) Exclusive NOR (Ex-NOR/X-NOR) operation:




$$\begin{aligned} Y &= \overline{A \oplus B} = \overline{A' \cdot B + A \cdot B'} \\ &= \overline{A' \cdot B} \cdot \overline{A \cdot B'} = A \cdot \overline{B} + \overline{A} \cdot B \end{aligned}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$\left[\begin{array}{l} \text{No. of } 1 \text{ in input if odd, output} = 1 \\ \text{No. of } 1 \text{ in input if even, output} = 0 \end{array} \right]$

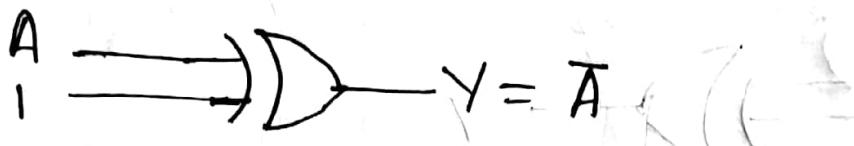- Realisation of NOT gate using XOR gate:



$$\begin{aligned}
 A \oplus B &= A\bar{B} + \bar{A}B \\
 &= A \cdot 1 + \bar{A} \cdot 1 \\
 &= A \cdot 0 + \bar{A} \\
 &= \bar{A}
 \end{aligned}$$

- Realisation of NOT gate using X-NOR gate:



$$\begin{aligned}
 A \oplus B &= A'B + AB = \bar{A} \cdot 0 + A \cdot 0 \\
 &= \bar{A} \cdot 1 + 0 = \bar{A}
 \end{aligned}$$

$$\begin{aligned}
 A \oplus A' &= \bar{A} \oplus A = 1 \\
 AA + A'A &=
 \end{aligned}$$

A	B	$A \oplus B$	\bar{A}
0	0	0	1
0	1	1	1
1	0	1	0
1	1	0	0

For 2 inputs, there are 4 rows.

For n inputs, there are 2^n rows.

30/04/11

Boolean Algebra & Logic Simplification:

1854 - George Boole

Definitions: variable, boolean, complement, literal

Laws of Boolean Algebra:

$$\textcircled{1} \text{a) } A + B = B + A \quad [\text{Commutative laws}]$$

$$\text{b) } AB = BA \quad [\text{Commutative laws}]$$

$$\textcircled{2} \text{a) } A + (B + C) = (A + B) + C \quad [\text{Associative laws}]$$

$$\text{b) } A(BC) = (AB)C \quad [\text{Associative laws}]$$

$$\textcircled{3} \text{a) } A(B+C) = AB + AC \quad [\text{Distributive laws}]$$

$$\text{b) } A+BC = (A+B)(A+C) \quad [\text{Distributive laws}]$$

De Morgan's Theorems:

$$\text{i) } \overline{AB} = \overline{A} + \overline{B} \quad \text{ii) } \overline{A+B} = \overline{A} \cdot \overline{B}$$

[See the proofs from book]

* Rules of Boolean Algebra

$$1) A + 0 = A$$

$$2) A + 1 = 1 + A = 1$$

$$3) A \cdot 0 = 0$$

$$4) A \cdot 1 = A$$

$$5) A + A = A$$

$$6) A + \overline{A} = 1$$

$$7) A \cdot A = A$$

$$8) A \cdot \overline{A} = 0$$

$$9) (\overline{A}) = A$$

$$10) A + AB = A$$

$$11) A + \bar{A}B = A + B$$

$$12) (A+B)(\bar{A}+C) = A + BC$$

[See details from book]

* Duality Principle:

It states that every algebraic expression deducible from the postulates of Boolean Algebra remains valid if the operators and the identity elements are interchanged.

$$\text{Eg: if } A + \bar{A} = 1,$$

$$\text{then } A \cdot \bar{A} = 0$$

$$\text{if } A + 1 = 1, \text{ then } A \cdot 0 = 0$$

AND \leftrightarrow OR

0 \leftrightarrow 1

Prove:

Proof that:

$$A + \bar{A}C = A + C$$

$$\text{L.H.S} = A + \bar{A}C$$

$$= (A + \bar{A})(A + C) \quad [\text{Distributive law}]$$

$$= 1 \cdot (A + C) \quad [A + \bar{A} = 1]$$

$$= A + C$$

$$= \text{R.H.S.}$$

Alternate form:

A	C	$\bar{A}C$	$A + \bar{A}C$	$A + C$
0	0	0	0	0
0	1	0	0	0
1	0	1	1	1
1	1	1	1	1

* Simplification using Boolean Algebra:

i) $AB + A(B+C) + B(B+C)$

Solution:

$$= AB + AB + AC + BB + BC \quad (\text{Distributive law})$$

$$= AB + AC + B + BC \quad [\because BB = B, \\ AB + AB = AB]$$

$$= AB + AC + B \quad [\because B + BC = B]$$

$$= B + AC \quad [\because AB + B = B]$$

Ans: $B + AC$

ii) $[A\bar{B}(C+BD) + \bar{A}\bar{B}]C$

Solution:

$$= (\bar{A}\bar{B}C + \bar{A}\bar{B}BD + \bar{A}\bar{B})C \quad (\text{Distributive law})$$

$$= (\bar{A}\bar{B}C + A \cdot 0 \cdot D + \bar{A}\bar{B})C \quad [\because B\bar{B} = 0]$$

$$= (\bar{A}\bar{B}C + \bar{A}\bar{B})C$$

$$= \bar{A}\bar{B}CC + \bar{A}\bar{B}C \quad [(\text{Distributive law})]$$

$$= \bar{A}\bar{B}C + \bar{A}\bar{B}C \quad [\because CC = C]$$


$$= \bar{B}C(A + \bar{A})$$

$$= \bar{B}C \cdot 1 \quad [\because A + \bar{A} = 1]$$

Ans: $\bar{B}C$

• Boolean Functions:

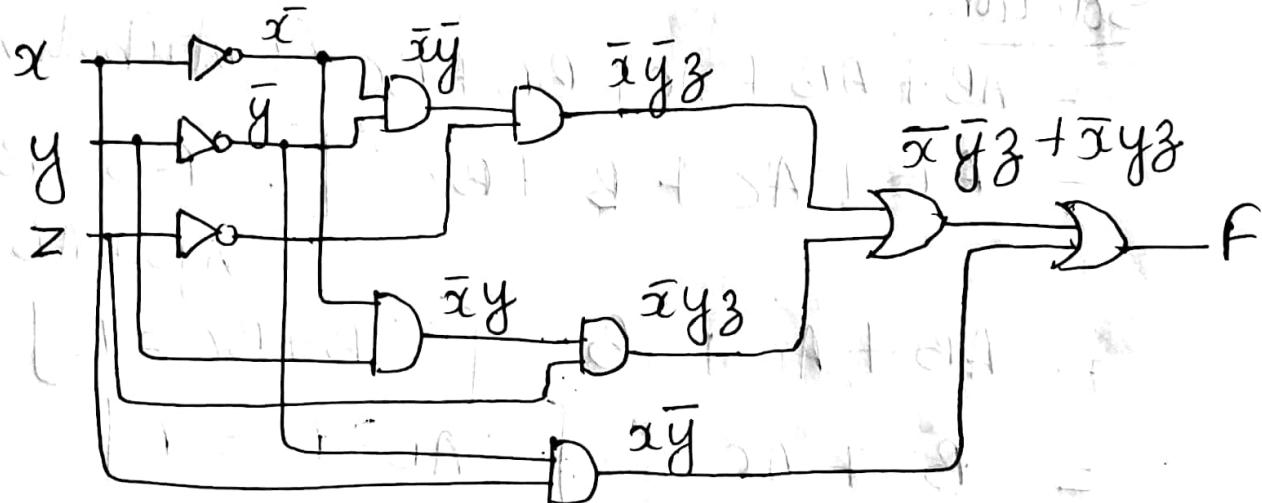Implement $F = \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}z$



Truth table:

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Since OR,
thus checking only
one term is
sufficient

Variable : symbol holding logic value (0 or 1)

Boolean : true or false holding 16 variables

Complement : inverted or / not form

Literal : variable that may be itself or its complement

for example 10010101010101010101010101010101

representable in standard binary form

and in standard binary form

10010101010101010101010101010101

10010101010101010101010101010101

representable in standard binary form

01/05/17

- Binary codes for the decimal digits

- i) BCD (Binary coded decimal) or 8-4-2-1 code

- In this code, decimal digits 0 through 9 are represented by their natural binary equivalents using 4 bits and each decimal digit of a decimal number is represented by this 4 bit code individually. For example:

<u>Decimal</u>	<u>Binary</u>	<u>BCD</u>
0	0000	0 000
5	0101	0 101
9	1001	1 001
25	11001	00100101

- ii) Excess-3 Code

The code for each decimal digit is obtained by adding decimal 3 to the natural BCD code of the digit.

Example: Decimal

Excess-3 code

7

10 10

6

10 01

iii) $2,4,2,1$ Code:

Decimal

$2-4-2-1$ code

7

0111

7

1101

9

1111

3

1001

3

0011

iv) $8,4,-2,-1$ code:

Decimal

$8,4,-2,-1$ code

1

0111

6

1010

• Coding Conversion

Decimal

$2,4,2,1$

$8,4,-2,-1$

code

code

0

0000

0000

1

0001

0111

2

0010

0110

3

0011

0101

v) The Reflected Code or Gray Code

a) Binary to Gray Conversion.

Binary: $\begin{array}{cccccc} & 1 & 0 & 1 & 1 & 0 \\ \downarrow & + & \downarrow & + & \downarrow & + \\ 1 & 1 & 1 & 0 & 1 & 1 \end{array}$

Gray: $\begin{array}{cccccc} & 1 & 1 & 0 & 1 & 1 \\ \downarrow & | & | & | & | & | \\ 1 & 1 & 1 & 0 & 1 & 1 \end{array}$

$$\begin{aligned} 0+0 &= 0 \\ 0+1 &= 1 \\ 1+0 &= 1 \\ 1+1 &= 0 \end{aligned}$$

$$0+0 = 0$$

$$\begin{array}{c} 0 \\ 0 \\ 0 \end{array}$$

b) Gray to binary conversion:

Gray: $\begin{array}{cccccc} & 1 & 1 & 0 & 1 & 1 \\ \downarrow & * & \downarrow & * & \downarrow & * \\ 1 & 0 & 0 & 1 & 1 & 0 \end{array}$

Binary: $\begin{array}{cccccc} & 1 & 1 & 0 & 1 & 1 \\ \downarrow & | & | & | & | & | \\ 1 & 0 & 0 & 1 & 1 & 0 \end{array}$

• Error-detection codes:

Parity bit: A parity bit is an extra bit included with a message to make the total number of 1's either odd (odd parity) or even (even parity).

Say,

message:

10110

odd parity

$\begin{array}{r} 10110 \\ + 0 \\ \hline 10110 \end{array}$

even parity

1

Tues
Quiz Chap 1 & 2

7/05/17

• Hamming Code:

Hamming c

Hamming code is a simple error detection - correction technique. It can be used to detect & correct one bit ~~error~~ change in an encoded code word.

Example: Determine the single error correcting code for 1011101110 .

Solution:

Total no. of bits in the original message, $n = 9$

Say, we require p parity bits. We know,

$$2^p \geq n + p + 1 \rightarrow 2^4 \geq 9 + 4 + 1 \rightarrow 16 \geq 14$$

min. bits: $p = 4$

So, we will send

$$n+p = 13 \text{ bits}$$

0 1 1 0 1 1 1 0 0 bit position

1	2	3	4	5	6	7	8	9	10	11	12	13
P_1	P_2	P_3	P_4	P_1	P_2	P_3	P_4	P_1	P_2	P_3	P_4	P_1
P_1	P_2	P_3	P_4	P_1	P_2	P_3	P_4	P_1	P_2	P_3	P_4	P_1
0 0 1 1 (3)	0 1 1 0 (6)	0 1 1 1 (7)	1 0 0 1 (9)	1 0 1 1 (11)	1 1 0 0 (12)	1 1 0 0 (12)	1 1 0 0 (12)	1 1 0 0 (12)	1 1 0 0 (12)	1 1 0 0 (12)	1 1 0 0 (12)	1 1 0 0 (12)

$$P_1 = 1 \underline{+} 0 \underline{+} 0 \rightarrow P_1 = 1$$

$$P_2 = 1 \underline{+} 1 \underline{+} 1 \rightarrow P_2 = 1$$

$$P_3 = 0 \underline{+} 1 \underline{+} 1 \rightarrow P_3 = 0$$

↳ parity bits
are positioned
in powers of 2

So, the sending message (hamming coded message) will be:

0 0 1 1 0 1 1 1 0 1 1 0

Receiving End:

Case 1: If no error occurs during transmission, we will get: 00 11 0 1 1 1 0 1 1 0 to check: 0011(3)
0100(4)
0110(6)
0111(7)
1000(8)

So, there is no error.

Case 2: Say, 6th position bit is altered during transmission & we get:

0 0 1 1 0 0 1 1 1 0 1 1 0

to check:

0011(3)
0100(4)
0111(7)
1000(8)
1001(9)
1011(11)
(XOR) 1100(12)
0110(4)

as, we got $(0110)_2$, i.e. 6 after XOR operation, so there is an error in 6th position. So, the original sending message was: 0011011110110

8/05/17

Chapter - 2

Standard forms of Boolean Expressions:

- Standardization makes the evaluation, simplification and implementation of Boolean expressions much more systematic and easier. All Boolean expressions can be converted into either of 2 standard forms

1. The SUM OF PRODUCTS (SOP) FORM :

Eg: $AB + A'BC$, $ABC + CDE + B'CD'$ etc

2. THE PRODUCT OF SUM (POS) FORM:

$$(A'+B)(A+\bar{B}+C), \\ (A'+B'+C') (C+D'+E) (B'+C+D) \text{ etc}$$

• Canonical FORM:

Boolean functions expressed as a sum of minterms or products of maxterms are said to be in canonical form.

Eg:

$$\begin{array}{l} \text{Maxterms} \\ M_0, A+B+C \\ M_1, A+B+C' \\ M_2 = A'+B'+C' \end{array}$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1

Minterms

$$\begin{array}{l} m_0, A'B'C' \\ m_1, A'B'C \\ m_2, A'BC \end{array}$$

$$F = \Sigma(1, 4, 5, 6, 7)$$

or,

$$F = \overline{\Pi}(0, 2, 3)$$

- Determining standard expressions from a truth table:

Example 1: $F(A, B, C, \cancel{D}) = \Sigma(1, 4, 5, 6, 7)$

$$= A'B'C + AB'C' + AB'C + ABC' + ABC$$

$$= A'B'C + AB'(C' + C) + AB(C' + C)$$

$$= A'B'C + AB' + AB \quad [\because C' + C = 1]$$

$$= A'B'C + A(B' + B)$$

$$= A'B'C + A \quad [\because B + B' = 1]$$

$$= (A + A')(A + B'C) \quad [\text{Applying distributive law}]$$

$$= A + B'C \quad [\because A + A' = 1]$$

Ans: $= A + B'C$

Example 2: $F(A, B, C) = \overline{\Pi}(0, 2, 3)$

$$= (A + B + C)(A + \overline{B} + C)(A + \overline{B} + \overline{C})$$

$$= (AA + A\overline{B} + AC + AB + B\overline{B} + BC)(A + \overline{B} + \overline{C})$$

$$= (A + AB' + AC + AB + 0 + BC + B'C + C)(A + B' + C') \quad [\because B\overline{B} = 0, A + A = 0, NA = A]$$

$$\begin{aligned}
 &= (A+A+Ac+C+c)(A+\bar{B}+\bar{C}) \\
 &= (A+Ac+C)(A+\bar{B}+\bar{C}) \quad [\because A+A=A] \\
 &= (A+C)(A+B'+C') \quad [\because A+AC=A] \\
 &= AA + AB' + AC' + AC + B'C + CC' \\
 &= A + AB' + A + B'C \quad [\because C+\bar{C}=1, C\bar{C}=0] \\
 &= A + A + B'C \quad [\because A+AB'=A] \\
 &= A + B'C \quad [\because A+A=A]
 \end{aligned}$$

Ans. $A + B'C$

$\left[\Sigma \rightarrow \text{SOP}, \Pi \rightarrow \text{POS} \right]$
 $\left[m \rightarrow \text{minterm}, M \rightarrow \text{maxterm} \right]$

09/05/17

- Conversion between minterm & maxterm:
- SOP to POS conversion:

Example 1: $F(A, B, C) = A'B'C' + A'BC + ABC' + ABC$

$$= \Sigma(2, 3, 6, 7)$$

$$= \bar{\Pi}(0, 1, 4, 5)$$

$$= (A + B + C)(A + B + C')$$

$$(A' + B + C)(A' + B + C')$$

Ans: $(A + B + C)(A + B + C')(A' + B + C)(A' + B + C')$

Example 2: $F(A, B, C) = A + B'C$

$$= A(B'C' + B'C + BC' + BC) + B'C(A + A')$$

$$[\because X + X' = 1]$$

$$= ABC' + AB'C + ABC + ABC + AB'C +$$

$$A'B'C$$

$$= AB'C' + AB'C + AB'C + ABC + A'B'C$$

$$= \Sigma(4, 5, 6, 7, 1)$$

$$= \bar{\Pi}(0, 2, 3)$$

$$= (A + B + C)(A + B' + C)(A + B' + C') \text{ (Ans.)}$$

* Whichever var. will be missing, all of their combinations have to be AND with the existing var.

$$B'C' + BC' + B'C + BC$$

$$= B'(C' + C) + B(C + C')$$

$$= (B' + B)(C' + C)$$

$$= 1 \cdot 1 = 1$$

• Converting POS to SOP:

$$\begin{aligned}
 \text{Example: } F(A, B, C) &= (A+B'+C)(A'+B) \\
 &= AA' + AB + A'B' + BB' + A'C + BC \\
 &= AB + A'B' + A'C + BC \quad [\because xx' = 0] \\
 &= AB(C+C') + A'B'(C+C') + A'C(B+B') + \\
 &\quad (C+C')(A+A')BC(A+A') \quad [\because x+x'=1] \\
 &\Rightarrow ABC + ABC' + A'B'C + A'B'C' + A'BC + \\
 &\quad A'B'C' + ABC + A'BC \\
 &= ABC + ABC' + A'B'C + A'B'C' + A'BC \\
 &= AB(C+C') + A'B'(C+C') + A'BC \quad [\because x+\bar{x}=1] \\
 &\Rightarrow AB + A' \{(B'+BC)\} \\
 &= AB + A' \{(B'+B)(B'+C)\} \quad [\because x+yz \\
 &\quad = (x+y)(x+z)] \\
 &= AB + A'(B'+C) \quad [\because B'+B=1] \\
 &= AB + A'B' + A'C \quad (\text{Ans.})
 \end{aligned}$$

* If $F(x, y, z) = 1$ that means,

$$F \in \Sigma(0, 1, 2, 3, 4, 5, 6, 7)$$

$$= \pi(NIL)$$

~~Quiz upto here (16/05)'17)~~

* Whichever var. is missing, i.e. x , the $(x+x')$ is to be AND with existing var.

Example: older number of infinite & open - A
when a digit marker being added to already
written digits of digital fraction with the

Example of addition of two
number in binary. $1101 + 1010$

1	1	0	1
1	0	1	0

0	1	0	1	0
1	0	1	0	1

Example of subtraction of two

14/05/17

Chapter - 3

Karnaugh Map (K-Map):

A K-map is similar to a truth table because it presents all of the possible values of input variable and the resulting output for each value.

- Two variable K-Map:

No. of grids = 2^n , where n = no. of variables

m_0	m_1
m_2	m_3

- Three variable K-map:

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

- Four variable K-map:

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_2	m_8	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

Input	Output	
x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

• Simplify using K-map (SOP minimization):

$$i) F(x, y) = \sum(1, 2, 3)$$

$$ii) F(x, y, z) = \sum(2, 3, 4, 5)$$

$$iii) F(A, B, C, D) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$

- Groups can be made horizontally or vertically.

- Groups can be of 2 or 4 (for two variable).

- Groups can be of 2 or 4 (for two variable).


- Always form biggest group possible.

- Always try to put all 1s in a group.

- Denote each group with a different symbol.

- Express Find expression of each group and OR them

Solution:

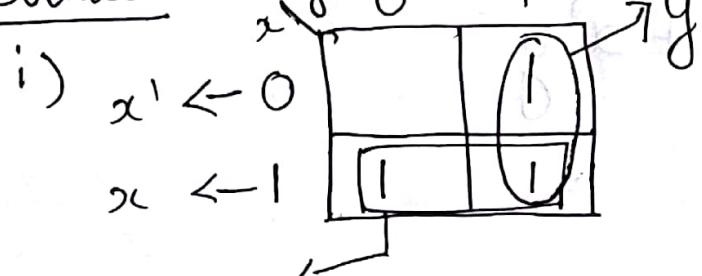

$$\text{Ans: } x + y$$

- K-map can be used to simplify boolean expressions.

- If all outputs are 1, then the simplified expression is simply 1.

ii) - MSB (Most significant bit) is placed at lower part, i.e. denotes columns.

$x'z'$	$y'z'$	$y'z$	yz	yz'
$x'0$	1	1	1	1
$x'1$	1	1		

$\rightarrow xy'$

- Groups can be formed of 2/4/8.

- Horizontal / vertical groups, also in same if 1 is at two ends, they can be grouped as well.


- Groups of 4 can be:



or




or

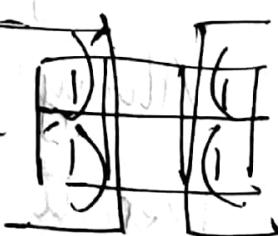

- Common variables are found & ANDed.

$$\therefore \text{Ans: } xy' + x'y$$

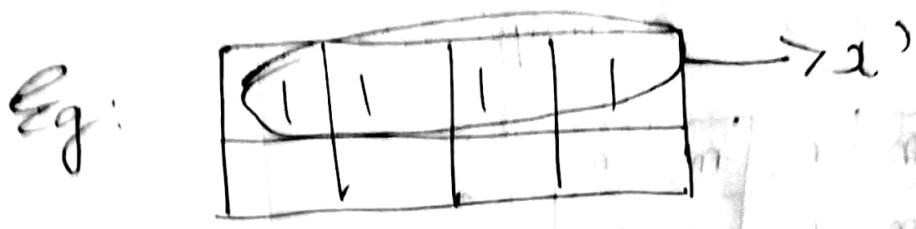

- No common variables from columns.

→ $\{1, 2, 3, 4\} \cap \{5, 6, 7, 8\} = \emptyset$

→ $\{1, 2, 3, 4\} \cap \{9, 10, 11, 12\} = \emptyset$

→ $\{1, 2, 3, 4\} \cap \{13, 14, 15, 16\} = \emptyset$

→ $\{1, 2, 3, 4\} \cap \{5, 6, 7, 8\} \cap \{9, 10, 11, 12\} \cap \{13, 14, 15, 16\} = \emptyset$

→ $\{1, 2, 3, 4\} \cup \{5, 6, 7, 8\} \cup \{9, 10, 11, 12\} \cup \{13, 14, 15, 16\} = \{1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16\}$

→ $\{1, 2, 3, 4\} \cup \{5, 6, 7, 8\} \cup \{9, 10, 11, 12\} \cup \{13, 14, 15, 16\} = \{1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16\}$

→ $\{1, 2, 3, 4\} \cup \{5, 6, 7, 8\} \cup \{9, 10, 11, 12\} \cup \{13, 14, 15, 16\} = \{1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16\}$

→ $\{1, 2, 3, 4\} \cup \{5, 6, 7, 8\} \cup \{9, 10, 11, 12\} \cup \{13, 14, 15, 16\} = \{1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16\}$

→ $\{1, 2, 3, 4\} \cup \{5, 6, 7, 8\} \cup \{9, 10, 11, 12\} \cup \{13, 14, 15, 16\} = \{1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16\}$

→ $\{1, 2, 3, 4\} \cup \{5, 6, 7, 8\} \cup \{9, 10, 11, 12\} \cup \{13, 14, 15, 16\} = \{1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16\}$

→ $\{1, 2, 3, 4\} \cup \{5, 6, 7, 8\} \cup \{9, 10, 11, 12\} \cup \{13, 14, 15, 16\} = \{1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16\}$

→ $\{1, 2, 3, 4\} \cup \{5, 6, 7, 8\} \cup \{9, 10, 11, 12\} \cup \{13, 14, 15, 16\} = \{1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16\}$

15/05/17


- Four-variable K-map:

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{11}	m_{10}
m_8	m_9	m_{11}	m_{10}

- Simplify the following functions using K-map:

- $F = \sum(0, 1, 2, 8, 10, 11, 14, 15)$
- $F = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$
- $F = A'B'C' + B'C'D' + A'B'C'D' + AB'C'$

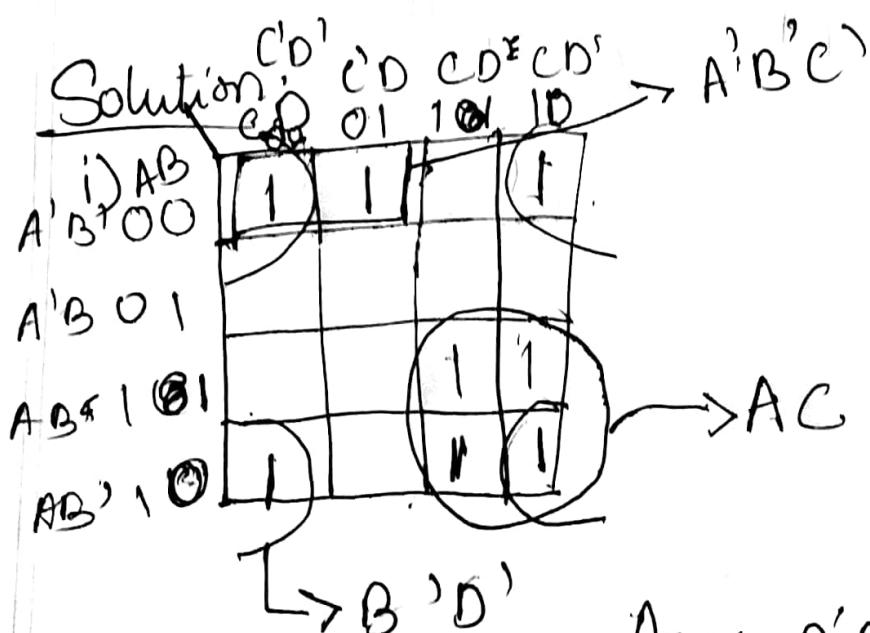- Check max³ minterm, eq. 15 - 4 bits needed
 $\therefore 4$ var



Ans: $B'D' + AC + A'B'C'$

- Groups of 2 →

1	1
---	---
- Groups of 4 →

1	1	1	1
---	---	---	---

1	1	1	1
1	1	1	1
1	1	1	1
1	1	1	1

- Groups of 8 →



1	1	1	1
1	1	1	1
1	1	1	1
1	1	1	1

Eg:

1	1	1	1
1	1	1	1
1	1	1	1
1	1	1	1

ABCD

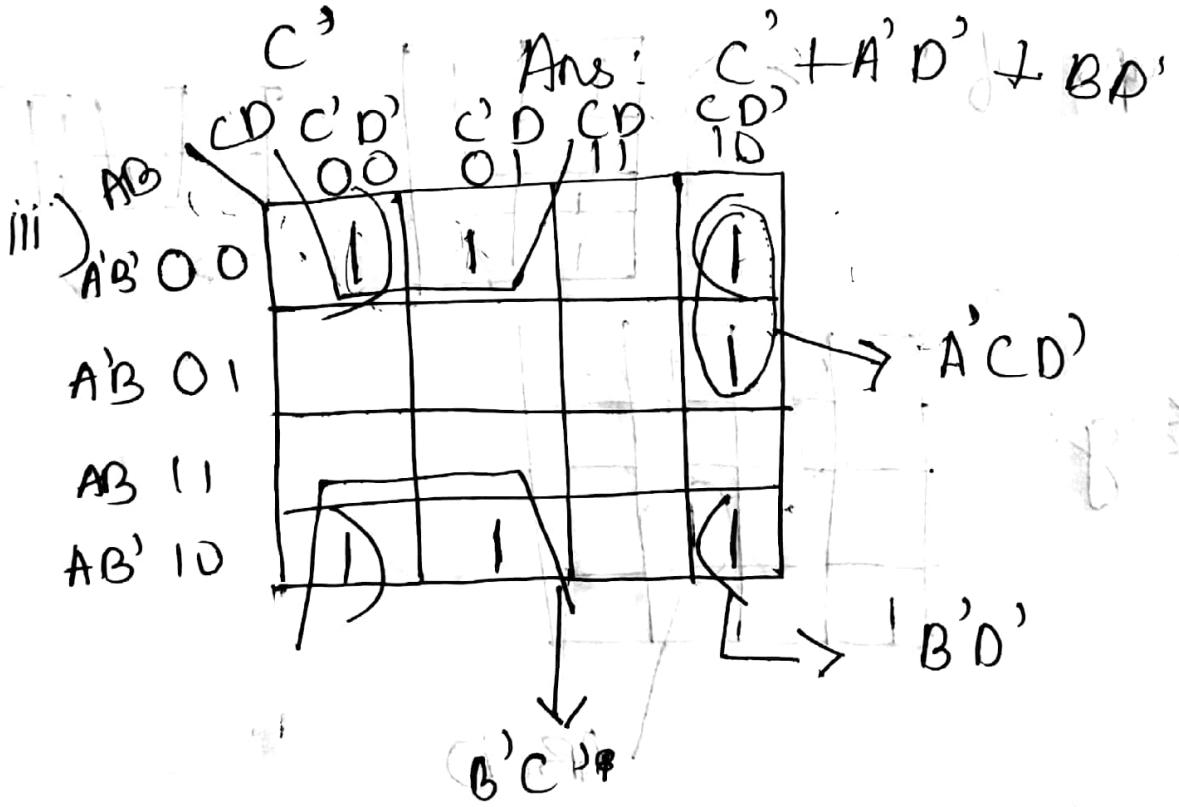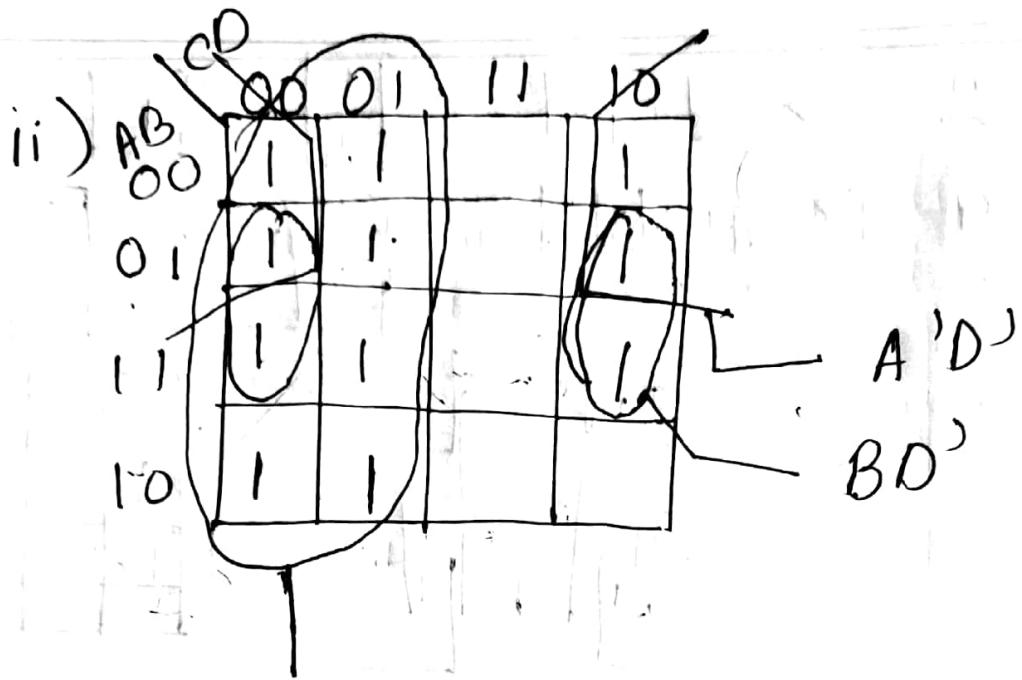
$$(a^2 + b^2 + c^2)A = ab \\ (a^2 + b^2 + c^2)B = -$$



$$\begin{aligned}
 \text{Ans: } & A'CD' + B'C'D' + B'D' \\
 = & B'(C'D') + A'CD'
 \end{aligned}$$

Karnaugh Map POS Minimization
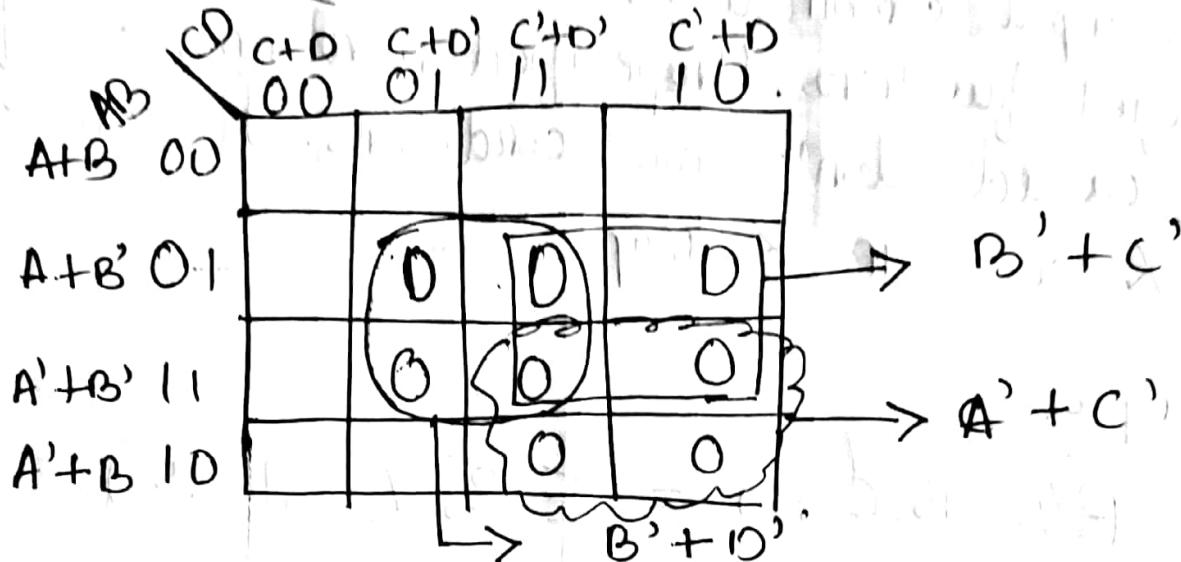
$$F_1 = \overline{A} (5, 6, 7, 10, 11, 13, 14, 15)$$



- Maxterm (0) given.
- POS format: 0 → not prime, 1 → prime

$$\therefore \text{Ans: } (B'+D') (A'+C') (B'+C')$$

$$B'D' + A'D' + A'C' = 1$$

$$B'D' + A'D' + A'C' = 1$$

$$P = 0$$

$$0000$$

Minimized POS expression:
The function is 1 for minterms 5, 6, 7, 10, 11, 13, 14, 15.

21/05/16

- Don't care conditions:

Functions that have unspecified output for some input combinations are called incompletely specified functions. Unspecified minterms of a function are called 'don't care' conditions. It can be represented by X or d in K-map.

Example:

$$i) F(A, B, C, D) = \sum(3, 7, 8, 11, 15)$$

$$d = \sum(0, 2, 5)$$

$$ii) F(A, B, C, D) = \sum(1, 3, 7, 11, 15)$$

$$d = \sum(0, 2, 5)$$

$$iii) F = A'B'D' + A'CD + A'BC$$

$$d = A'BC'D' + ACD + AB'D'$$

Eg: BCD \rightarrow Excess 3 code.

$$0 - 9$$

$$\begin{array}{ccc} \therefore 0000 & \rightarrow & \overline{\overline{1}} \\ \downarrow & & \downarrow \\ 1001 & \rightarrow & \overline{1} \end{array}$$

~~for 10,~~ Using 4 var K-map, for 10, 11, 12, 13, 14, 15 and 16, use (X) or d'

- 5 variable K-map:

AB\CD'E'	C'D'E'							
AB\000	0	1	3	2	6	7	5	4
AB\010	8	9	11	10	14	15	13	12
AB\110	24	25	27	26	30	31	29	28
AB\100	16	17	19	18	22	23	21	20

- Example: Simplify using K-map:

$$F = \Sigma(0, 2, 4, 6, 9, 11, 13, 15, 17, 21, 25, 27, 29, 31)$$

Mark 1's in K-map
 (0, 2, 4, 6, 9, 11, 13, 15, 17, 21, 25, 27, 29, 31)

• 6 Variable K-map:

ABC \ DEF

		000	001	011	010	110	111	101	100
		000	1	3	2	6	7	5	4
		001	8	9	11	10	14	15	13
		011	24	25	27	26	30	31	29
		010	16	17	19	18	22	23	21
		110	48	49	51	50	54	55	53
		111	56	57	59	58	62	63	61
		101	40	41	43	42	46	47	45
		100	32	33	35	34	38	39	37
									36

Simplify $F = \sum (6, 9, 13, 18, 19, 25, 27, 29, 41, 45, 57, 61)$
 (H.W)



1) Solution:

AB	CD	00	01	11	10
00	X		1	X	
01		X	1		
11			1		
10		1		1	

X - may be
0 or 1

~~A'B'C'D'~~

CD

- don't care may or may not be grouped. It will be grouped only if a '1' can be grouped with it.

Ans: $CD + B'C'D'$

AB	CD	00	01	11	10
00	X	1	1	X	
01		X	1		
11			1		
10		1		1	

Ans: $A'B' + CD$

	$CD' D'$	$C'D$	$C'D'$	CD
$A'B' 00$	1	.	.	1.
$A'B' 01$				
$AB' 11$				
$AB' 10$				


Solution:

- 5 var K-map is two 4 var K-map.
- If all 1's are in one cell, either right or left, grouping rules are like 4 var K-map.
- If mixed, ie. if 1's are in both cells. When folded, cells which overlap can be grouped.

Eg: 31th pos can be grouped with 15, 30, 29,

23

and 27.

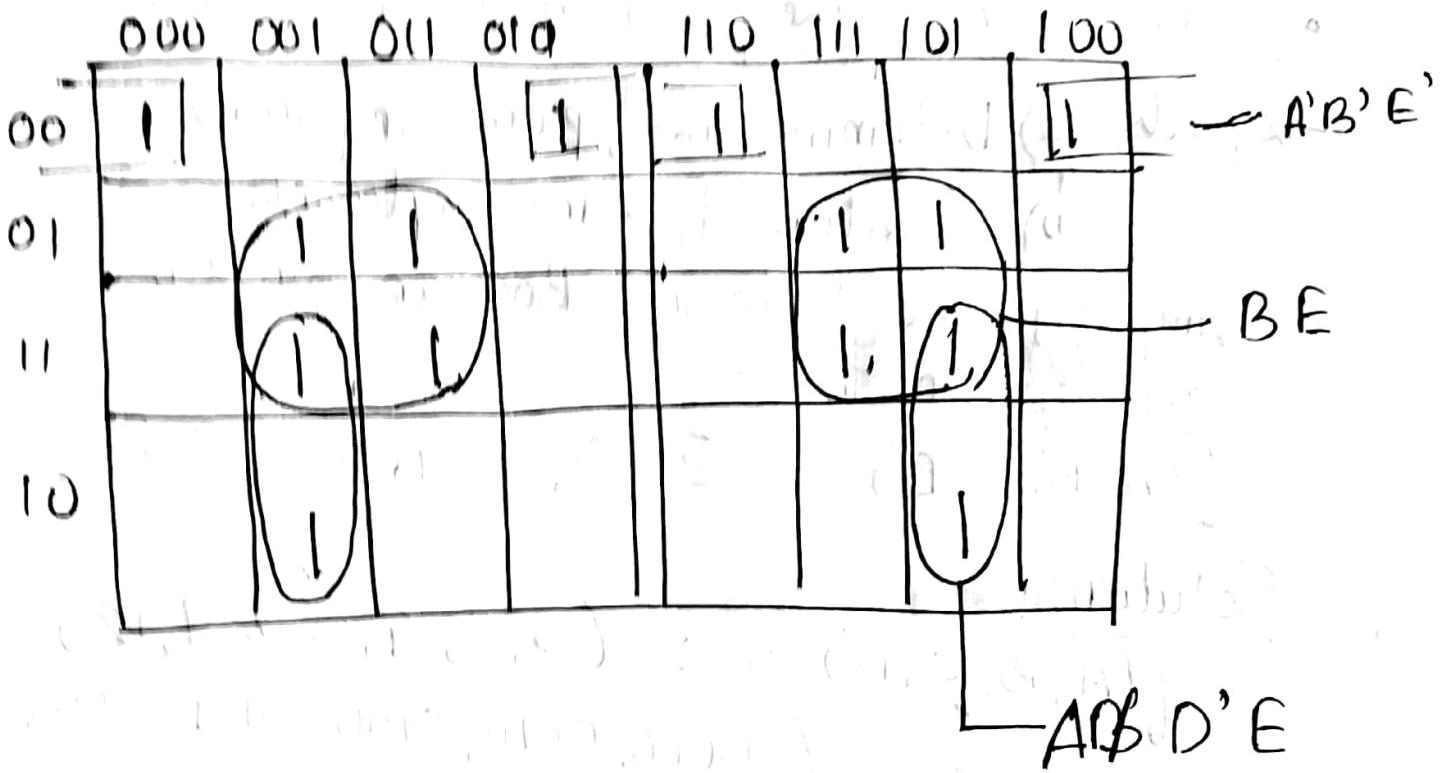

$$\text{Ans} = A'B'E + BE + BD'E$$

- For 6 var. K-map, take whichever ones are common for two folds.

& A

1

0

1

0

1

0

1

0

N/

22/05/17

Ouine - McCluskey / Tabulation Method:

- 2 parts: a) Determination of prime implicants,
b) Selection of prime implicants

Simplify the following Boolean function by using the tabulation method:

$$f(A, B, C, D) = \sum(0, 2, 4, 5, 8, 9, 12)$$

Solution:

$$f(A, B, C, D) = \sum(0, 2, 4, 5, 8, 9, 12)$$

$$\begin{aligned} &= \sum(0000, 0010, 0100, 0101, 1000, 1001, \\ &\quad 1100) \quad [\text{binary equivalent}] \end{aligned}$$

Step 1: Determination of prime implicants.

(a)

	A	B	C	D
0 Is	0	0	0	0
1 Is	2	0	0	1
2 Is	4	0	1	0
3 Is	8	1	0	0
4 Is	5	0	1	0
5 Is	9	1	0	0
6 Is	12	1	1	0

(b)

A	B	C	D	No. of diff. bits = 1
0	0	0	0	
0	2			
0	4	0	0	
0	8	0	0	
4, 5	0	1	0	
4, 12		1	0	
8, 9	1	0	0	
8, 12	1	1	0	

L compared with immediate above group.

Use those nos used
from (b) and that of (c)

(c)	A	B	C	D
0, 4, 8, 12	-	-	0	0
0, 8, 4, 12	-	-	0	0

So, prime implicants:
 $A'B'D' + A'B'C' + AB'C' + C'D'$

Check between groups
for 1 in same position
and with diff. of only 1 bit.

Step 2: Selection of prime implicants Place 1 in place of diff. bit.

$A'B'D'(0,2)$	0	2	4	5	8	9	12
$A'B'D'(0,2)$	X	X					
$A'BC'(4,5)$			X	X			
$AB'C'(8,9)$					X	X	
$C'D'(0,4,8,12)$	X		X		X		X

∴ Essential prime implicants: $A'B'D' + A'BC' + AB'C' + C'D'$

There is no uncheckered minterm value, so the unsimplified answer is:

$$f(A, B, C, D) = A'B'D' + A'BC' + AB'C' + C'D' \quad (\text{Ans})$$

L choose the single crosses from each column
- Final ans must have all essential prime implicants

Chapter -4

Combinational Logic

A combinational circuit consists of logic gates whose outputs at any time are determined directly from the present combination of inputs without regard to previous inputs.

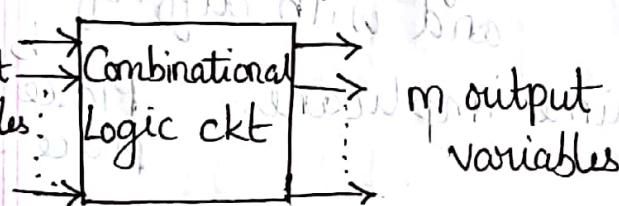


Fig: Block Diagram of combinational ckt.

- Design procedure of combinational logic ckt.
 - ① The problem is stated
 - ② The no. of available input variables & required output variables is determined.
 - ③ The input and output variables are assigned letter symbols.
 - ④ The truth table is derived.
 - ⑤ The simplified Boolean function for each output is obtained.
 - ⑥ The logic diagram is drawn.

Example: Design a 3-bit square circuit.

Solution: Say input variables: A, B, C
output variables: $F_1, F_2, F_3, F_4, F_5, F_6$

• Truth table:

Input			Output					
A	B	C	F_1	F_2	F_3	F_4	F_5	F_6
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1
0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	0	0	1
1	0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0	1
1	1	0	1	0	1	0	1	0
1	1	1	1	1	0	0	0	1

• Boolean functions:

• Boolean functions

$$F_1 = \Sigma(6, 7) = AB\bar{C} + ABC = AB$$

$$F_2 = \Sigma(4, 5, 7) = A(\bar{B} + C)$$

$$F_3 = \Sigma(3, 5) = C(A \oplus B)$$

$$F_4 = \Sigma(2, 6) = B\bar{C}$$

$$F_5 = 0, \quad F_6 = C$$

- ## • Block diagram:

Do it yourself

[Quiz #2
13/06/17 - Tuesday]

29/05/17

Carry in:

$$\begin{array}{r} 101 \\ + 001 \\ \hline 110 \end{array}$$

Carry out:

$$\begin{array}{r} 110 \\ + 011 \\ \hline 1001 \end{array}$$

- Half adder: adds 2 bits and produces a sum & a carry output.

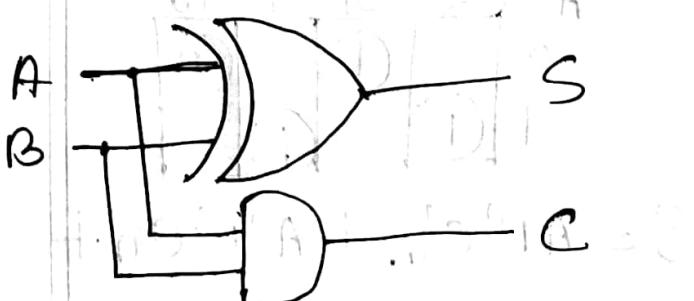


Fig: block diagram of a half adder

Truth table

Input		Output	
A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Circuit diagram:



Output equations:

$$S = \overline{A}B + A\overline{B} = A \oplus B$$

$$C = AB$$

$$\begin{aligned} S &= \overline{A}B + A\overline{B} \\ S &= A \oplus B \end{aligned}$$

- Full adder: accepts 2 input bits & an input carry and generates a sum output & an output carry.

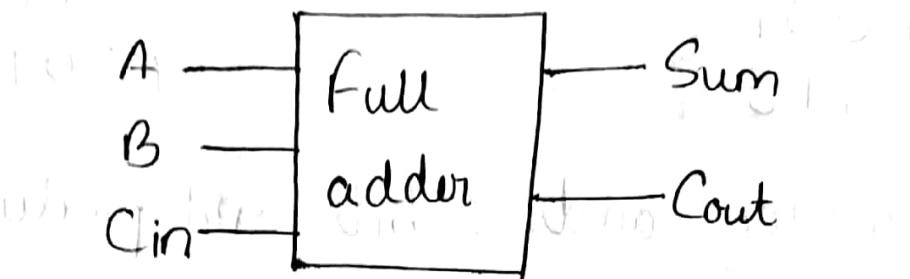


Fig: Block diagram

Truth table

Input			Output	
A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Output Equations:

Cin		000	01	11	10
A	B	0	1	0	1
0	0	0	1	0	1
1	0	1	0	1	0

$$\text{Cout} = AC_{in} + AB + BC_{in}$$

Sum:

Cin		00	01	11	10
A	B	0	1	0	1
0	0	0	1	0	1
1	0	1	0	1	0

$$S = AB'C_{in} + A'B'C_{in} +$$

$$ABC_{in} + A'BC_{in}$$

$$= C_{in}(AB' + A'B) + C_{in}(A'B + AB)$$

$$= C_{in}x + C_{in}x'$$

$$= C_{in} \oplus x$$

Ckt diagram:

Do it yourself

$$= \text{Cin} \oplus (AB' + A'B)$$

$$= \text{Cin} \oplus (A \oplus B)$$

Say,

$$x = AB' + A'B$$

$$\therefore x' = A'B + AB$$

* Self study

- i) Arrangement of 2 half adders to form a full adder
- ii) half subtractor
- iii) full subtractor
- iv) carry look ahead adder

• Binary parallel adder: (definition)

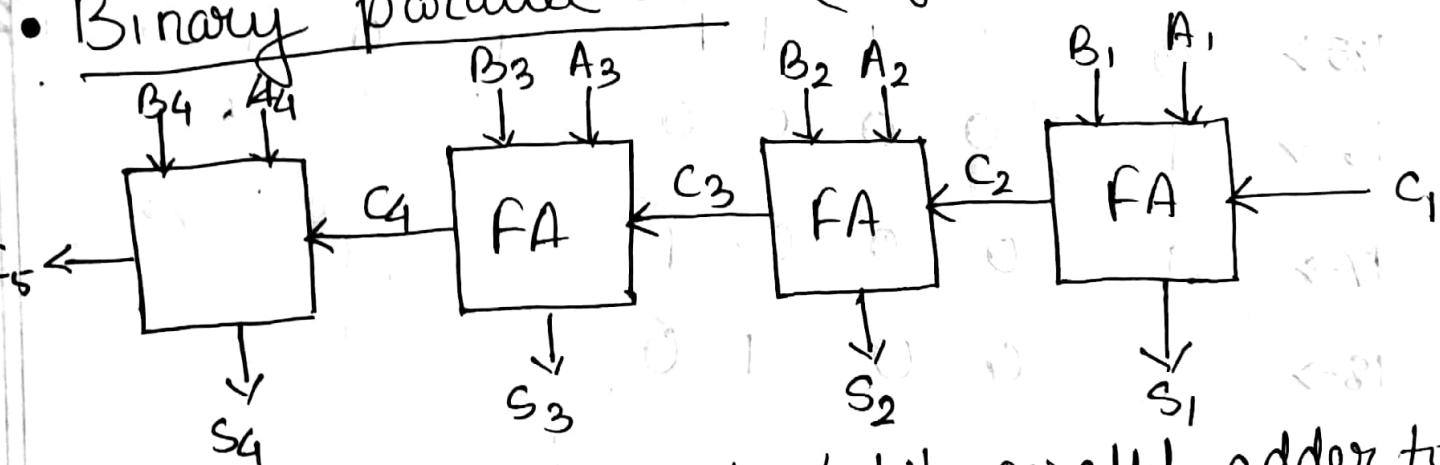


Fig: Block diagram of 4 bit parallel adder to add $(A_4 A_3 A_2 A_1)$ and $(B_4 B_3 B_2 B_1)$

30/05/17

- BCD Adder: A BCD adder is a circuit that adds two BCD digits in parallel & produces a sum digit also in BCD.

Binary

	Cout	S_4	S_3	S_2	S_1	BCD	Cout	S_4	S_3	S_2	S_1
0 →	0	0	0	0	0	0	0	0	0	0	0
9 →	0	1	0	0	1	9	0	1	0	0	1
10 →	0	1	0	1	0	10	1	0	0	0	0
11 →	0	1	0	1	1	11	1	0	0	0	1
12 →	0	1	1	0	0	12	01	0	0	1	0
13 →	0	1	1	1	1	13	0	1	0	0	1
16 →	1	0	0	0	0	16	1	0	0	0	0
17 →	1	0	0	0	1	17	1	0	0	1	0
18 →	1	0	0	1	0	18	10	0	1	0	0

$$X = \text{Cout} + \overbrace{S_4(S_3 + S_2)}^1$$

$$X = \underbrace{\text{Cout}}_{16-18} + S_4 S_3 + S_4 S_2$$

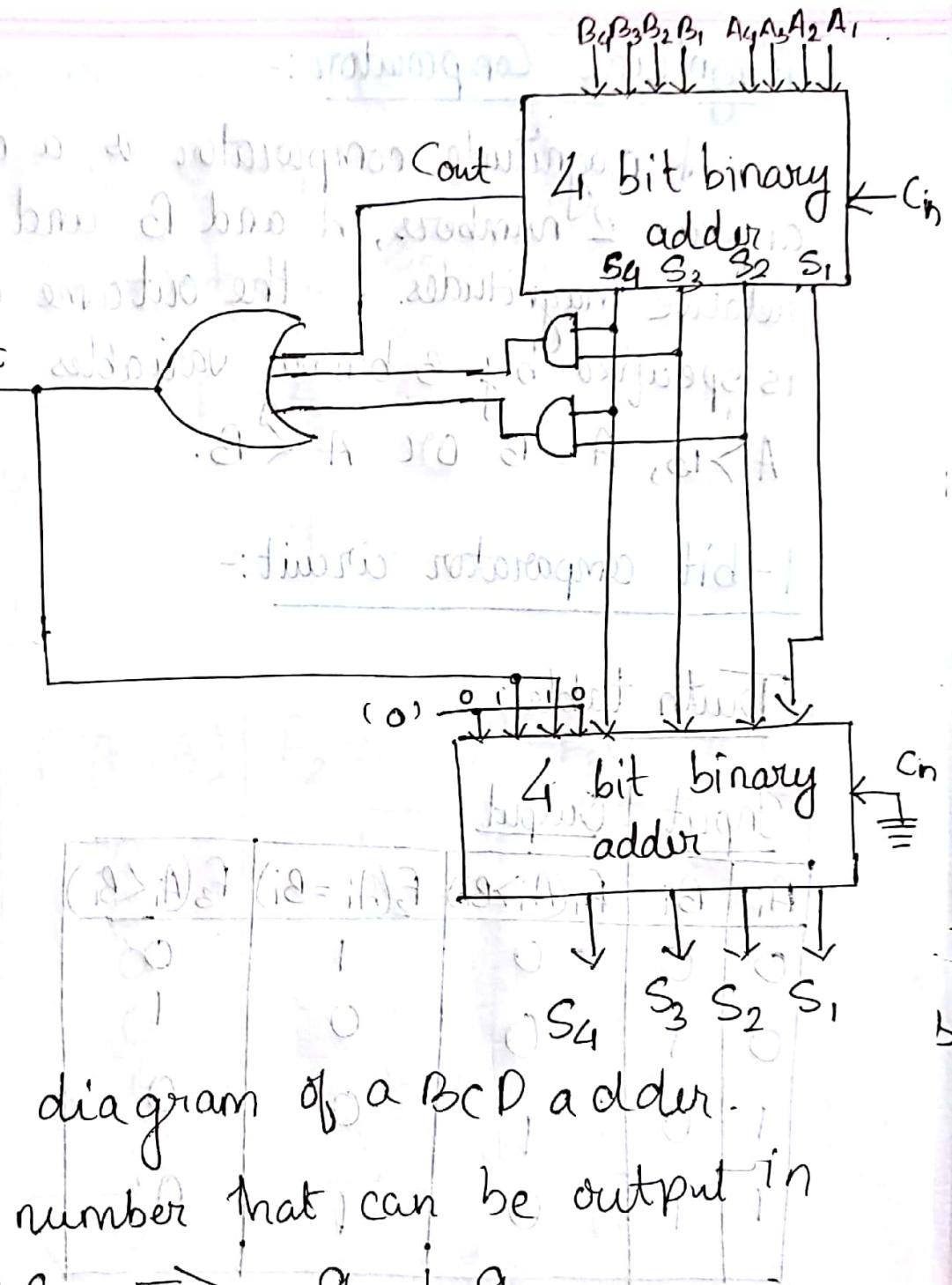


Fig: block diagram of a BCD adder.

* Maximum number that can be output in

$$\text{BCD} = 18 \Rightarrow 9 + 9$$

$$18 = 1000$$

$$1000 = 100100$$

Max no. of 1's in BCD is 3

4/06/17

Magnitude Comparator :-

A magnitude comparator is a combinational ckt that compares 2 numbers, A and B and determines their relative magnitudes. — the outcome of the comparison is specified by 3 binary variables that indicate whether $A > B$, $A = B$ or $A < B$.

1-bit comparator circuit:-

Truth table:

<u>Input</u>	<u>Output</u>	$f_1(A_i > B_i)$	$f_2(A_i = B_i)$	$f_3(A_i < B_i)$
0 0		0	1	0
0 1		0	0	1
1 0		1	0	0
1 1		0	1	0

Output equations: $f_1 = A_i B_i'$ $f_2 = A_i' B_i + A_i B_i'$
 $= A_i \oplus B_i$

$$f_3 = A_i' B_i$$

Ckt diagram: Draw it yourself

Two bit comparator:

$$A = A_2 A_1, \quad B = B_2 B_1$$

$$F_1(A > B) = (A_2 > B_2) + (A_2 = B_2)(A_1 > B_1)$$

$A_2 A_1$		$B_2 B_1$		F_1	F_2	F_3
0	0	0	0			
1	1	1	1			

A	B	$F_1(A > B)$	$F_2(A = B)$	$F_3(A < B)$
$A_2 A_1$	$B_2 B_1$			
00	00	0	1	0
00	01	0	0	1
00	10	0	0	1
00	11	1	0	0
01	00	1	1	1
11	11	0	1	0

Use minterms to find equations

$$F_1(A > B) = (A_2 < B_2) + (A_2 = B_2)(A_1 < B_1)$$

$$F_2(A = B) = A_2' B_2 + (A_2 \oplus B_2)(A_1' B_1)$$

$$F_3(A < B) = (A_2 = B_2)(A_1 = B_1) = (A_2 \odot B_2)(A_1 \odot B_1)$$

5/06/17

Multiplexer / MUX / Data Selector:

- A digital multiplexer is a combinational ckt that selects binary information from one of many input lines and directs it to a single output line.
- The selection of a particular input line is controlled by a set of selection lines. Normally, there are 2^n input lines & n selection lines.
- The size of a MUX is specified by the number 2^n of its inputs line & the single output line.

Uses:

Example: 4×1 MUX

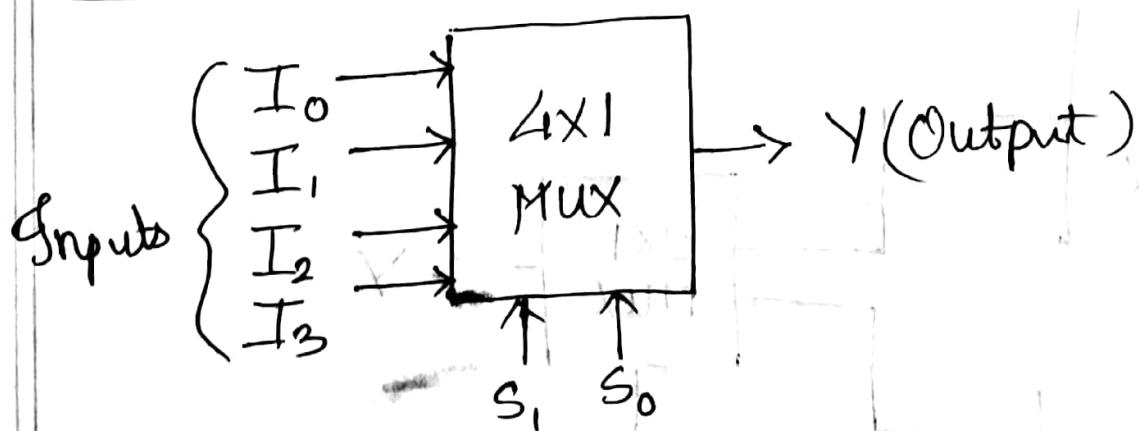


Fig: Block diagram of a 4×1 MUX

Function table of a 4x1 MUX:

S_1, S_0	Y	$I_0 = 0, Y = 0$	$I_0 = 1, Y = 1$
0 0	I_0		
0 1	I_1		
1 0	I_2		
1 1	I_3		

Output Equation:

$$Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$

Mux Expansion:

* Design a 4x1 MUX using 2x1 MUX's only.

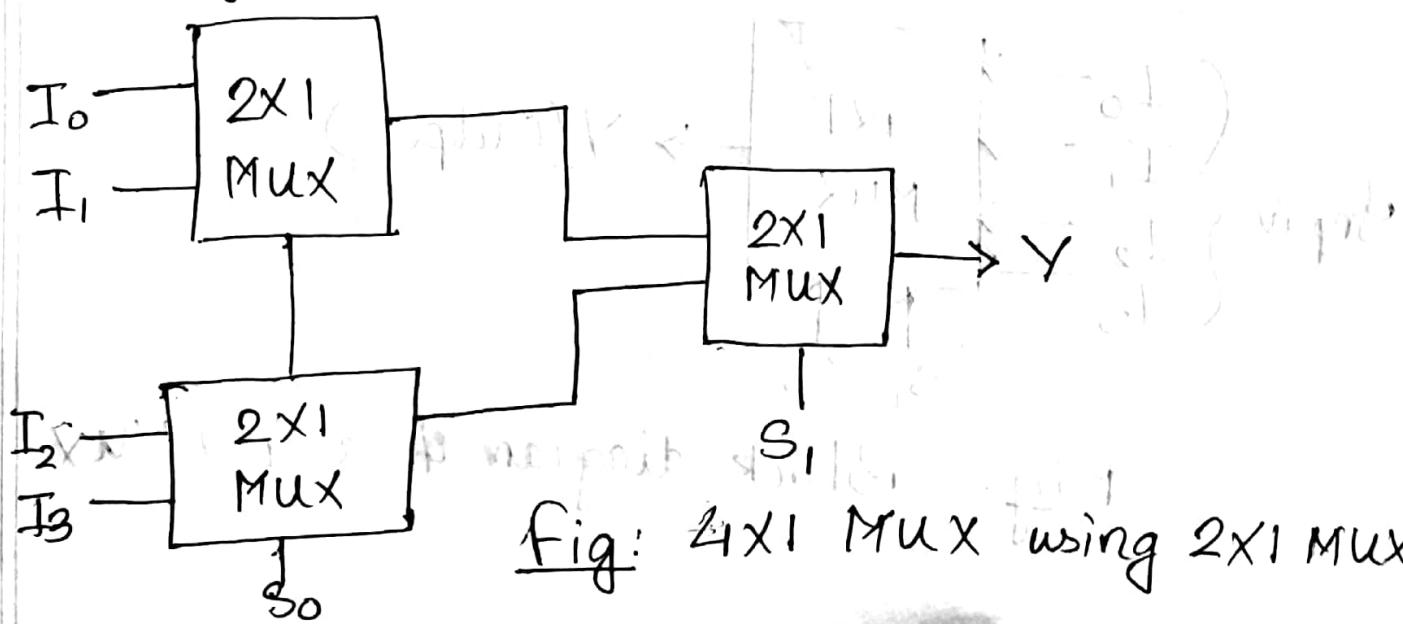


Fig: 4x1 MUX using 2x1 MUXs.

** 06/06/'17
End of N.B.

11/06/17

Decoder :-

A decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines.

Eg: 2×4 , 3×8 , 4×16 decoders etc.

- Active low enable (\bar{E}) - IC activates with enable pin
- Active high enable (E) - " " " " " " 1.
there is enable pin. ICs have some extra pins. One of
- Example: 2×4 decoder

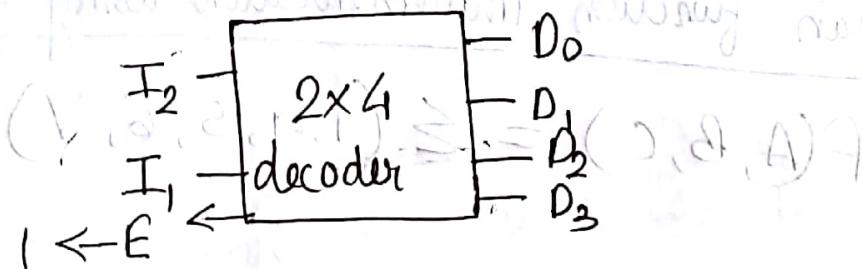


Fig: 2×4 decoder.

Truth Table:

I ₂	I ₁	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Output equations:

$$D_0 = \overline{I_2} I_1$$

$$D_1 = \overline{I_2} \overline{I_1}$$

$$D_2 = I_2 \overline{I_1}$$

$$D_3 = I_2 I_1$$

Logic Diagram:

See from book.

• Boolean function implementation using decoder:

$$f(A, B, C) = \sum(1, 4, 5, 6, 7)$$


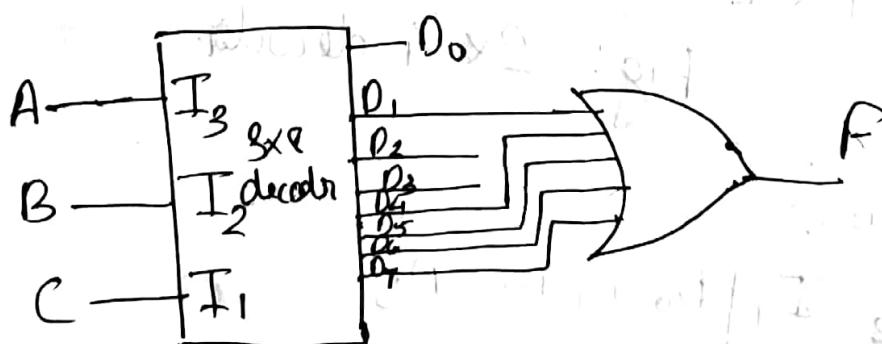


Fig: Implementation of f

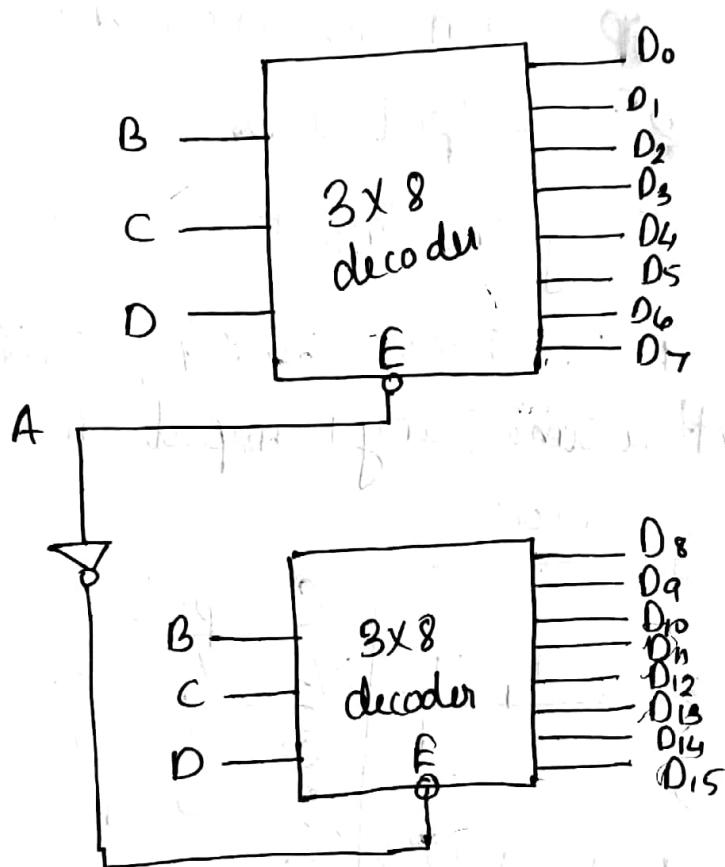- Design a 4×16 line decoder using two 3×8 decoders:



- Use NAND gate when active low enable used.

• Encoders:

- Does reverse operation to decoder
- Input lines: 2^n , output lines : n
- Constraint : only one input is active at a time

Example : 4×2 , 8×3 , 16×4 , 512×9 encoder etc. (At a time, any 1 input has to be 1, rest 0.)

• 8×3 binary encoder:


Input								Output		
I ₇	I ₆	I ₅	I ₄	I ₃	I ₂	I ₁	I ₀	Y ₂	Y ₁	Y ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	1
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Equations:

$$Y_2 = I_7 + I_6 + I_5 + I_4$$

$$Y_1 = I_7 + I_6 + I_3 + I_2$$

$$Y_0 = I_7 + I_5 + I_3 + I_1$$

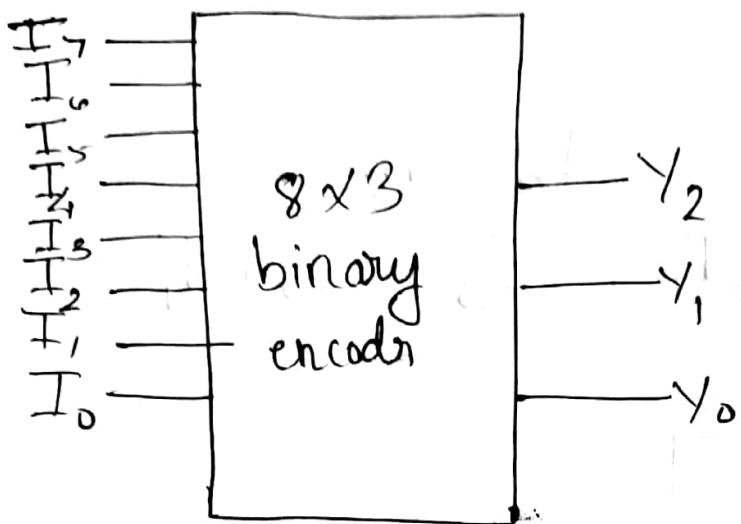

- Circuit diagram

See from book

- Priority encoders

- Encoder with priority function
- Multiple inputs may be true simultaneously.
- Higher priority input gets the precedence

- 4-input Priority Encoder:


Priority order: $I_3 > I_2 > I_1 > I_0$

Input				Output		
I_3	I_2	I_1	I_0	Y_1	Y_0	
1	x	x	x	1	1	0000 xx
0	1	x	x	1	0	
0	0	1	x	0	1	
0	0	0	1	0	0	

Equations:

$$Y_1 = I_3 + \bar{I}_3 I_2 = I_3 + I_2$$
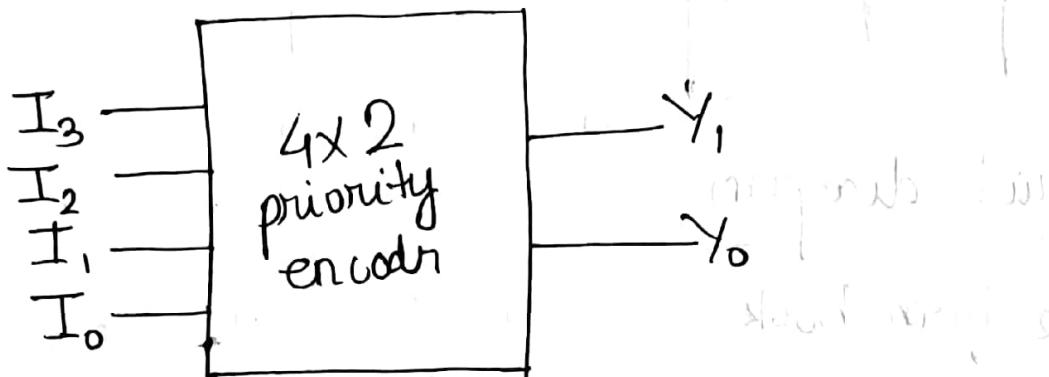
$$Y_0 = I_3 + \bar{I}_3 \bar{I}_2 I_1 = I_3 + \bar{I}_2 + I_1$$



Quiz #3

11/07/17


Tuesday.

Up to here (Chapter 4 remaining)

Chapter - 5

04/07/17

Sequential Circuit

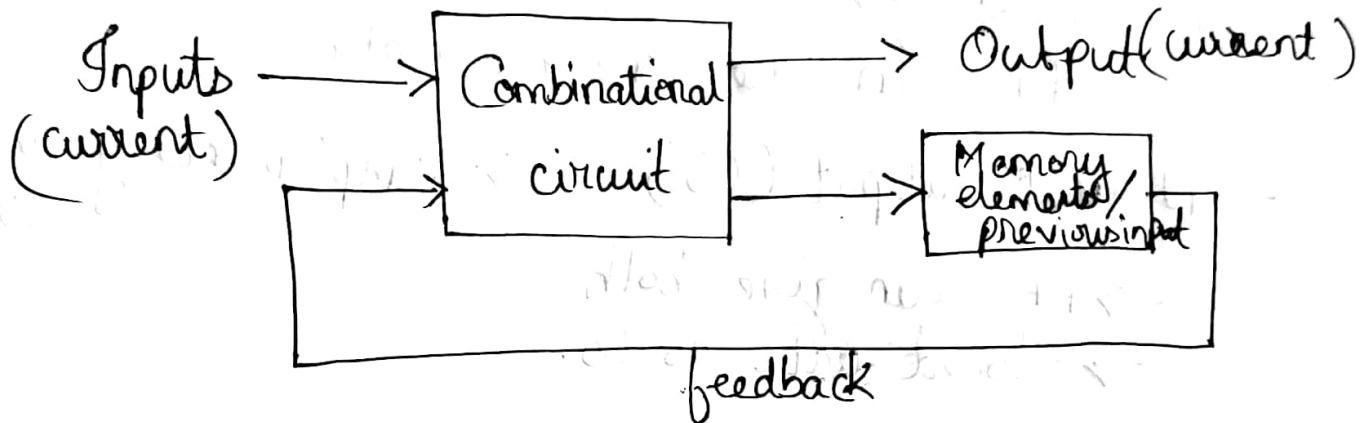

Sequential circuit eg: football scoring.

$$\text{Output} = f(\text{input}, \text{previous output})$$

- A memory element is required to store previous output.

Classification of sequential circuit:

- Asynchronous sequential circuit: output changes as soon as input changed
- Synchronous sequential circuit: output does not change simultaneously. It is dependant on time. Clock pulse when pressed, output changes, or else output doesn't change.

Flip-flops:

- Memory elements which store output are called flip-flops (FFs.)
- One FF can store one-bit data.
- Normal output (Q) \rightarrow Complementary output (Q')
 - ↳ FFs can give both
 - \rightarrow Stored data as Q .
- 4 types of FFs : i) SR
ii) JK
iii) T
iv) D

Basic flip-flop circuit:

SR FF:

- using NOR gate
- using NAND gate

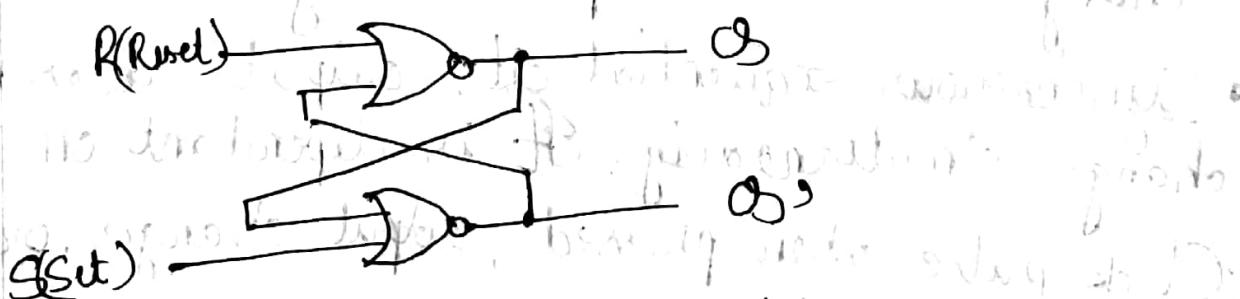


Fig: using NOR gate

S	R	Q	Q'
1	0	1	0
* 0	0	1	0
0	1	0	1
* 0	0	0	1
1	1	0	0

→ For same inputs, different outputs are obtained, due to different previous outputs.

Initially, Q & Q' 's values aren't known

$$S \rightarrow 1, Q' = 0$$

$$R \rightarrow 0 \therefore Q \rightarrow 1$$

If any one of the input is 1, output is 0.

Now the values of Q & Q' are known.

$$Q \rightarrow 1, Q' \rightarrow 0$$

Applying, $S \rightarrow 0, R \rightarrow 0$

$$\therefore Q' \rightarrow 0$$

$$\therefore Q \rightarrow 1$$

Applying, $S \rightarrow 0, R \rightarrow 1$

$$Q' \rightarrow 0$$

$$Q \rightarrow 0$$

$$\therefore Q' \rightarrow 1$$

* We can never use S and $R = 1$ at the same time in SR FF, since both Q & $Q' = 0$ which is not possible logically.

The inputs should begin with at least one of them being 1.

$$S \rightarrow 1, \emptyset \rightarrow 1$$

$$R \rightarrow 1, \emptyset' \rightarrow 1$$

Now it's time to add a left & right.

$$O \leftarrow \emptyset, 1 \leftarrow \epsilon$$

$$1 \leftarrow \epsilon, O \leftarrow \emptyset$$

O is right of the right end of the first.

Now we have to find another symbol.

$$O \leftarrow \emptyset, 1 \leftarrow \epsilon$$

$$1 \leftarrow \epsilon, O \leftarrow \emptyset \text{ right}$$

$$O \leftarrow \emptyset$$

$$1 \leftarrow \epsilon, O \leftarrow \emptyset$$

$$O \leftarrow \emptyset$$

$$O \leftarrow \emptyset$$

$$1 \leftarrow \epsilon$$

With the 1 & the 2 now we can start


to do what seems like it will work
when you see for a number 0:

B


9/07/17

- Clocked SR Flip-flop (FF):

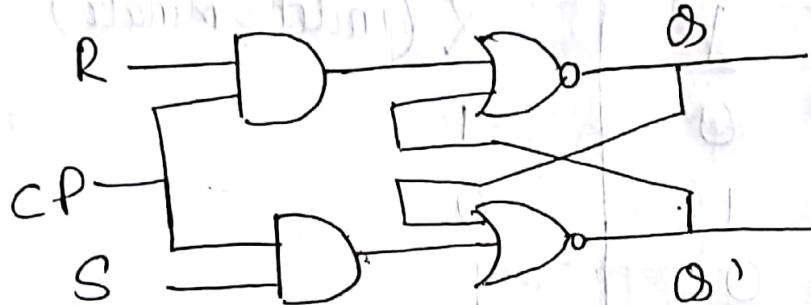The clocked SR FF in the following fig. consists of a basic NOR FF and 2 \oplus AND gates.



a) logic diagram

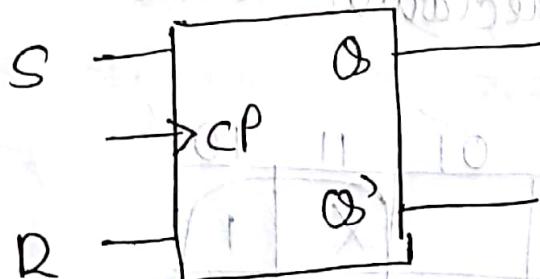

b) graphic symbol

(t) - Previous of P
 current i/p
 current o/p

$\phi(t)$	S	R	$\phi(t+1)$	L
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	X (indeterminate)	1
1	0	0	1	1
1	0	1	0	1
1	1	0	1	1
1	1	1	X (indeterminate)	1

c) characteristic table

ϕ	SR	00	01	11	10
0			X	1	
1	1	1	X	1	

$$\phi(t+1) = S + R' \phi$$

d) Characteristic equation

S	R	$O(t+1)$
0	0	0
0	1	0
1	0	1
1	1	X

e) Truth table


$O(t)$	$O(t+1)$	S	R
0	0	0	X
0	1	1	0
1	0	0	1

b) excitation table


S	R	$O(t+1)$
0	0	0
1	1	1
0	1	1

$O(t)$	$O(t+1)$
0	0
1	1

- Clocked D flip flop:

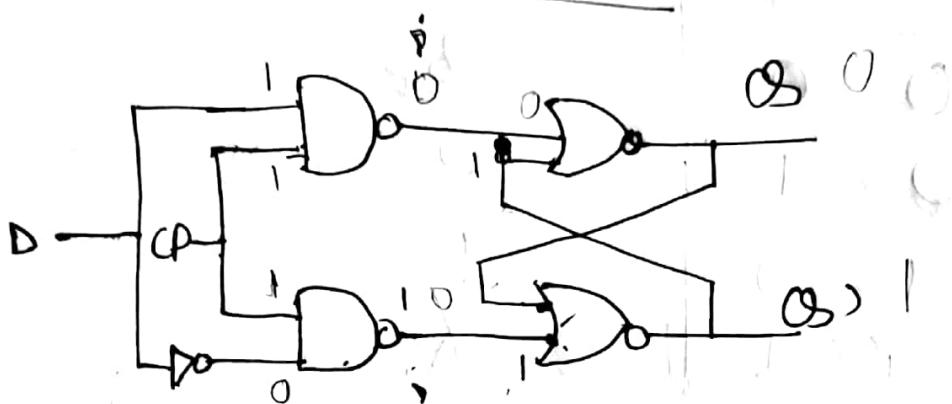

a) logic diagram

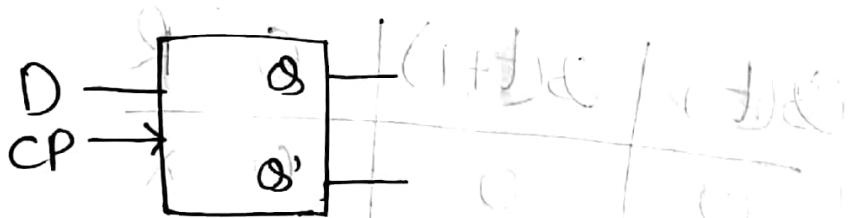

b) graphical symbol

Q	D	$Q(t+1)$
0	0	0
0	1	1
1	0	0
1	1	1

c) characteristic table

d) characteristic equation:

$$Q(t+1) = D$$

e) Truth table

D	$Q(t+1)$
0	0
1	1

f) Excitation table:

$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

$\bar{Q}(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0


T	$Q(t+1)$
0	Q_t
1	Q'_t

Truth Table

e) Excitation table

- Conversions

From JK FF to TFF:

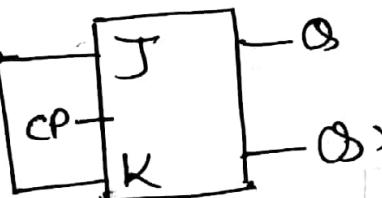


JK:

$$\begin{aligned}
 Q(t+1) &= JQ' + K'Q \\
 &= JQ' + J'Q \quad (\because J=K) \\
 &= J \oplus Q
 \end{aligned}$$


T:

$$Q(t+1) = T \oplus Q$$

- Clocked T flip flop

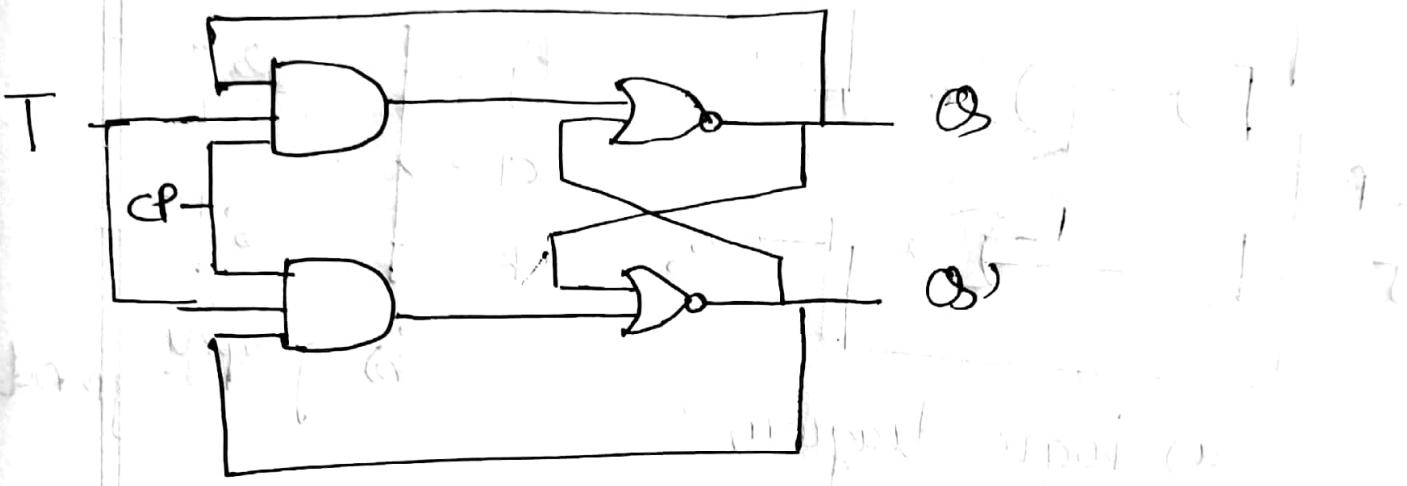


a) Logic diagram

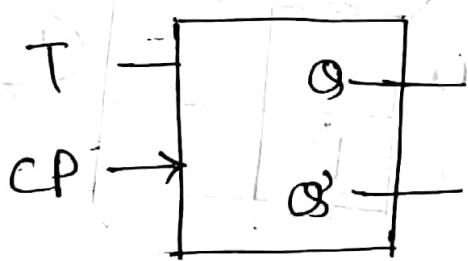

b) Graphic symbol

Q	T	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

c) Characteristic Table

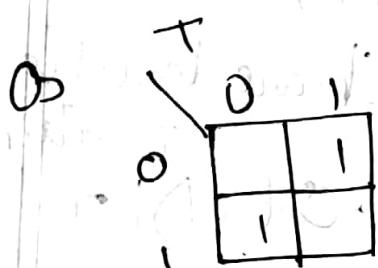


$$\begin{aligned} Q(t+1) &= \bar{T} Q + T' Q \\ &= T \oplus Q \end{aligned}$$


d) Characteristic equation.

10/07/11

Clocked JK Flip flop:

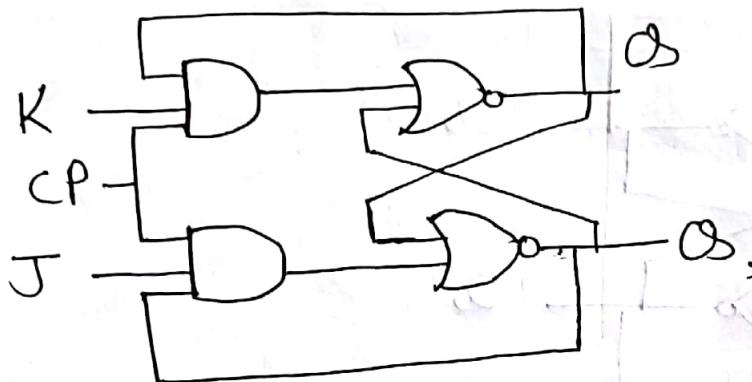

a) logic diagram

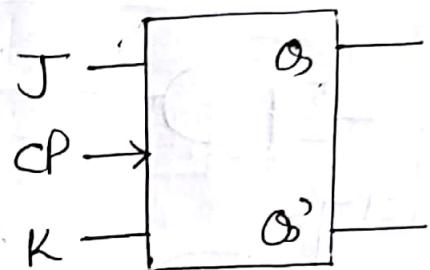

b) graphic symbol

$Q(t)$	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

c) Characteristic table

J	K	$Q(t+1)$
0	0	$Q(t)$ (unchanged)
0	1	$Q(t)$ (reset)
1	0	$Q(t)$ (set)
1	1	$Q'(t)$ (toggle)

e) Truth table

$Q(t)$	J	K	$Q(t+1)$
0	0	0	0
0	0	1	1
1	0	0	1
1	0	1	0
1	1	1	1

~~$Q(t+1) = \bar{J}Q(t) + \bar{K}Q(t)$~~


$$Q(t+1) = JQ(t) + K'Q(t)$$

d) Characteristic equation.

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

b) Excitation table

From JK FF to D FF:

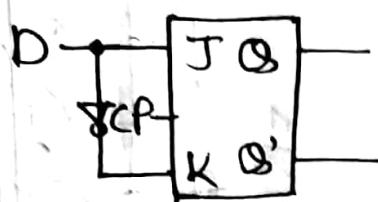

JK:

$$\begin{aligned}
 Q(t+1) &= JQ' + K'Q \\
 &= JQ' + (J')'Q \quad [\because K = J] \\
 &= JQ' + JQ \quad [\because (J')' = J] \\
 &= J(Q + Q') \quad [\because Q + Q' = 1]
 \end{aligned}$$

D:

$$Q(t+1) = D$$

Triggering of flip flops:

i) Positive edge triggering:


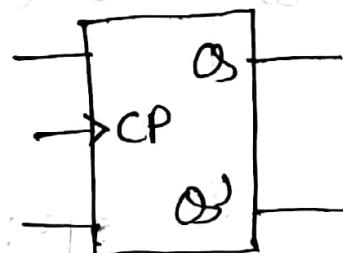


Fig: positive edge triggering

ii) Negative edge triggering:

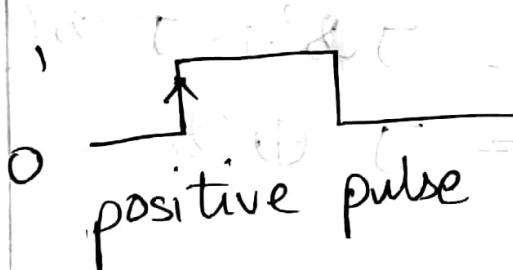

Negative
pulse



Fig: Negative edge triggering.

• Master slave Flip flop : (Self study)

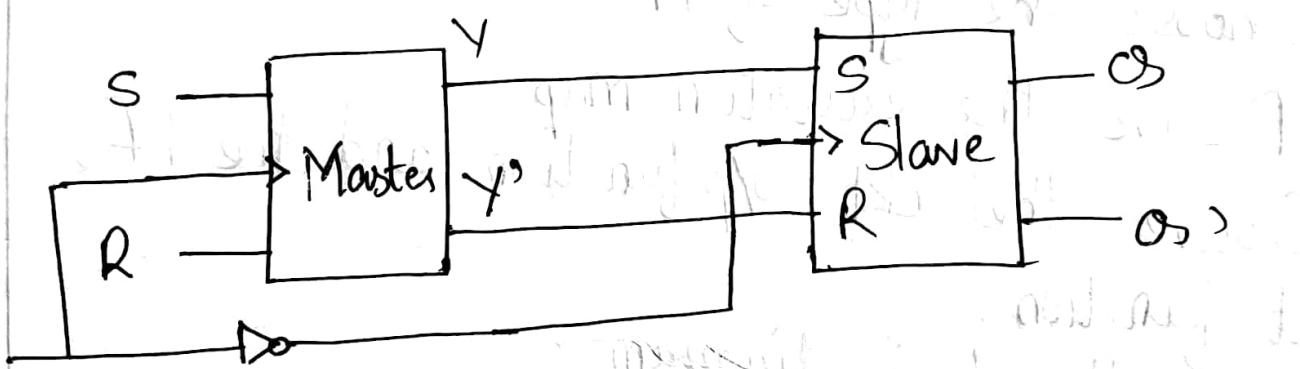



Fig: Master slave SR FF

16/07/17

Design Procedure of Synchronous Sequential Circuit

- i) Problem is stated.
- ii) Obtain the state table.
- iii) State reduction (X)
- iv) Assign binary values to each state.
- v) Determine the number of FFs needed and assign a letter symbol to each.
- vi) Choose the type of FF to be used.
- vii) Derive the excitation map.
- viii) Derive the ckt o/p function and the FFs input function.
- ix) Draw the logic diagram.

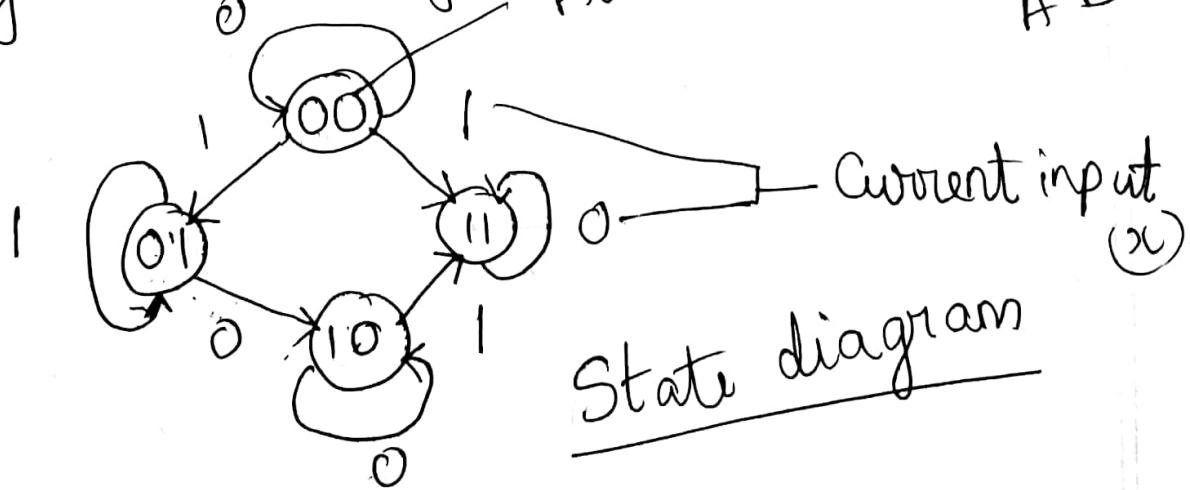Example: Design a synchronous sequential ckt for the given state diagram.



Solution:

State table:

Present state		Next state			
		$x = 0$		$x = 1$	
A	B	A	B	A	B
0	0	0	0	0	1
0	1	1	0	0	1
1	0	1	0	1	1
1	1	1	1	0	0

One FF can store 1-bit
We need 2 FFs. We will use 2 JK FFs.
For 2-bits,
generally

Excitation map:

Present state		Input	Next state		FF's inputs			
A	B	x	A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

- FF's input equations:

A	Bx	00	01	11	10
0				1	
1	X	X	X	X	

$$J_A = B\bar{x}$$

A	Bx	00	01	11	10
0		X	X	X	X
1				1	

$$K_A = Bx$$

A	Bx	00	01	11	10
0		1	X	X	
1		1	X	X	


A	Bx	00	01	11	10
0		X	X		1
1		X	X	1	

$$J_B = x$$

$$\bar{J} K_B = \bar{A} \oplus \bar{x}$$

- Logic Diagram:

Fig: logic diagram for the given problem

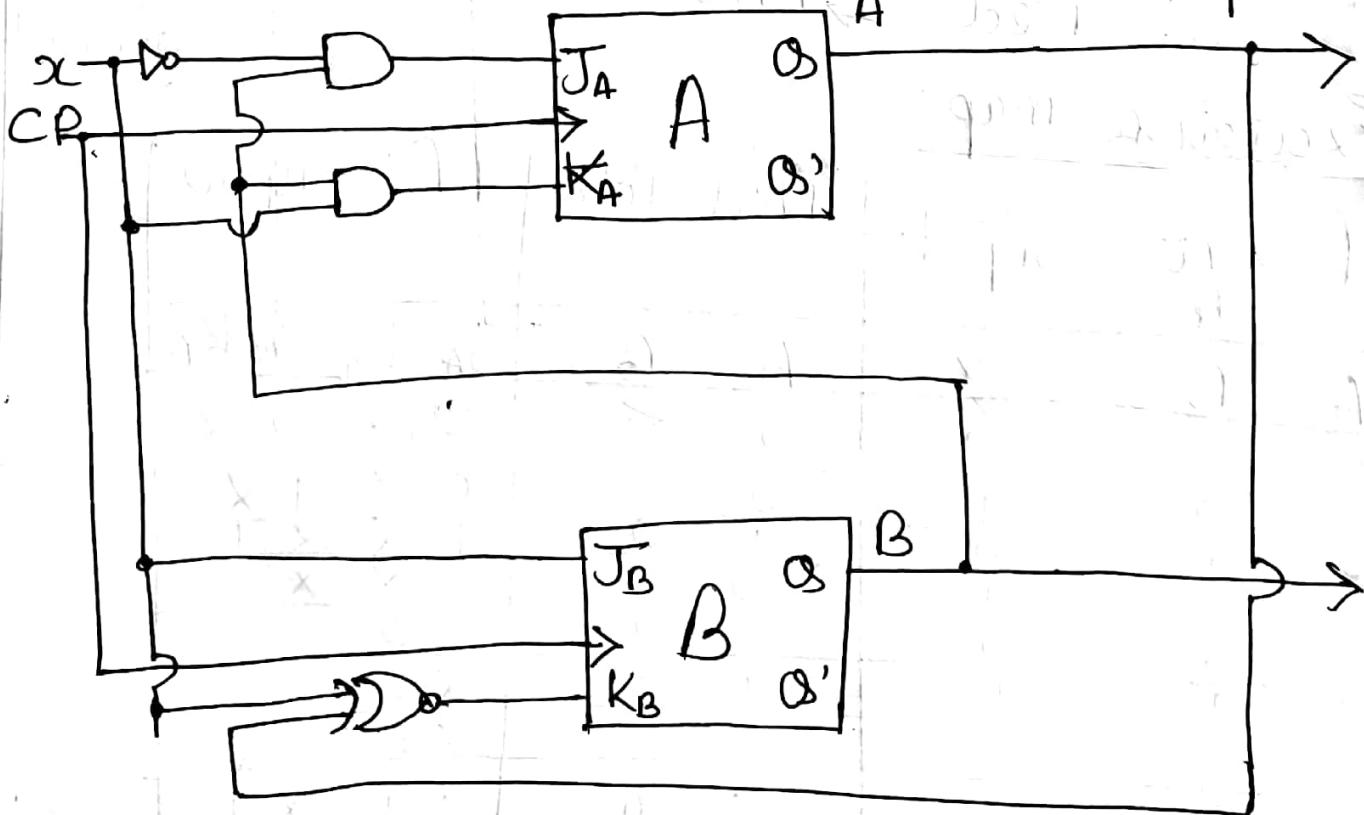

FF's Input Equations:

O_2	0	0	1
1	X	X	

O_2	0	0	1
0	X	X	
1	0	1	

$$J_2 = O_1$$

O_2	0	0	1
1	(1)	X	
0	1	X	

$$J \ K_1 = 1$$


O_2	0	0	1
0	X	X	
1	(X)	(X)	

$$K_1 = 1$$

O_2	0	0	1
0	X	(1)	
1	X	(1)	

$$K_1 = 1$$

Logic Diagram:

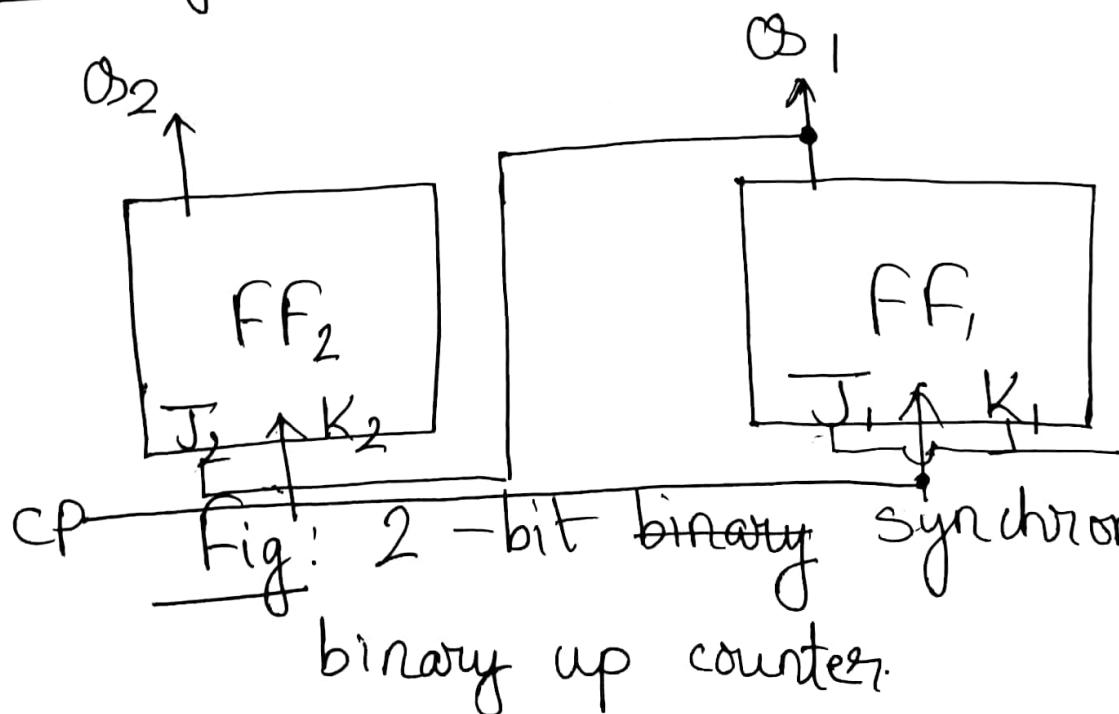

Chapter - 6

17/07/17

Design of Counters:

- Counter: A sequential ckt that goes through a prescribed sequence of states upon the application of input pulses is called a counter. A counter that follows the binary sequence is called a binary counter. An n bit binary counter consists of n FFs and can count in binary from 0 to $2^n - 1$.


- Example: Design a 2-bit binary up counter.

Solution:

Counting sequence:

0 → 1 → 2 → 3

State diagram:

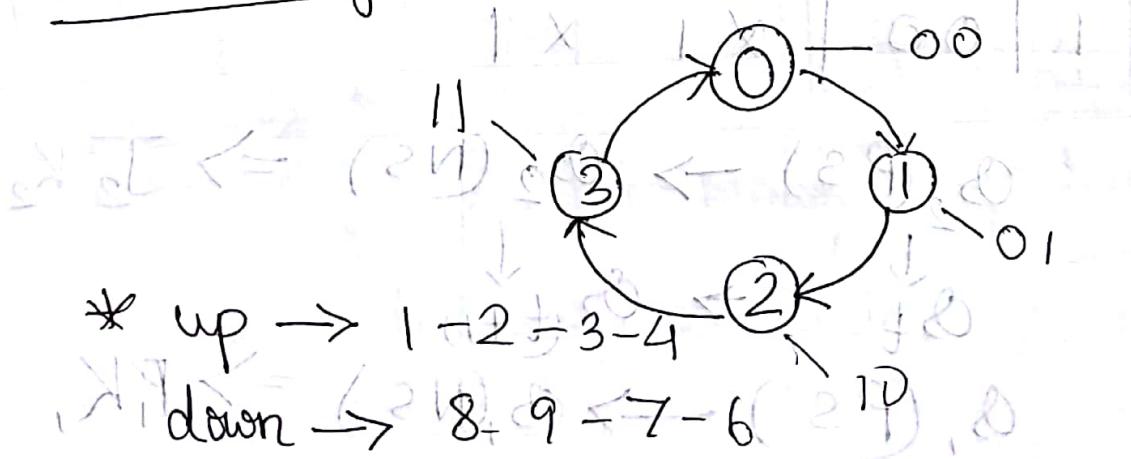

State table:

Present state (PS)		Next State NS	
Q_2	Q_1	Q_2	Q_1
0	0	0	1
0	1	0	0
1	0	1	1
1	1	0	0

Say, we will use 2 JK Flip flops

Excitation Map:

PS	NS	FF's Input
$Q_2 Q_1$	$Q_2 Q_1$	$J_2 K_2 \quad J_1 K_1$
0 0	0 1	0 X 1 X
0 1	1 0	1 X X 1
1 0	1 1	X 0 1 X
1 1	0 0	X 1 X 1

$$Q_2 (\text{PS}) \rightarrow Q_2 (\text{NS}) \Rightarrow J_2 K_2$$

$$Q_t \rightarrow Q_{(t+1)}$$

$$Q_1 (\text{PS}) \rightarrow Q_1 (\text{NS}) \Rightarrow J_1 K_1$$

FF's Input Equations:

based on present state

Q_2	0	0
	X	X

Q_2	0	0	1
	X	X	(X)
	0	0	1

Q_2	0	0	1
	(1)	1	X
	1	1	X

$$J_2 = Q_1$$

$$K_2 = Q_1$$


Q_2	0	0	1
	(X)	(X)	(X)
	0	0	1

Q_2	0	0	1
	X	(1)	(1)
	X	(1)	(1)

$$K_1 = 1$$

$$K_1 = 1$$

Logic Diagram:

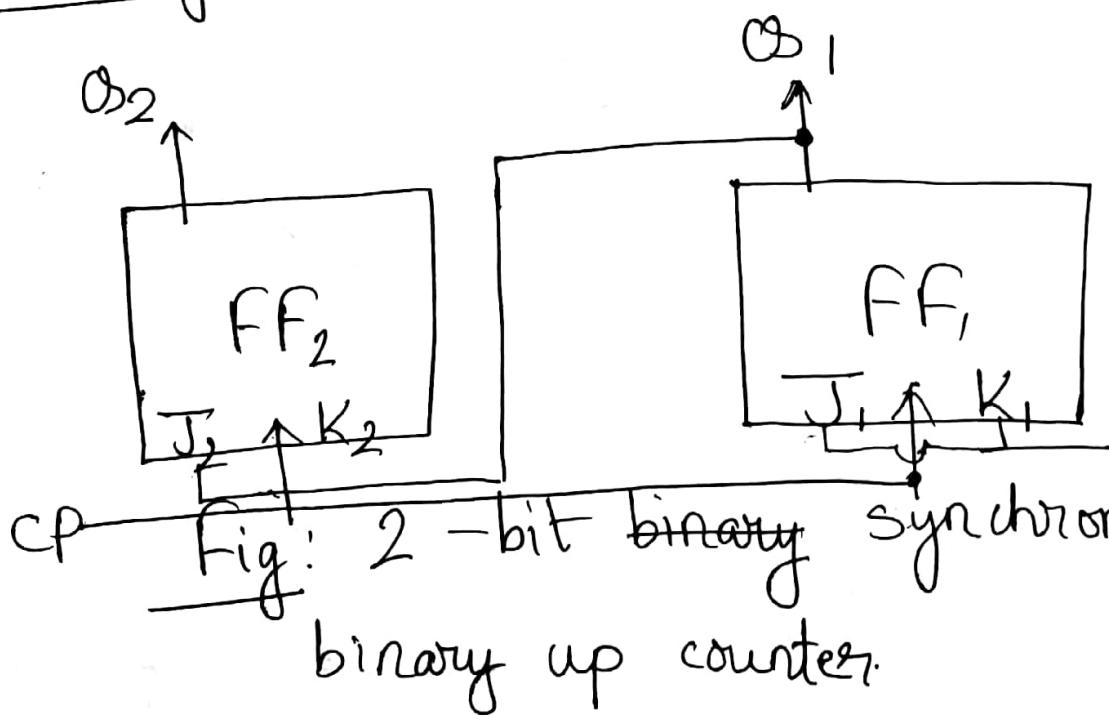

Exercises:

1. 2/3/4 bit synchronous binary up counter
2. 2/3/4 bit " " down "
3. 3 bit prime counter [2 - 3 - 5 - 7]
4. 3 bit / 4 bit odd counter
5. 3/4 bit even counter
6. Random counter

morphiD input

pol

↑

ok

↑

↑

↑

↑

↑

↑

↑

↑

↓↓↓↓↓↓↓↓↓↓

↓↓↓↓↓↓↓↓↓↓

↓↓↓↓↓↓↓↓↓↓


18/07/17

Binary Up-down Counter:


Design and implement 2-bit binary up-down counter.

Solution:


Counting sequence:

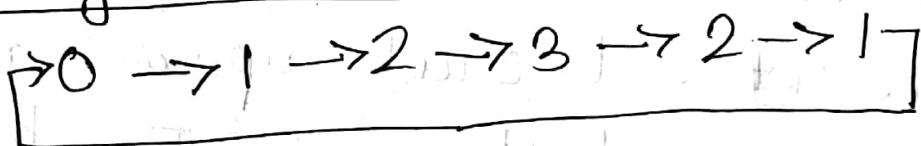

Upward count sequence:

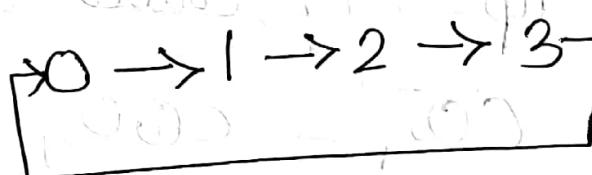

Downward count sequence:

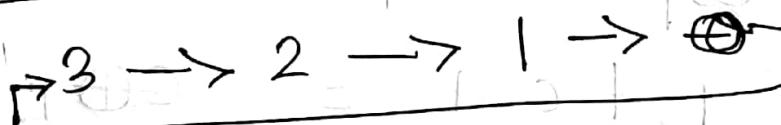

State table for upward count sequence:

Excitation map for upward count sequence:

FF's input equations for upward counts sequence

$$J_2 = Q_1, K_2 = Q_1, J_1 = 1, K_1 = 1$$

State table of excitation to map for downward count sequence:

FF's input equations for downward counts:

$$J_2 = \bar{Q}_1'; K_2 \bar{Q}_1 = Q_1'; J_1 = 1, K_1 = 1$$

Say, we have a control variable C and if $C=0$, our ckt will count upward and if $C=1$, our ckt will count downward. Then the final equations of our up-down counter will be:

$$J_2 = \bar{C}Q_1 + C\bar{Q}_1 = C \oplus Q_1$$

$$K_2 = \bar{C}Q_1 + C\bar{Q}_1 = C \oplus Q_1$$

$$J_1 = \bar{C} \cdot 1 + C \cdot 1 = C \oplus 1, C + C = 1$$

$$K_1 = \bar{C} \cdot 1 + C \cdot 1 = \bar{C} + C = 1$$

Logic Diagram:


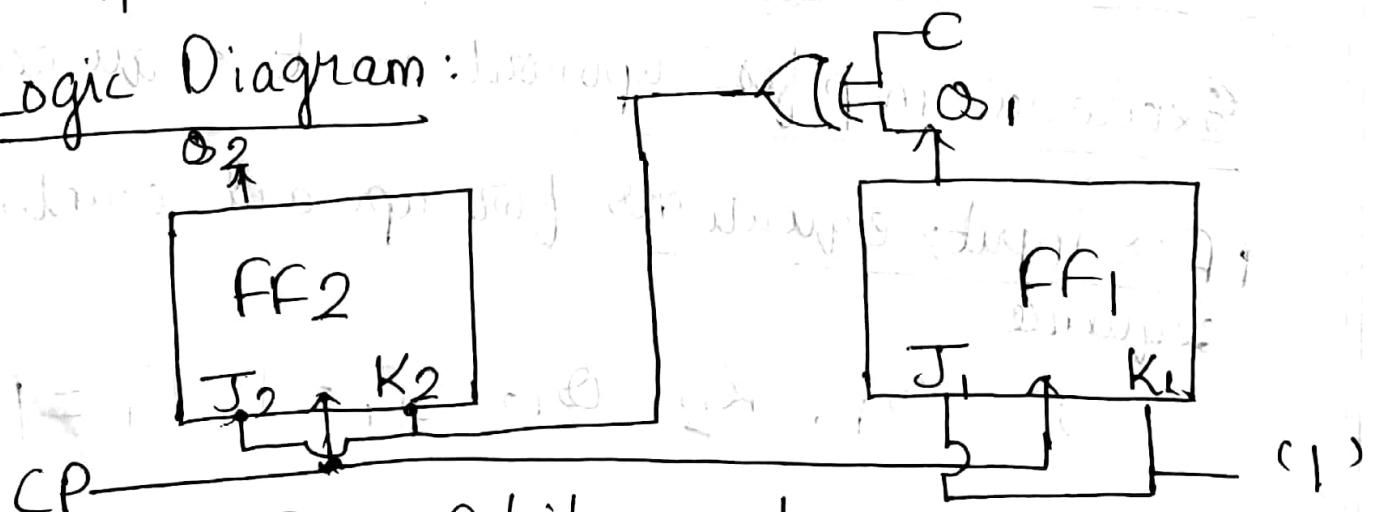


Fig: 2 bit up down counter

Timing diagram:

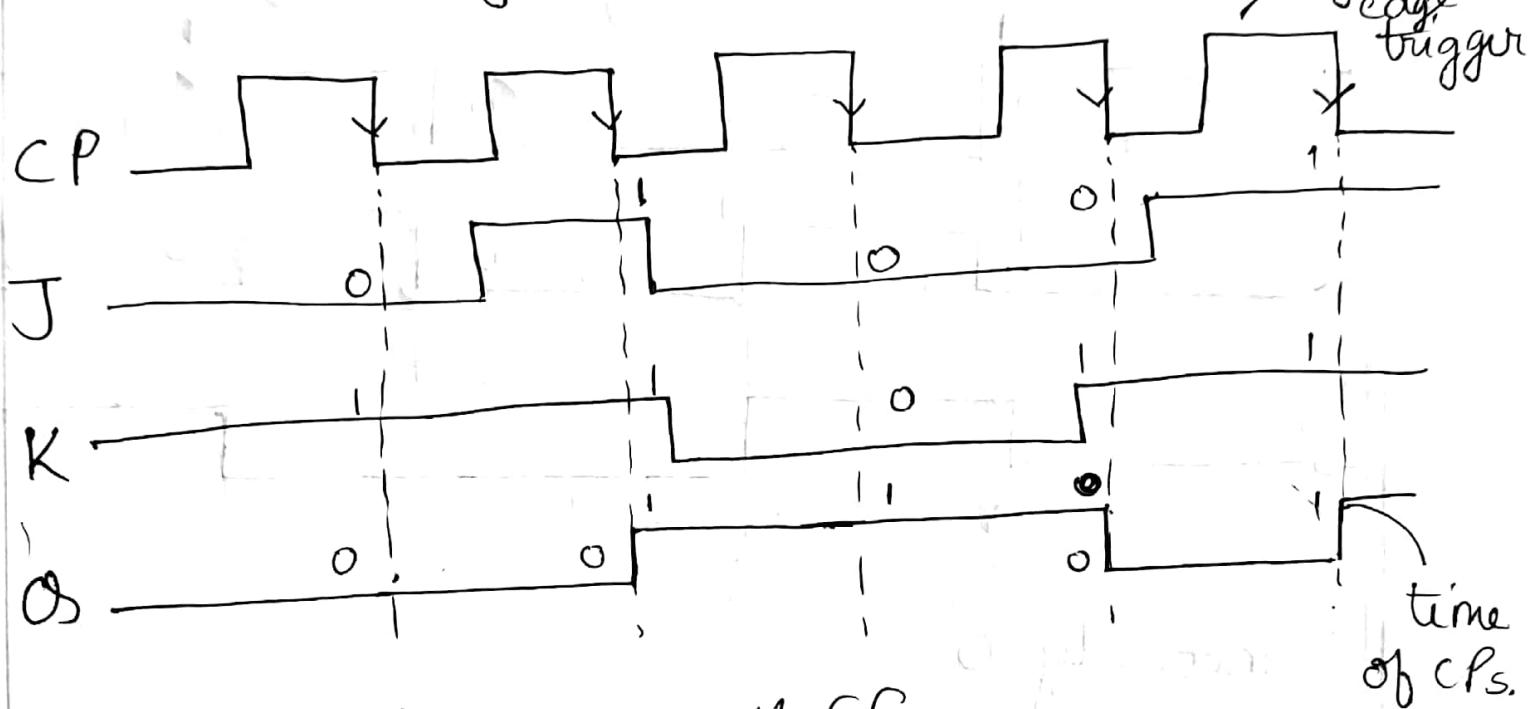Find the timing diagram for Q. (5 clock pulses)




Truth table of JK FF:

J	K	Q _{t+1}
0	0	Q _t
0	1	0
1	0	1
1	1	Q' _t

Quiz #4 upto here
25/07/'17

Q: 1 → 0 ⇒ output changes


Let Q's initial value = 0

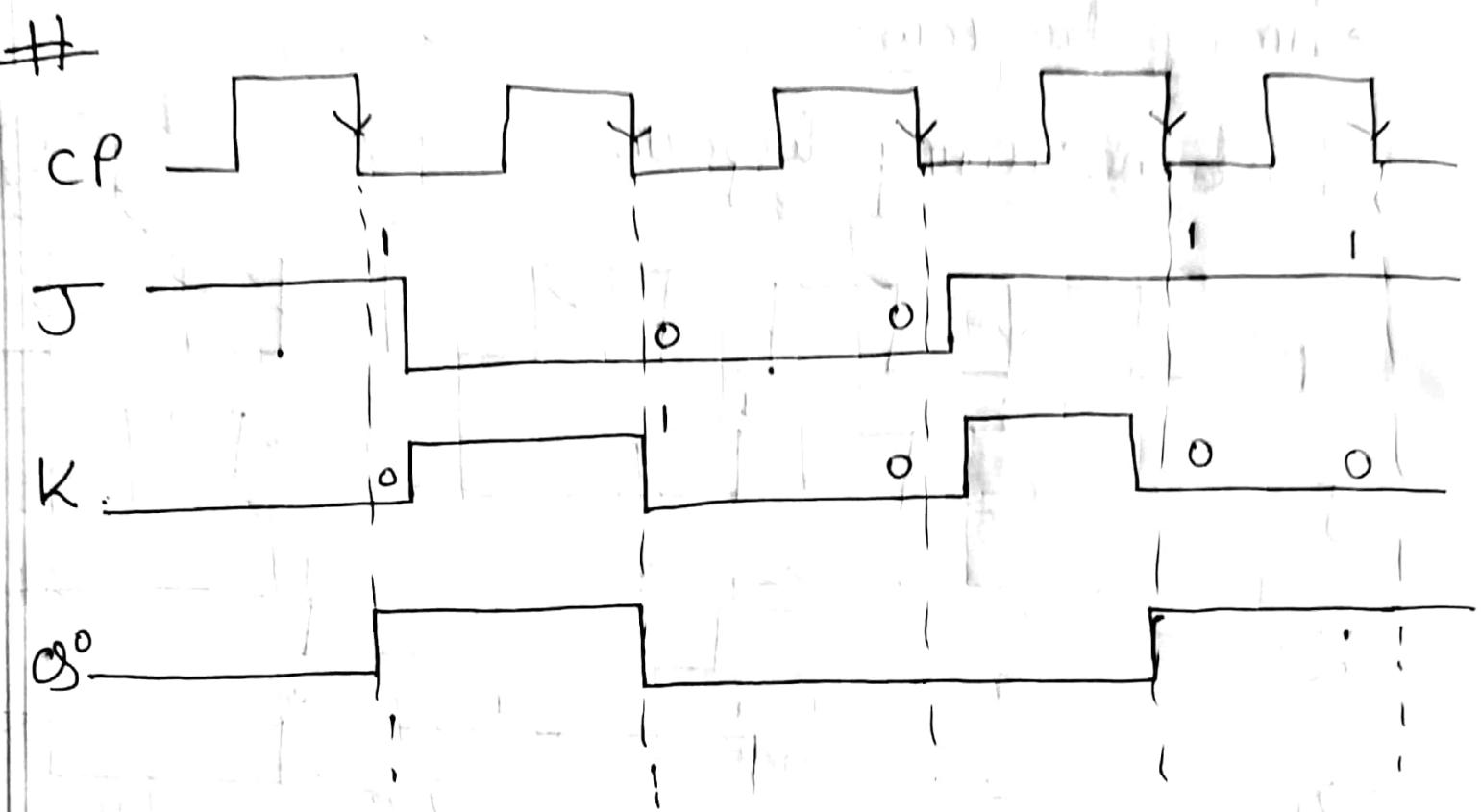

Q initially 0

23/07/17

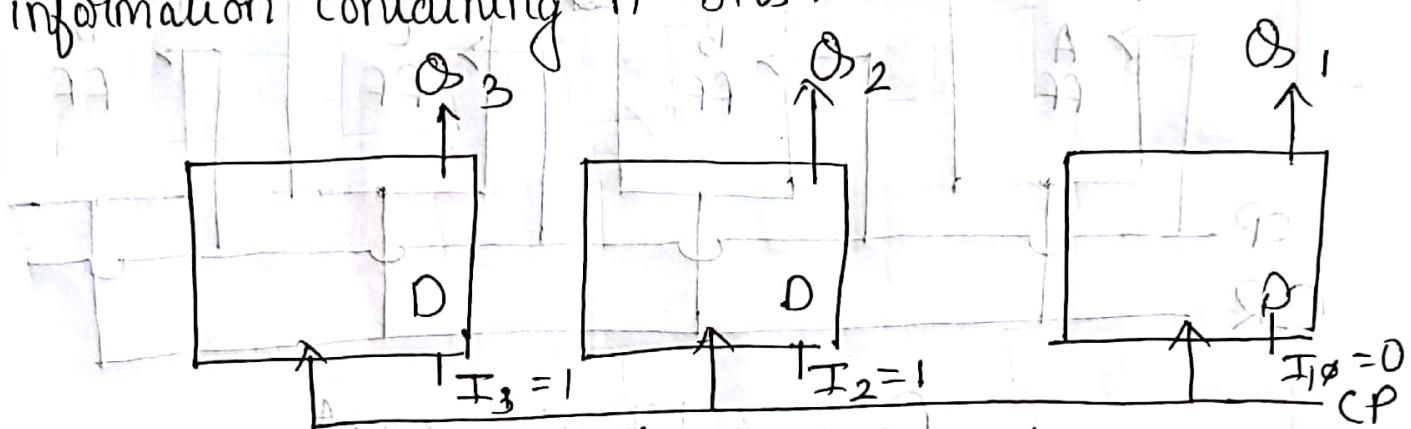Register - A n-bit register has a group of n FFs and is capable of storing any binary information containing n-bits.



D FF, Input = Output

Fig: 3 bit register.

Register with parallel load: Self study

Shift register:

0	0	0	1
0	0	1	0
0	1	0	0

A register capable of shifting its binary information either to the right or to the left is called a shift register.

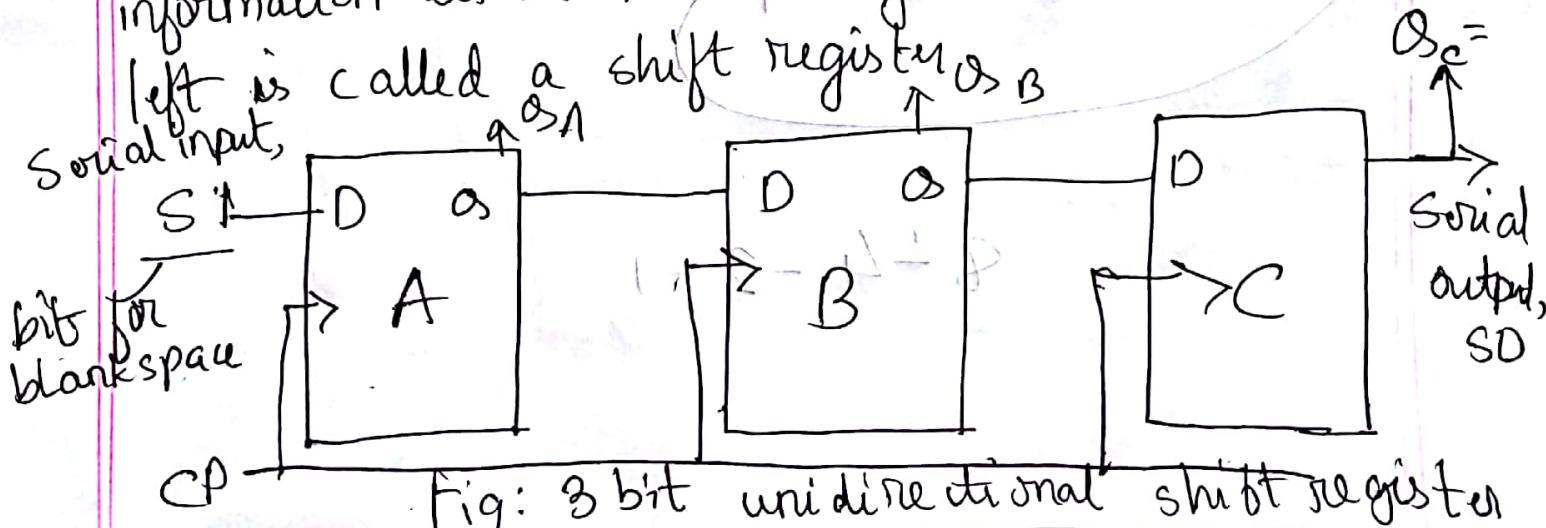


Fig: 3 bit unidirectional shift register


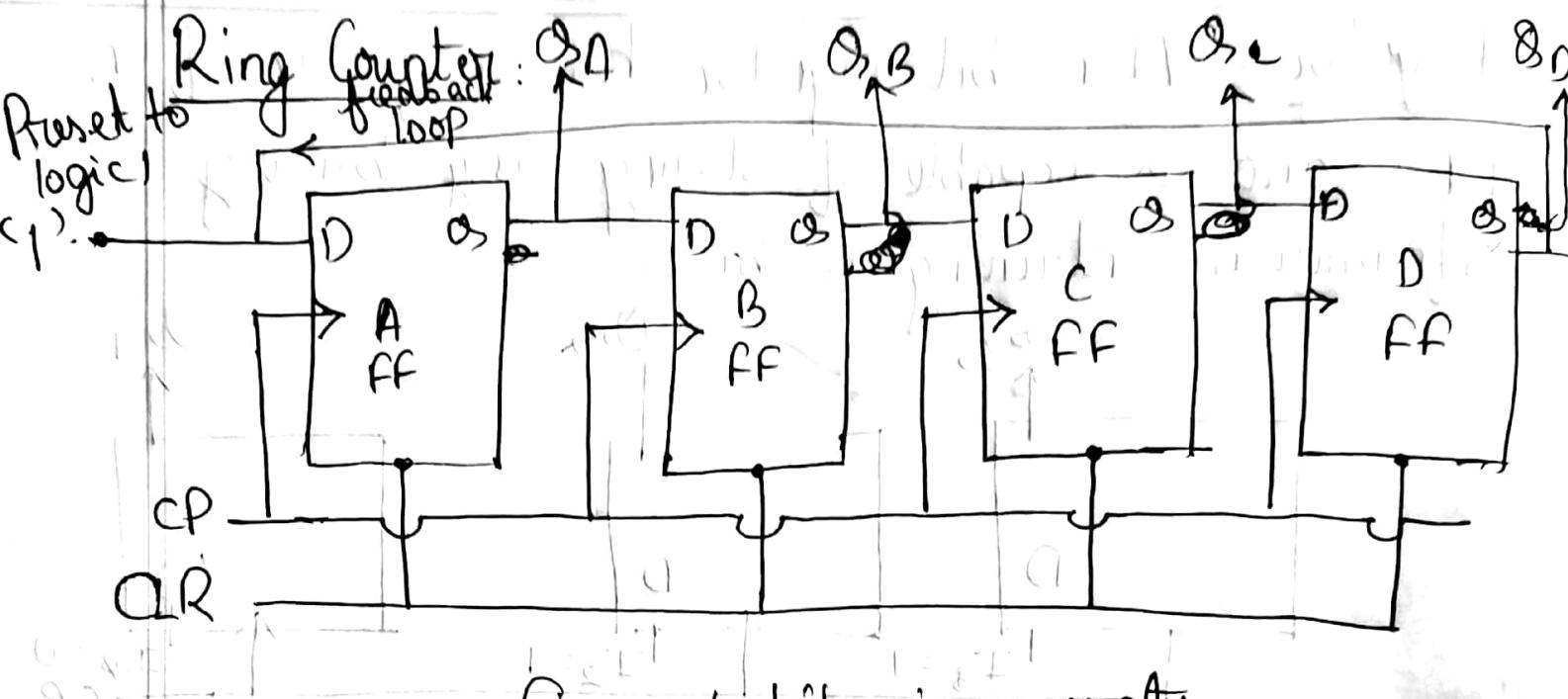


Fig: 4 bit ring counter
Counting sequence.

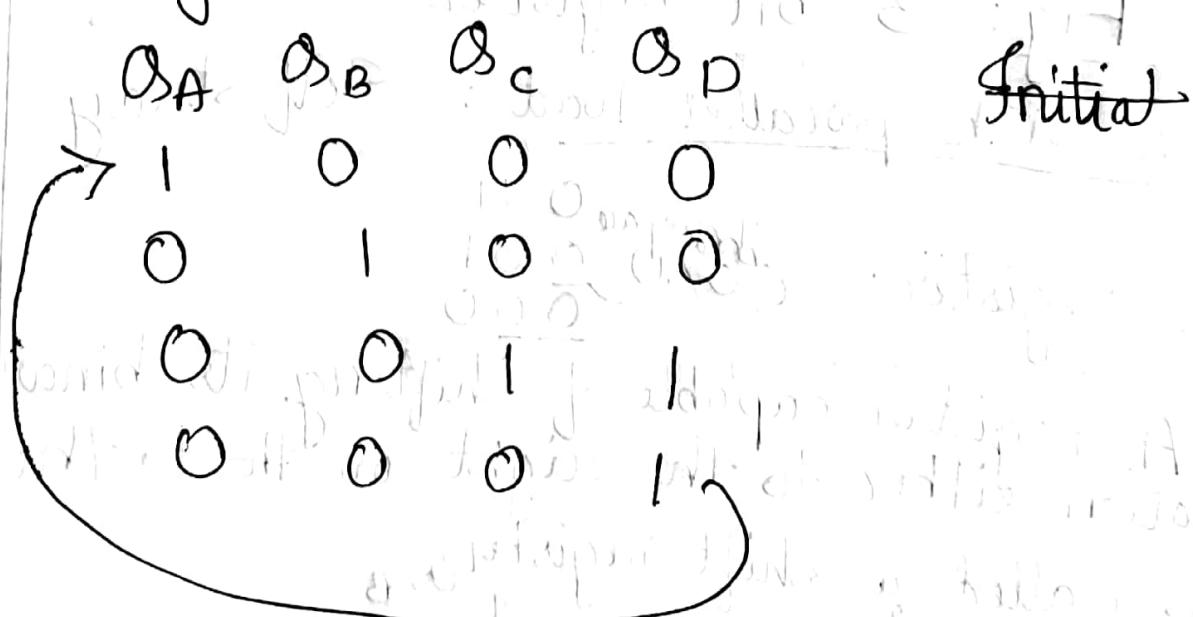

8 - 4 - 2 - 1

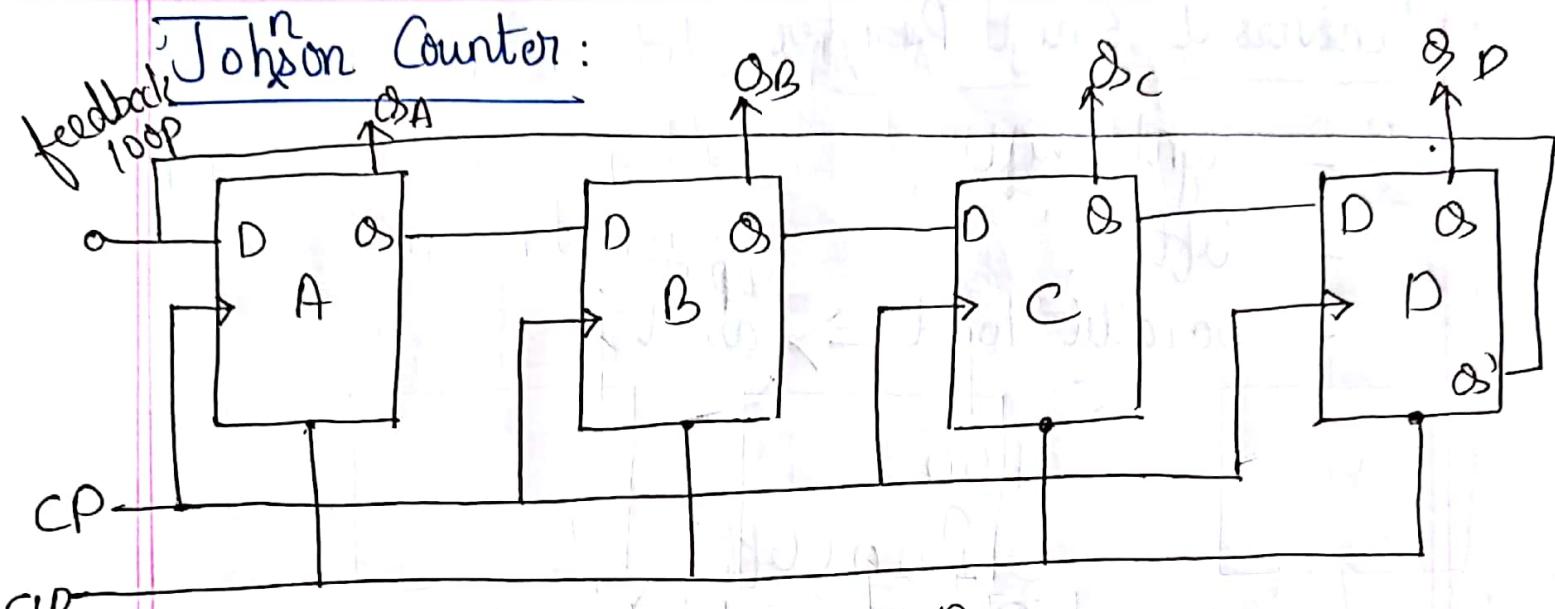


Fig: 4 bit Johnson counter

Counting sequence:

Q_A	Q_B	Q_C	Q_D
0	0	0	0
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1
0	0	0	0

Difference of J counter from R counts :-

feedback is Q' , not Q .

0 - 8 - 12 - 14 - 16 - 7

- 3 - 1

30/07/17

Universal Shift Register

- right shift

left

parallel load \Rightarrow input as it is.

100 |

0100 (left)

0010 (right)

4x1 Mux -

00

No change

01

Shift right

10

Shift left

11 Parallel load

4-bit Universal Shift Register:

(L-R) all selectors short

00

00 - I_0 - whatever is given in input

\Rightarrow output A_3

$$00 \Rightarrow I_0 - A_2$$

output - A_2

$$00 \Rightarrow I_0 - A_1$$

output - A_1

$$00 \Rightarrow I_0 - A_0$$

output - A_0

(L-R) :: All values same as before (A_3, A_2, A_1, A_0)

01 $\Rightarrow I_1 \Rightarrow A_3, A_2, A_1$ serial input (bit for shifting)
0/1 eq: 0
Output $\Rightarrow 0$ (instead of A_3)

$$01 \Rightarrow I_1 \Rightarrow A_3$$

Output $\Rightarrow A_3$ (instead of A_2)

$$01 \Rightarrow I_1 \Rightarrow A_2$$

O/P $\Rightarrow A_2$ (instead of A_1)

$$01 \Rightarrow I_1 \Rightarrow A_1$$

O/P $\Rightarrow A_1$ (instead of A_0)

$\therefore O/P \Rightarrow 0 A_3 A_2 A_1$

10

$A_2 A_1 A_0$

$I_2 (R \rightarrow L)$

$I_2 \Rightarrow 0$ (serial input)

$O/P \Rightarrow 0$

$I_2 \Rightarrow A_0$

$O/P \Rightarrow A_0$

$I_2 \Rightarrow A_1$

$O/P \Rightarrow A_1$

$I_2 \Rightarrow A_2$

$O/P \Rightarrow A_2$

$A_2 A_1 A_0 0$

11

all $I_3 \Rightarrow$ switch variable.

$I_3 \Rightarrow$ whatever given in switch var.

$I_3 I_2 I_1 I_0 = A_3 A_2 A_1 A_0$

Asynchronous / Ripple Counter:

Synchronous \Rightarrow common pulse

Asynchronous \Rightarrow one pulse, rest CP \rightarrow output of prev.

Negative edge trigger $\rightarrow 1 \rightarrow 0$

Positive " " $\rightarrow 0 \rightarrow 1$

31/07/17

• MOD Counter:-

- It is a counter that skips a certain number of steps that we set. For this, we have to force counter to recycle before going through all of the states in the binary sequence. MOD - N counter can count 0 to $N-1$.

Example : MOD - 6 Counter:

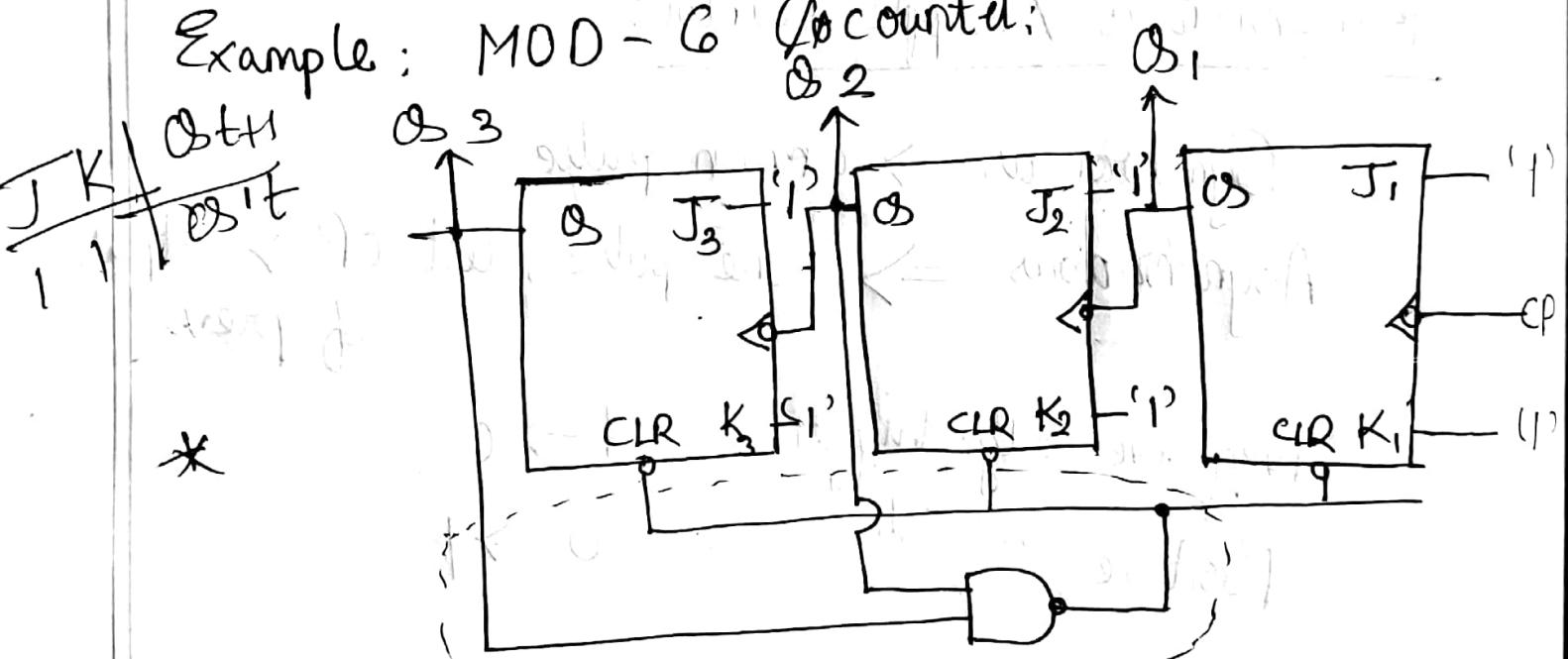


Fig : MOD - 6 Counter

• DBCD Ripple Counter:

MOD - 10 Counter

: can count 0 to 9

0-1 : No CP (since we
1-0 : CP edge)

	θ_3	θ_2	θ_1
1	0	0	0
2	0	0	1
3	0	1	0
4	0	1	1
5	1	0	0
6	1	0	1
7	1	1	0
8	X	1	0
9	X	1	1

CP \rightarrow value changes

No CP \rightarrow value same as prev.

counts 0-7 without dotted counts part

- To make 0-5, dotted part is needed to recycle.

- After 5, FF has to be cleared. (i.e. when C₆)

- 110 : $\theta_3 = \theta_2 = 1$ (only when C₆) No combinations

before this has both θ_3 and θ_2 as 1.

\therefore NAND gate : both input 1, output 0.

CLR : clears the FF.

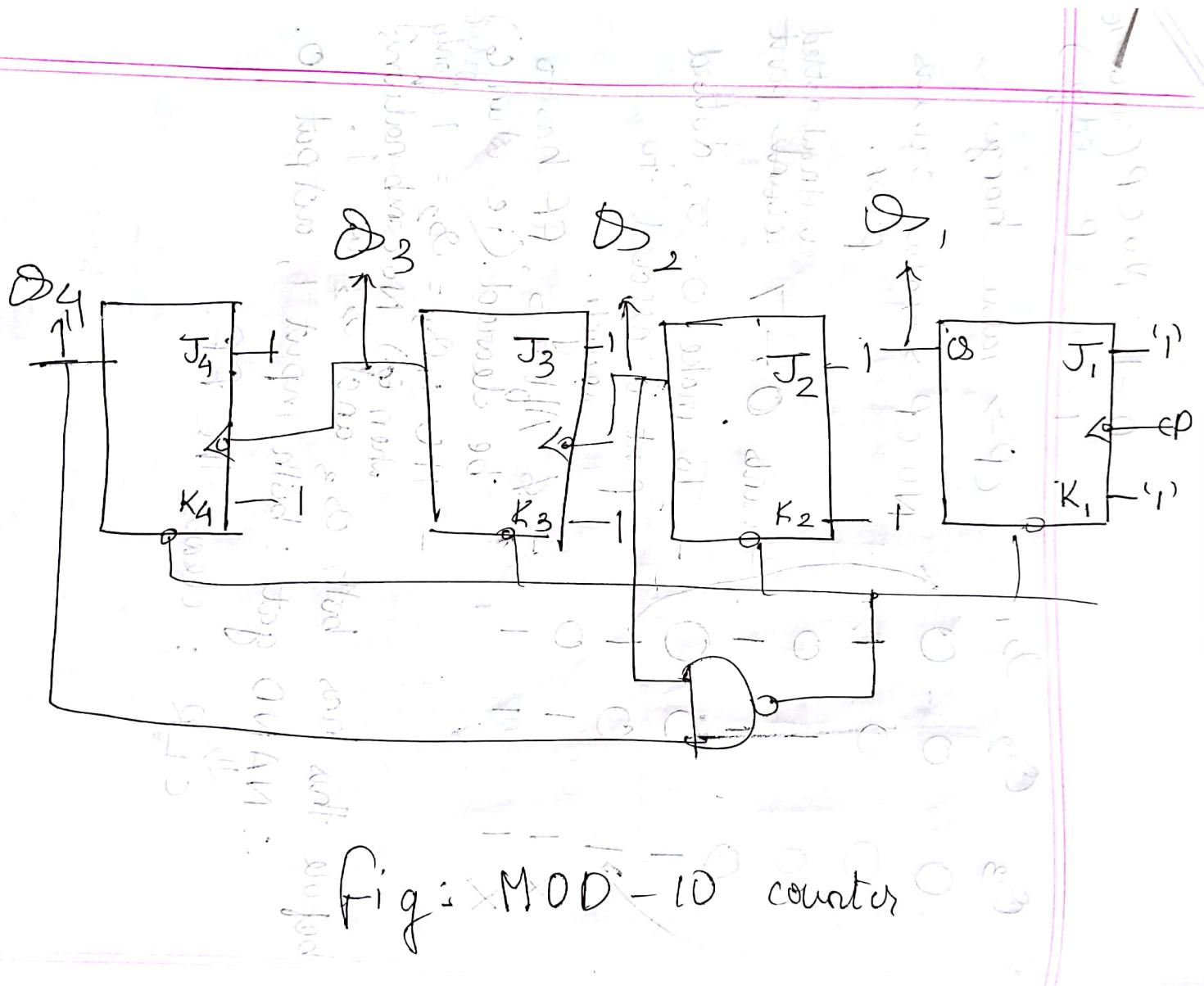


Fig: MOD-10 counter

Q_4 Q_3 Q_2 Q_1

0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

BCD counter IC: decade
counter.

I can count 0-9
i.e. has 4 FF.

Practice:

MOD 100 ✓

MOD 75 ✓

b) using 4×1 Mux :-

Implementation table :- $I_A' + I_B = F$

	I_0	I_1	I_2	I_3
A'	0	①	2	③
A	4	⑤	⑥	7


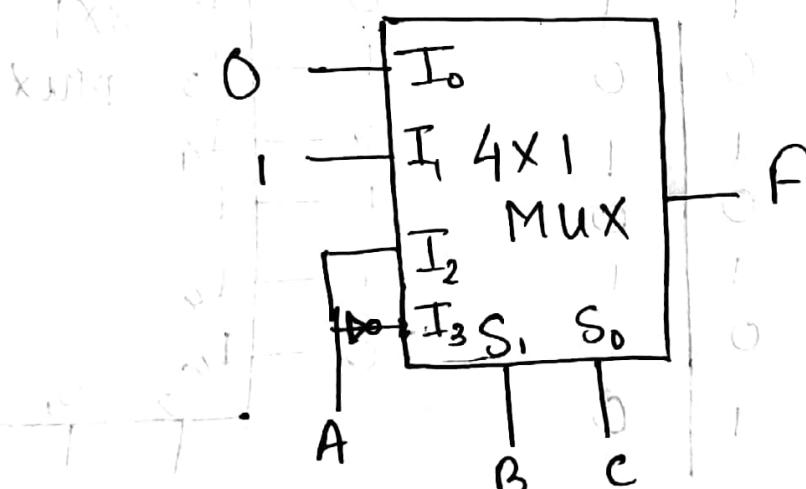


Fig:- using 4×1 Mux

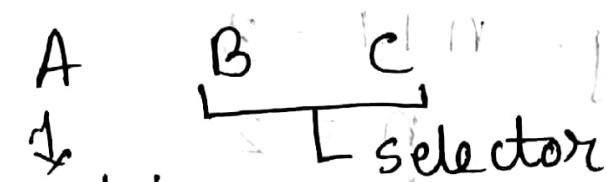* When a small sized Mux is used, then all inputs can't be connected in selectors. Then,



how it is used in 1×8 :-
input line


Boolean Function implementing using Mux:-

Implement $F(A, B, C) = \sum(1, 3, 5, 6)$ using

a) 8×1 MUX

b) 4×1 MUX

Solution :-

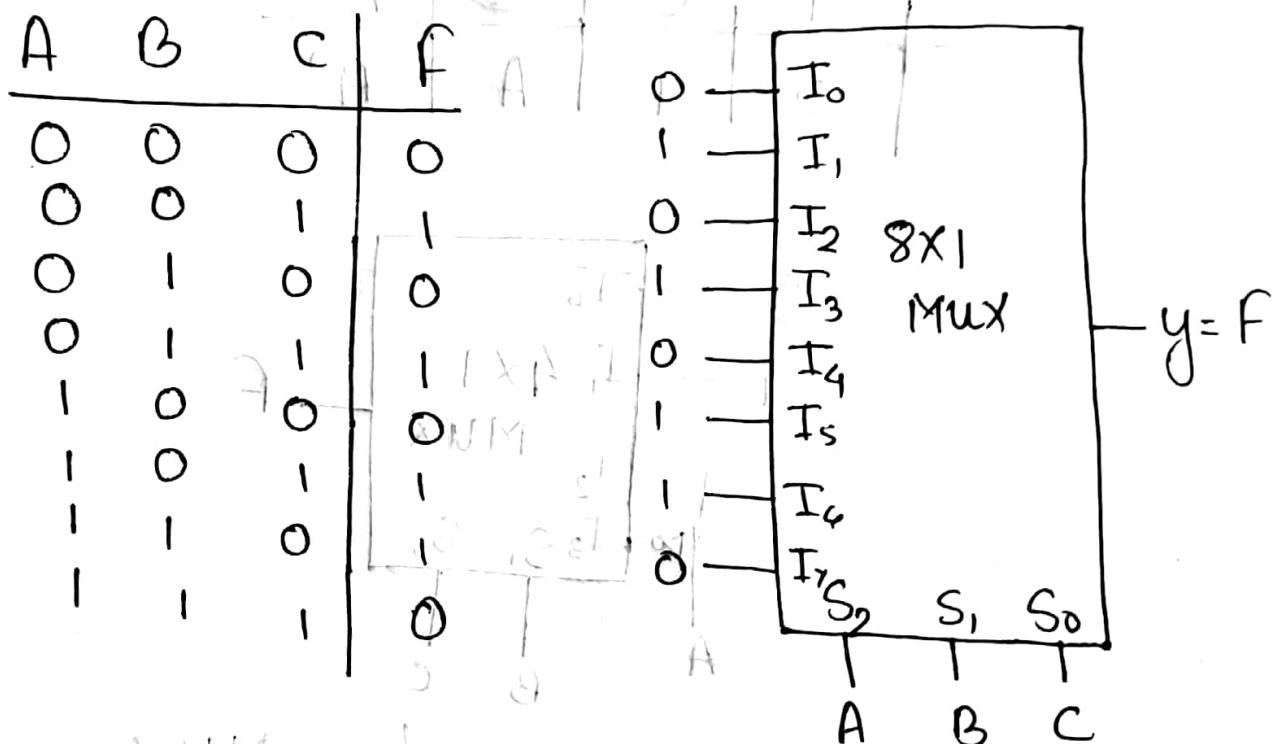

* If no. of input variable = $n+1$, a) using 8×1

use $2^n \times 1$ MUX.

$$\text{Eg: } n+1 = 3$$

$$\therefore n = 2$$

$\therefore 2^n \times 1 = 4 \times 1$ MUX used

Demultiplexer :-

Input line : 1

Output line : 2^n

Selectors : n

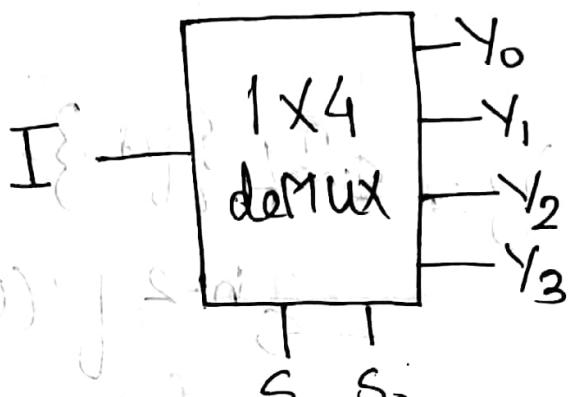


Fig : 1x4 deMux

Function table:

S_1	S_0	Y_0	Y_1	Y_2	Y_3
0	0	I	-	-	-
0	1	-	I	-	-
1	0	-	-	I	-
1	1	-	-	-	I