
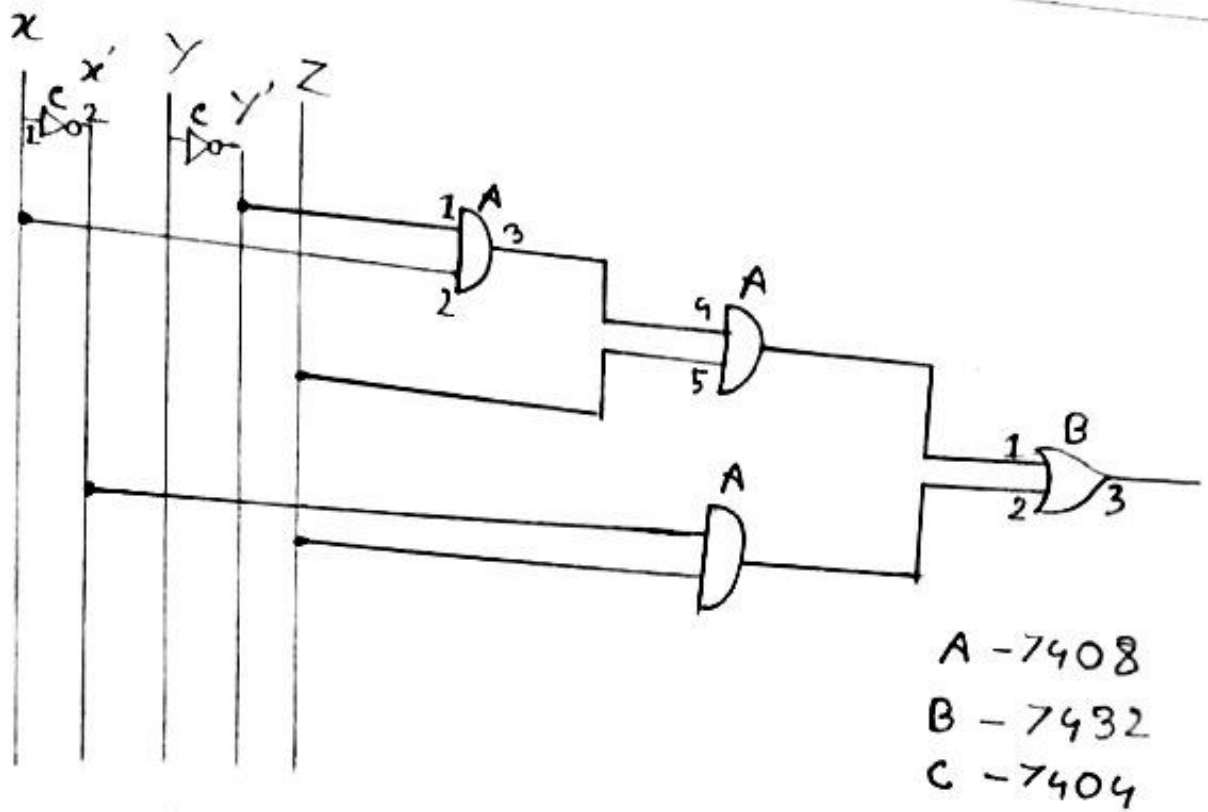


$$f_2 = xy'z + x'y'z$$

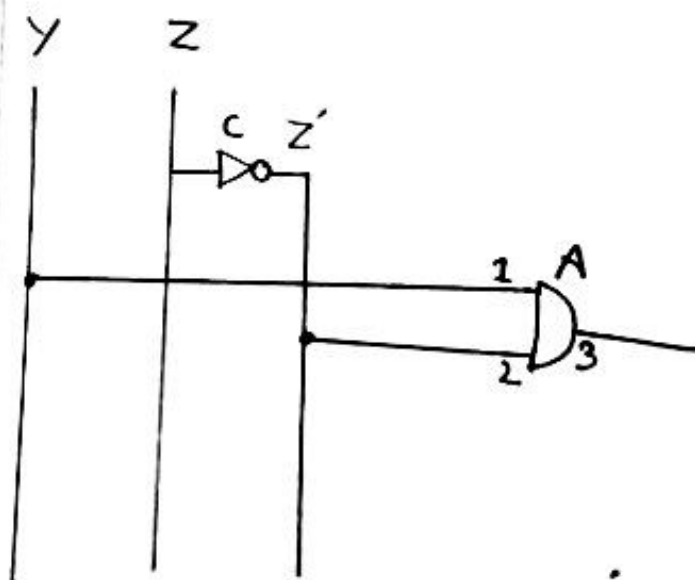


$$iii) f_3 = (xy + x'y)z'$$

$$= yz'$$




## Implementation of Basic gates:


AND chip IC:

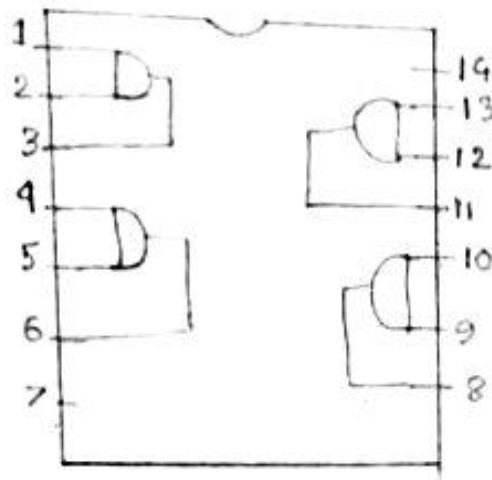

OR chip IC:

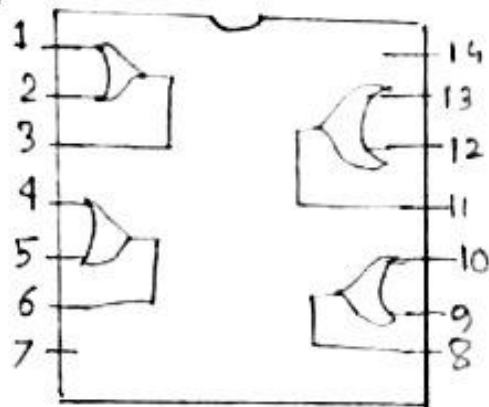

NOT chip IC:

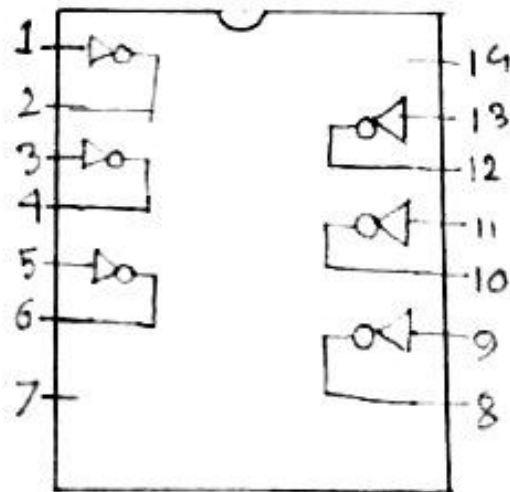

Truth Table.

$x$	$y$	$z$	$x'$	$y'$	$z'$	$xy$	$x'y$	$x'z$	$yz$	$xy/z$	$xy+xy$	$f_1 = x+yz$	$f_2 = xy/z+x'z$	$f_3 = (xy+x'y)z$
0	0	0	1	1	1	0	0	0	0	0	0	0	0	0
0	0	1	1	1	0	0	0	1	0	0	0	0	1	0
0	1	0	1	0	1	0	1	0	0	0	1	0	0	1
0	1	1	1	0	0	0	1	1	1	0	1	1	1	0
1	0	0	0	1	1	0	0	0	0	0	0	1	0	0
1	0	1	0	1	0	0	0	0	0	1	0	1	1	0
1	1	0	0	0	1	1	0	0	0	0	1	1	0	1
1	1	1	0	0	0	1	0	0	1	0	1	1	0	0

Output expression:


$$\begin{aligned} \text{i) } f_1 &= x + yz \\ &= x + yz \end{aligned}$$

$$\begin{aligned} \text{ii) } f_2 &= xy'z + x'z \\ &= xy'z + x'z \end{aligned}$$

$$\begin{aligned} \text{iii) } f_3 &= (xy + x'y) \cdot z' \\ &= (x + x')y \cdot z' \\ &= 1 \cdot y \cdot z' \\ &= z'y \end{aligned}$$

Block Diagram:

$$\text{i) } f_1 = x + yz$$

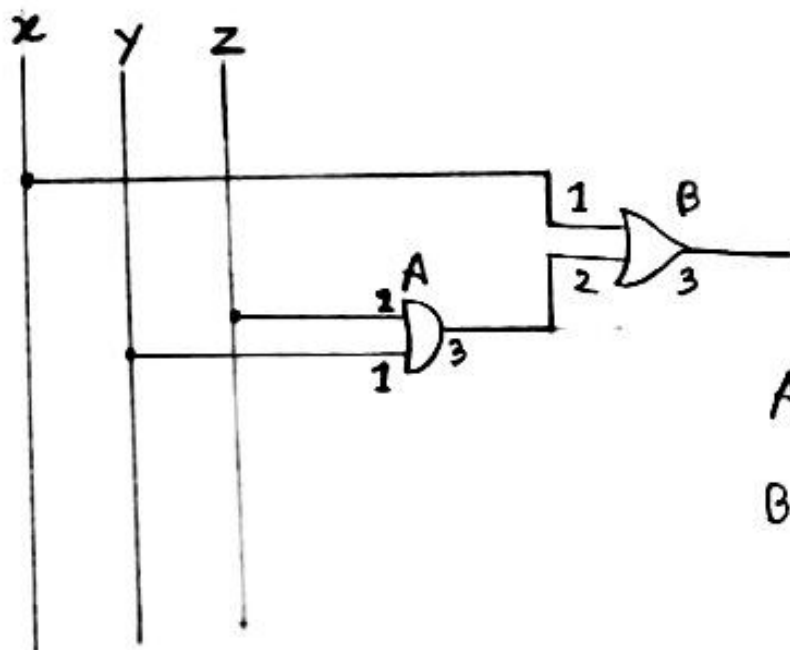

A = 7908

B = 7432

Name of the experiment:

Implimentation of simple function:

$$i) f_1 = x + yz$$

$$ii) f_2 = xy'z + x'z$$

$$iii) f_3 = (xy + x'y)z'$$

Objective:

Implimenting the given boolean function using basic logic gates. Also, if possible, simplified the given function to minimize the total cost.

Instrument:

i) AND chip IC - 1 piece (IC-7408)

ii) OR chip IC - 1 piece (IC-7432)

iii) NOT chip IC - 1 piece (IC-7404)

iv) Wires

v) Bread-board

OR Gate:

X	Y	F
0	0	0
0	1	1
1	0	1
1	1	1

Output Expression:

AND Gate:

$$F = x \cdot y$$

NOT Gate:


$$F = \bar{x}$$

OR Gate:

$$F = x + y$$

Block Diagram:

i) AND Gate:

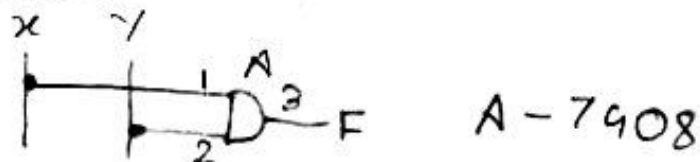

ii) NOT Gate



iii) OR Gate



Name of the Experiment: Implementation of the basic gates.

Objective:

The objective of the experiment is to understand how the basic boolean logic gates work and to implement them in digital lab.

Instrument:

- i) AND chip IC - 1 piece (IC-7408)
- ii) OR chip IC - 1 piece (IC-7432)
- iii) NOT chip IC - 1 piece (IC-7404)
- iv) Wires

Truth Table:

AND Gate

X	Y	F
0	0	0
0	1	0
1	0	0
1	1	1

NOT Gate

X	F
0	1
1	0